

ITSS

24th International Travelling Summer School on Microwaves and Lightwaves  
5-11 July 2014, Copenhagen, Denmark




# High Speed 12-bit Arbitrary Waveform Generator (AWG)

**André Ehlert**  
Ph.D.-Student

**Terahertz Photonics – Institute of Physics**  
**Goethe University Frankfurt am Main**

# Previous Work - Initial Point

Block diagram of the DDS

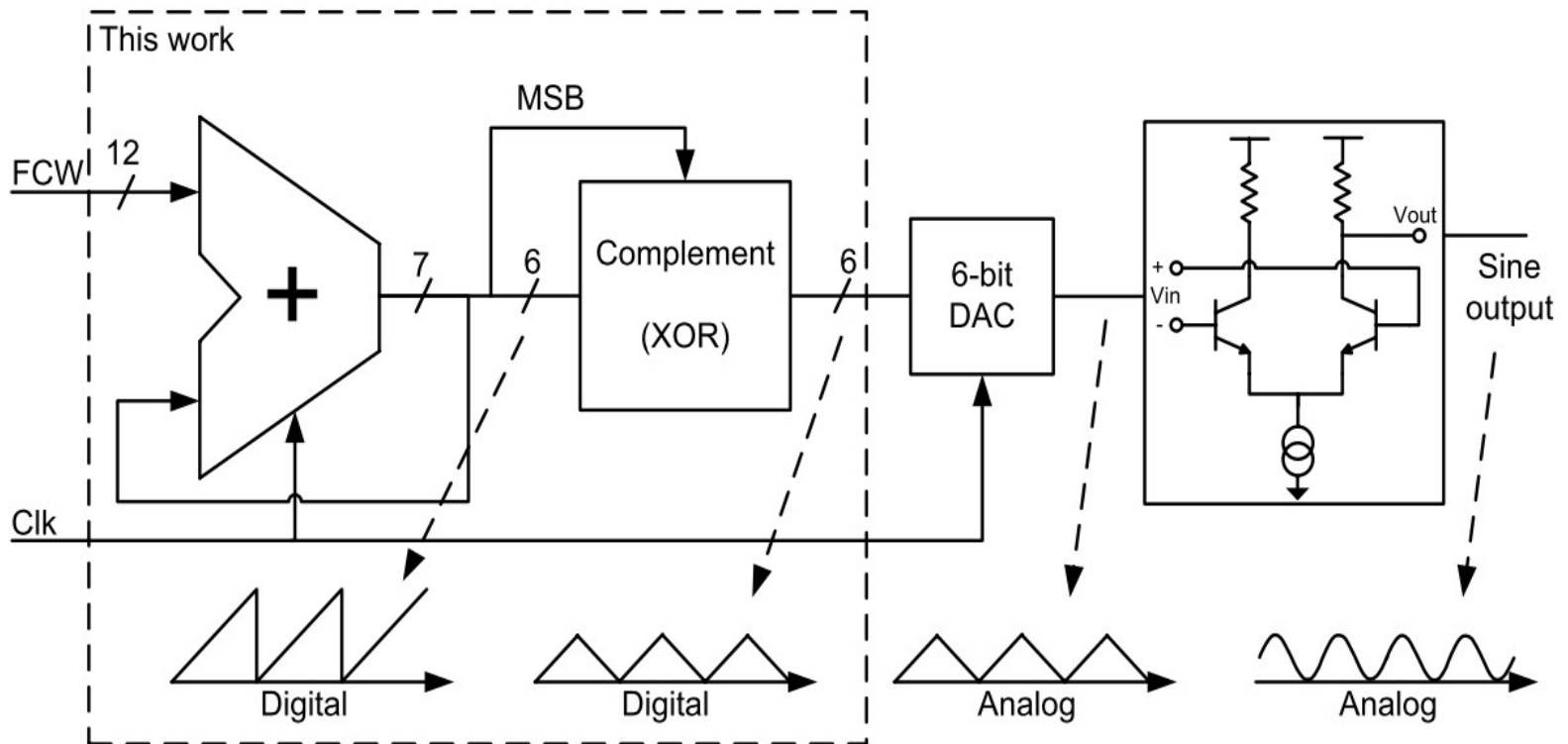



# Goals

## Enhancement of the accumulator

- Reduction of the power consumption (currently: ~1W)
- Providing a **Phase Control Word** (PCW) makes it possible to manipulate the phase of the output signal while the system is running
- Secondary: increasing the clock frequency (currently: 20GHz)


## Bringing together the accumulator and the DAC on one chip

- IHP from Frankfurt (Oder) provides a 6-bit DAC that can be used as a „black box“
- In the previous work the accumulator was a separate chip


# Current State - Accumulator

- In order to reduce the number of stages within the pipeline we can conflate each couple of 1-bit-adders to one new 2-bit-adder

1-bit-adder

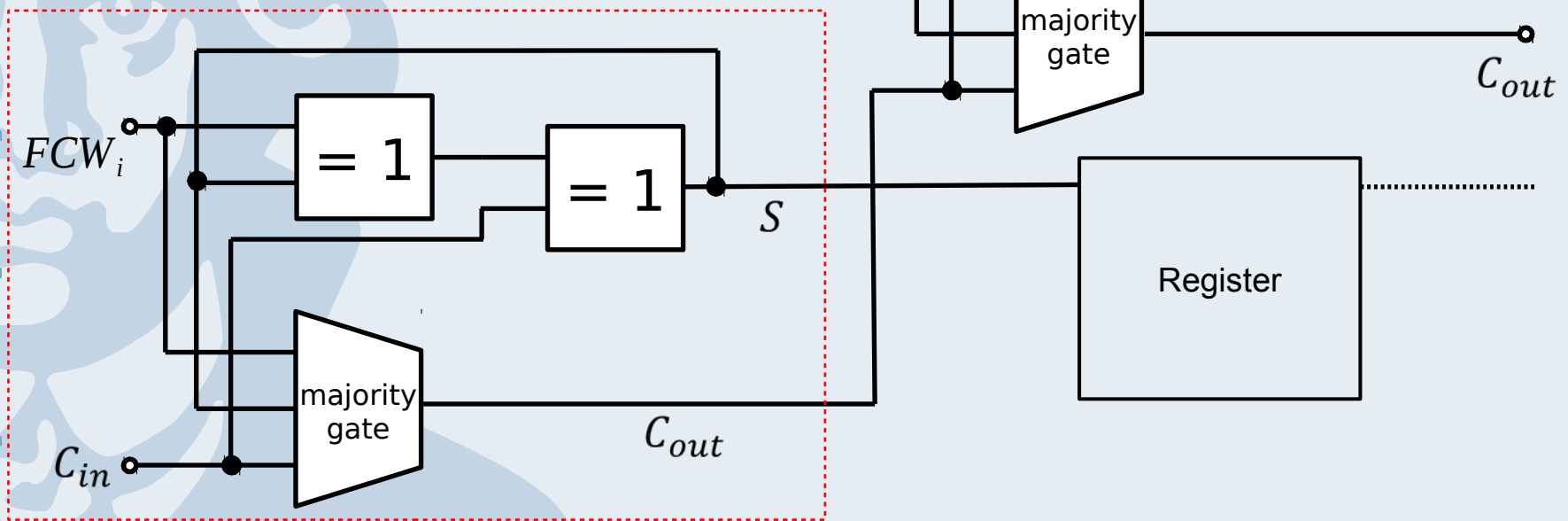

# Current State - Accumulator

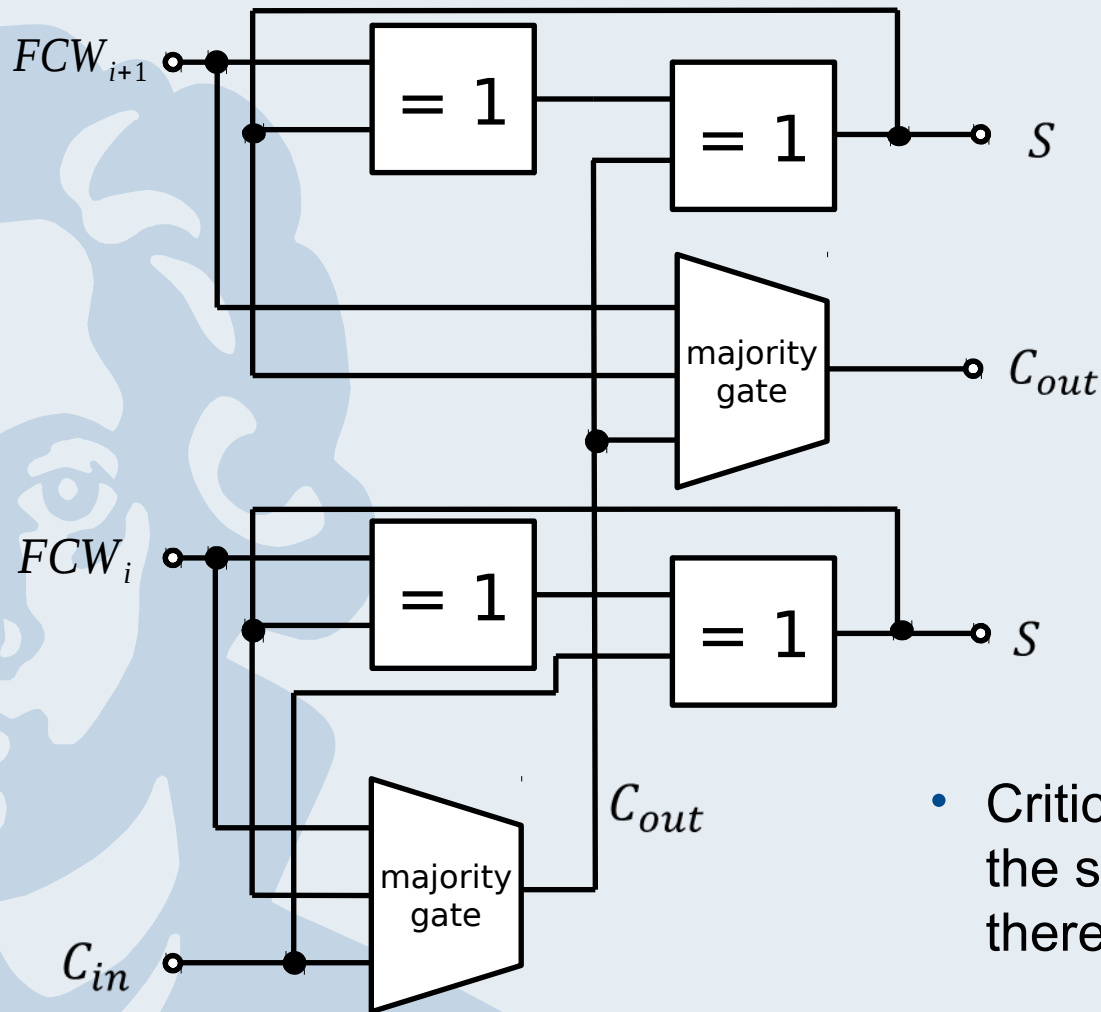


2-bit-adder

- Critical path length remains the same (2 gates), thus there's no loss in speed

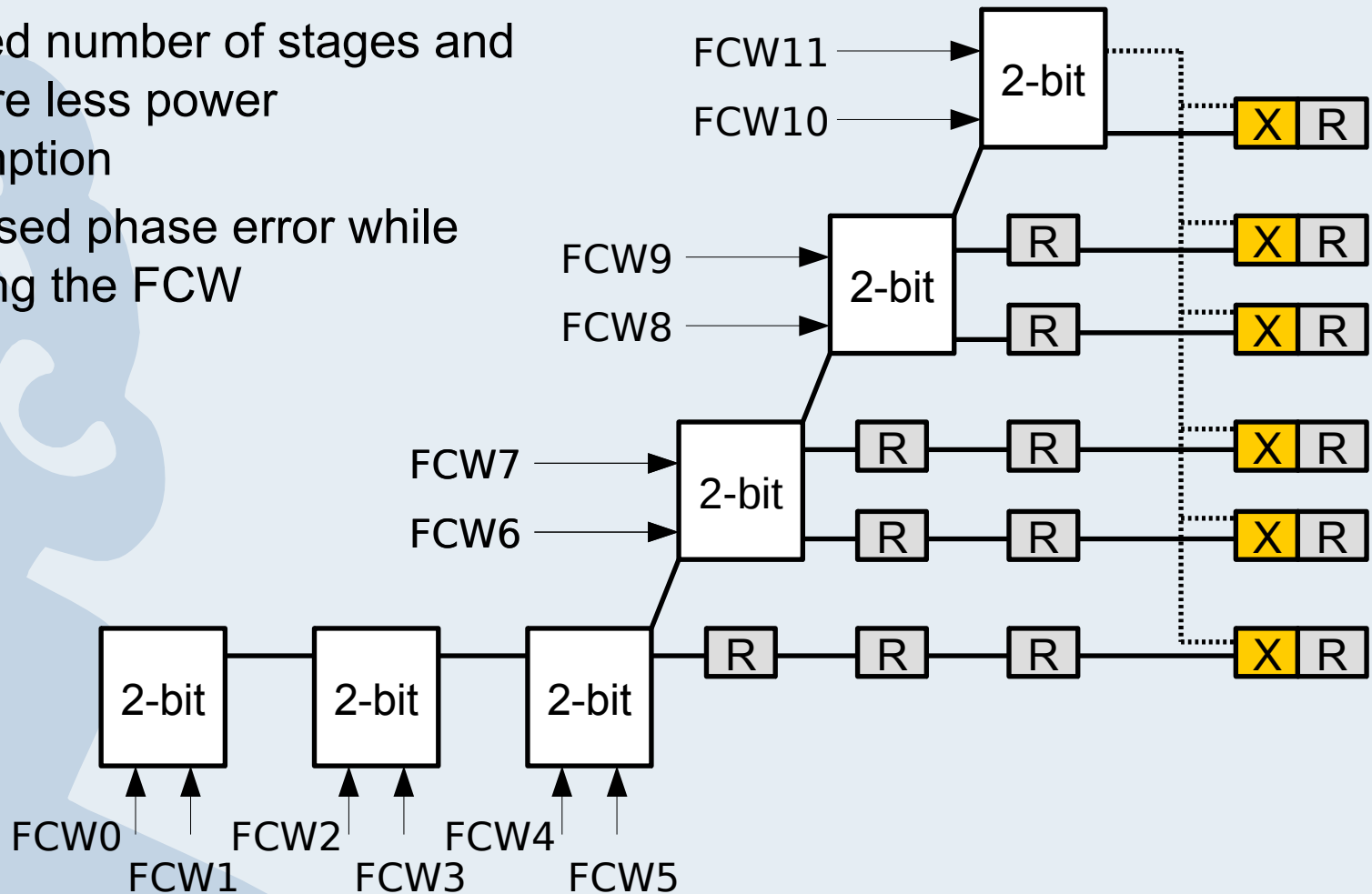
# Current State - Accumulator

- Reduced number of stages and therefore less power consumption
- Decreased phase error while switching the FCW


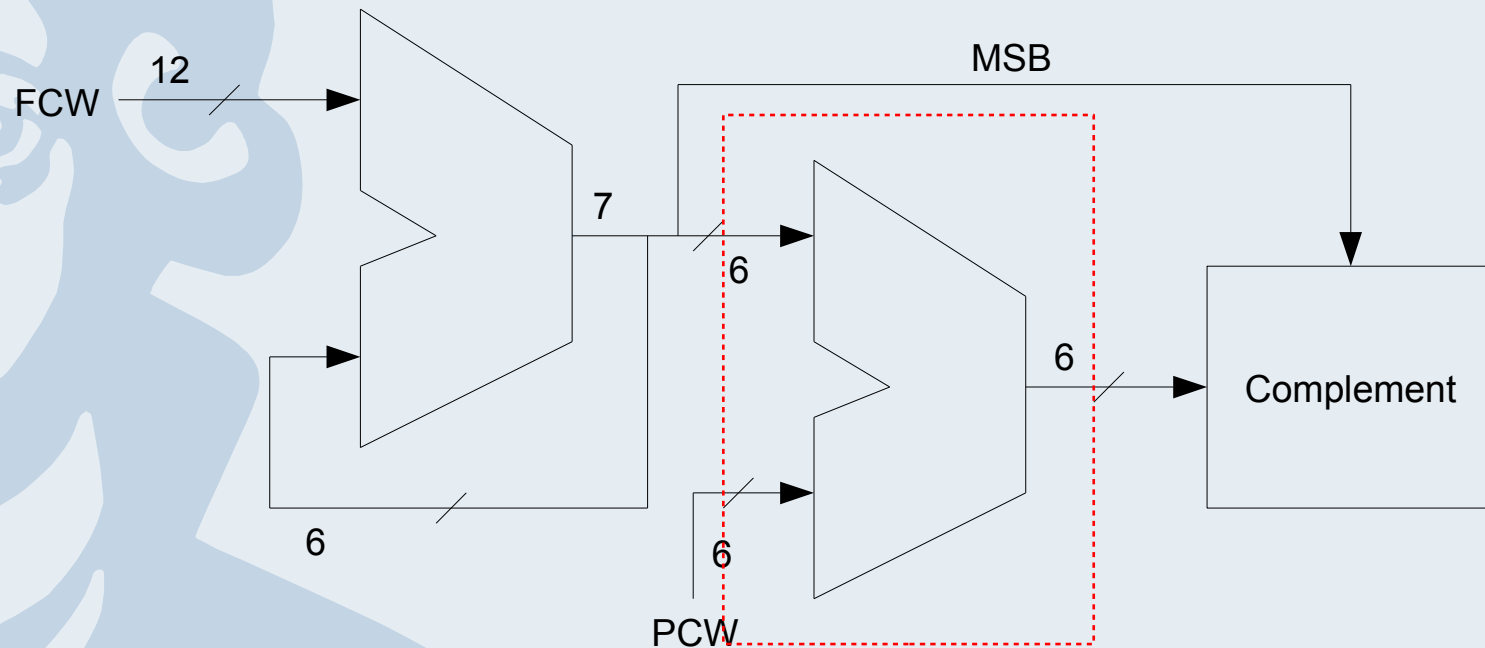
# Current State - Accumulator


- In order to provide a PCW, it's necessary to include further adders within the DDS
- This way the DDS becomes an **Arbitrary Waveform Generator (AWG)**




 
# Current State - Accumulator

- Further important issue: clock distribution
- At high frequencies it's necessary to control the clock skew very carefully
- Therefore a H-Tree structure is used to ensure that the signal path length from the clock source to each gate is exactly the same
- Layout is finished, but not simulated yet
- For a realistic simulation a line model will be used



# Future Plans

- Clock source shall be integrated on the chip:  
therefore a VCO (+PLL) is needed to generate a stable clock signal @25-30GHz
- Using another technology to run the chip at higher frequencies
  - Currently: 0.25 $\mu$ m SiGe:C BiCMOS technology with npn-HBTs up to  $f_T/f_{max} = 180/220GHz$
  - Planned: 0.13 $\mu$ m technology with npn-HBTs up to  $f_T/f_{max} = 250/300GHz$

# Acknowledgement



**Prof. Dr.-Ing. Viktor Krozer**  
**Institute of Physics, Goethe University Frankfurt am Main**



**IHP GmbH**  
**Innovations for High Performance Microelectronics**

Thank you for your attention!