

***Analysis Methods of Nonlinear Circuits  
and  
Stability under Large-Signal Conditions***

**G.Leuzzi**

***Dept. Electrical and Information Engineering - Univ. L'Aquila - Italy***




## Motivation:

### ***Stabilisation of nonlinear circuits under large-signal conditions***

- \* ***Nonlinear circuits under large-signal drive are subject to unwanted signals at spurious frequencies***
- \* ***These spurious signals are not detected by standard linear techniques***
- \* ***A stabilisation approach is highly desirable***









## Example:

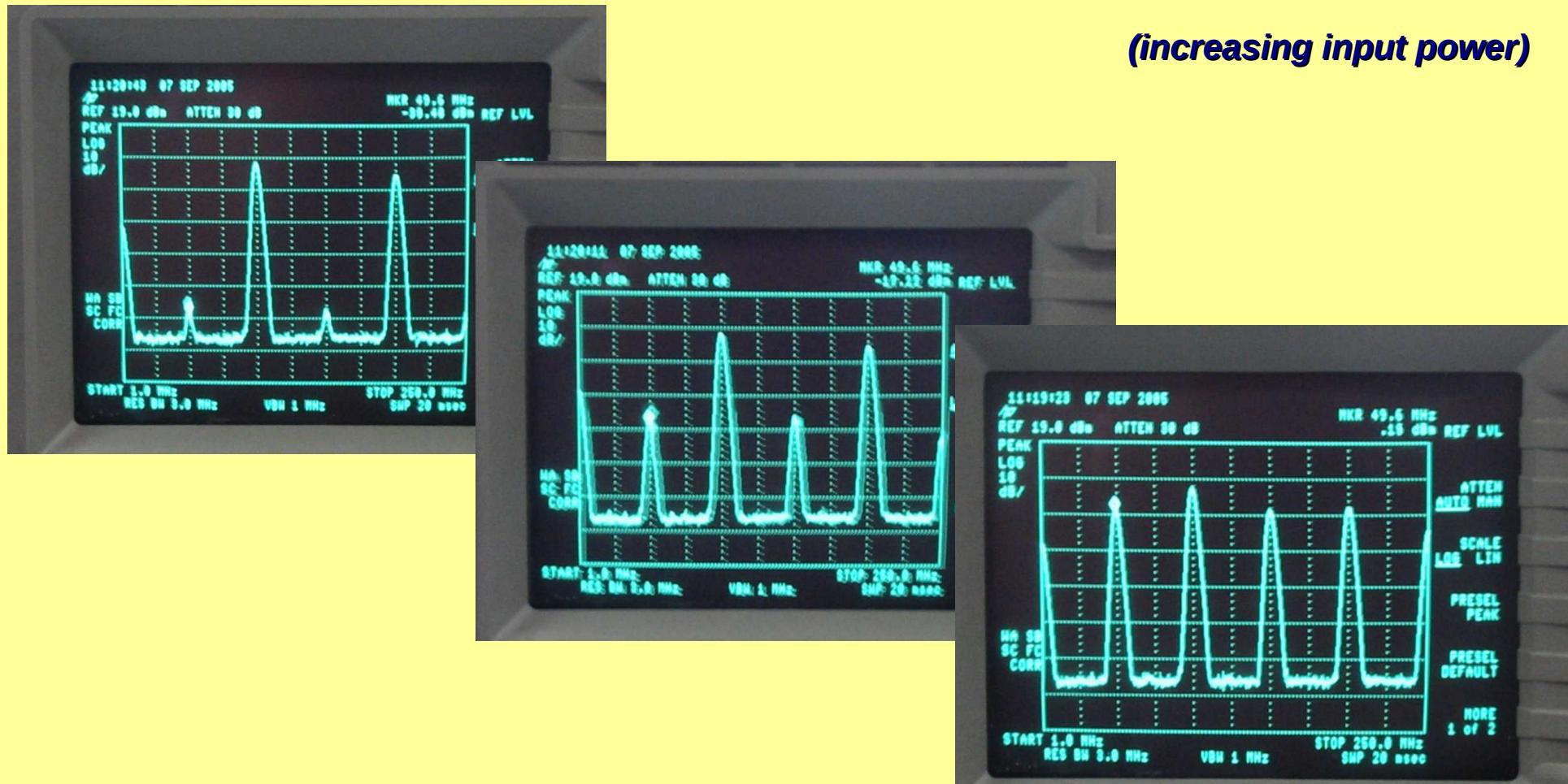



*Increasing input power*

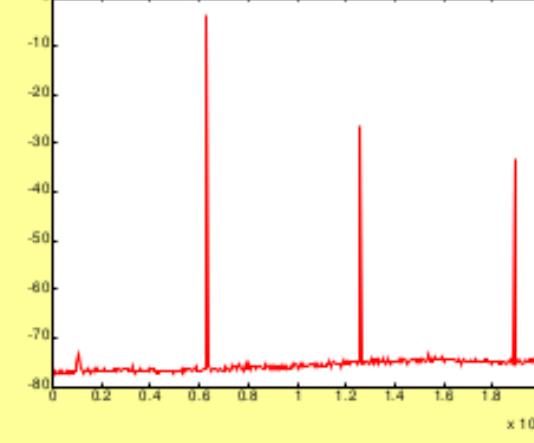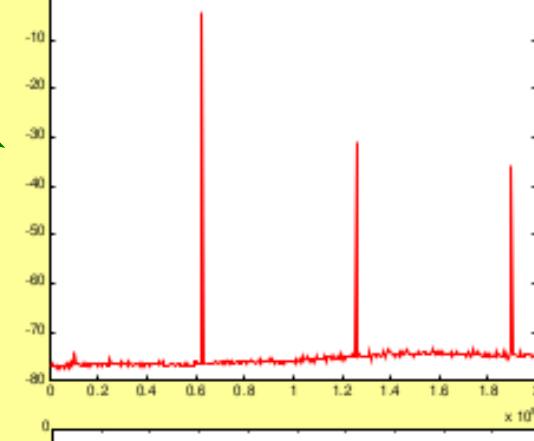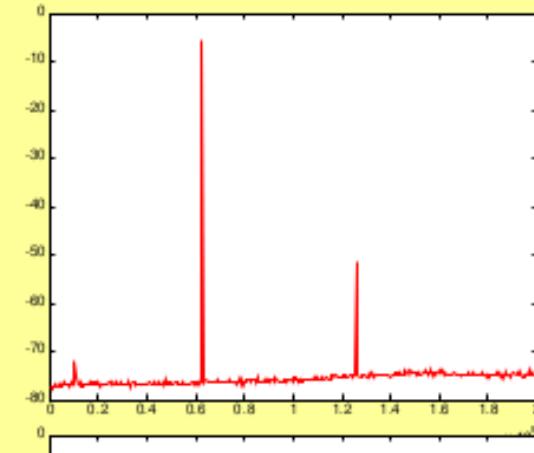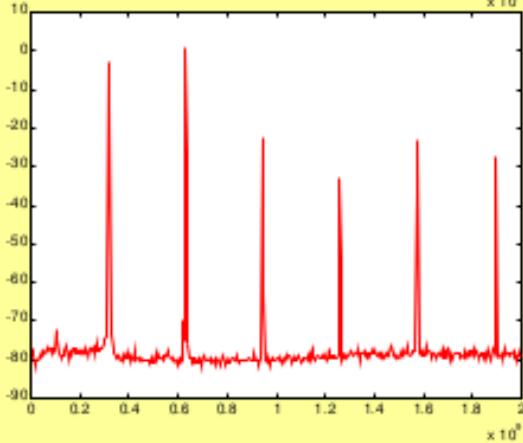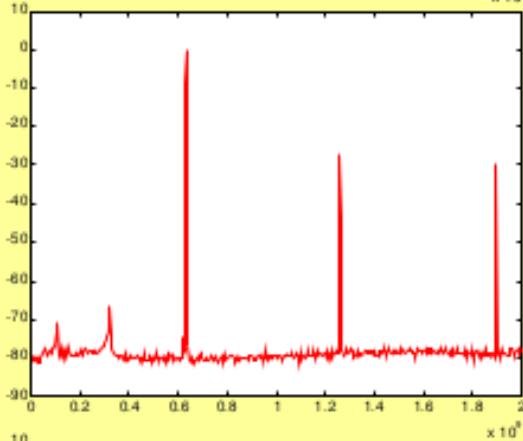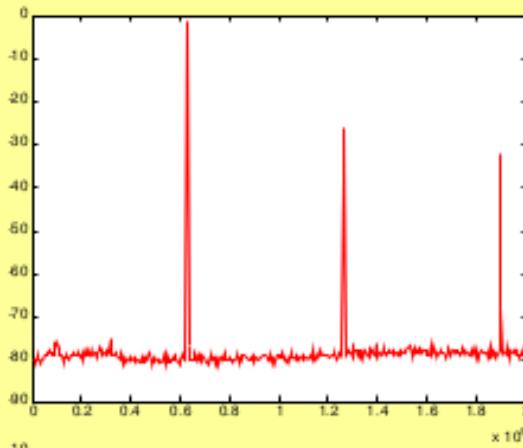


**stable**

**unstable**



## Example: power amplifier

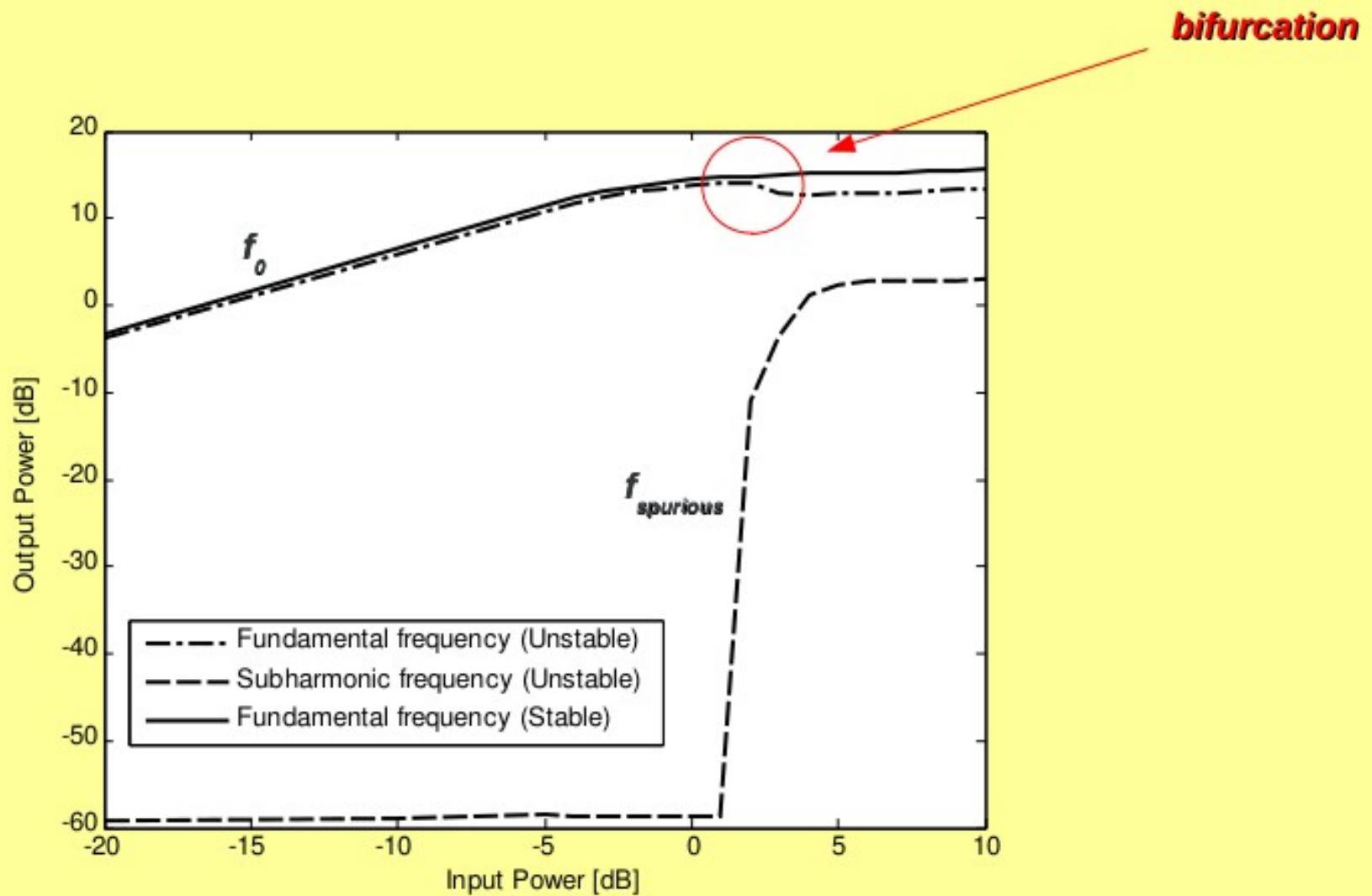




## Outline:


- \* ***Introduction***
- \* ***Detection of instabilities via nonlinear CAD simulation***
- \* ***The conversion matrix: toward a design approach***
- \* ***Applications: frequency divider, medium-power amplifier***
- \* ***Conclusions***


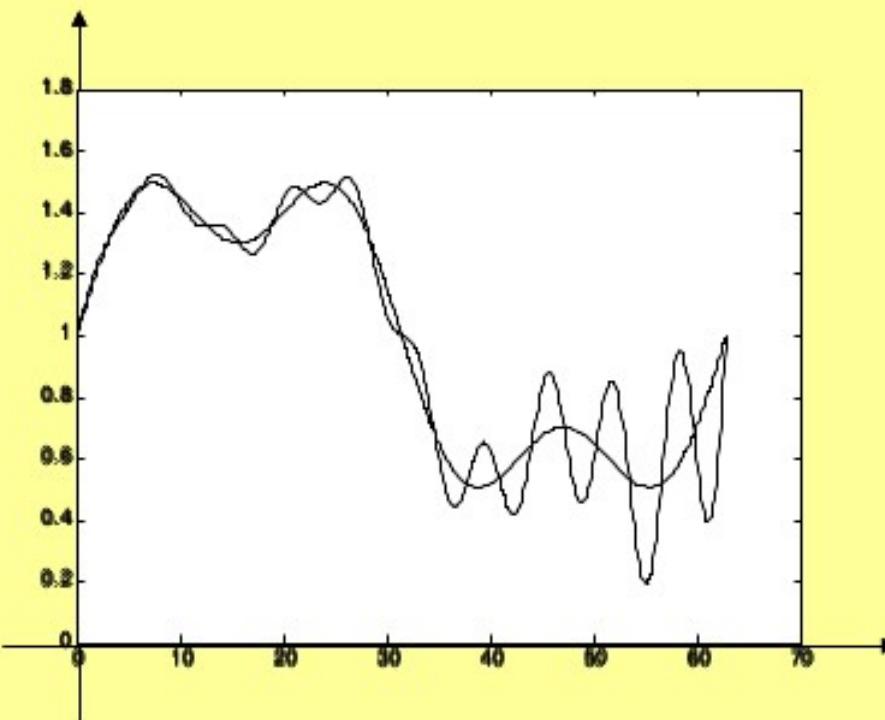
## Stability in small-signal / large-signal conditions:




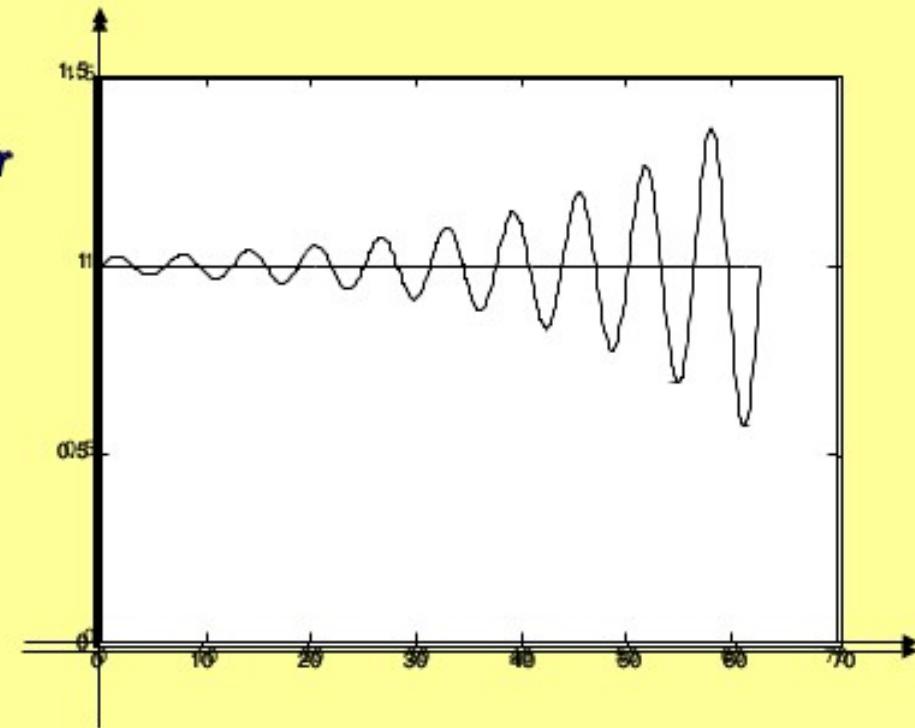
**Small-signal amplifier**  
**(Oscillator)**



**Mixer / Power amplifier**      **(Frequency divider)**




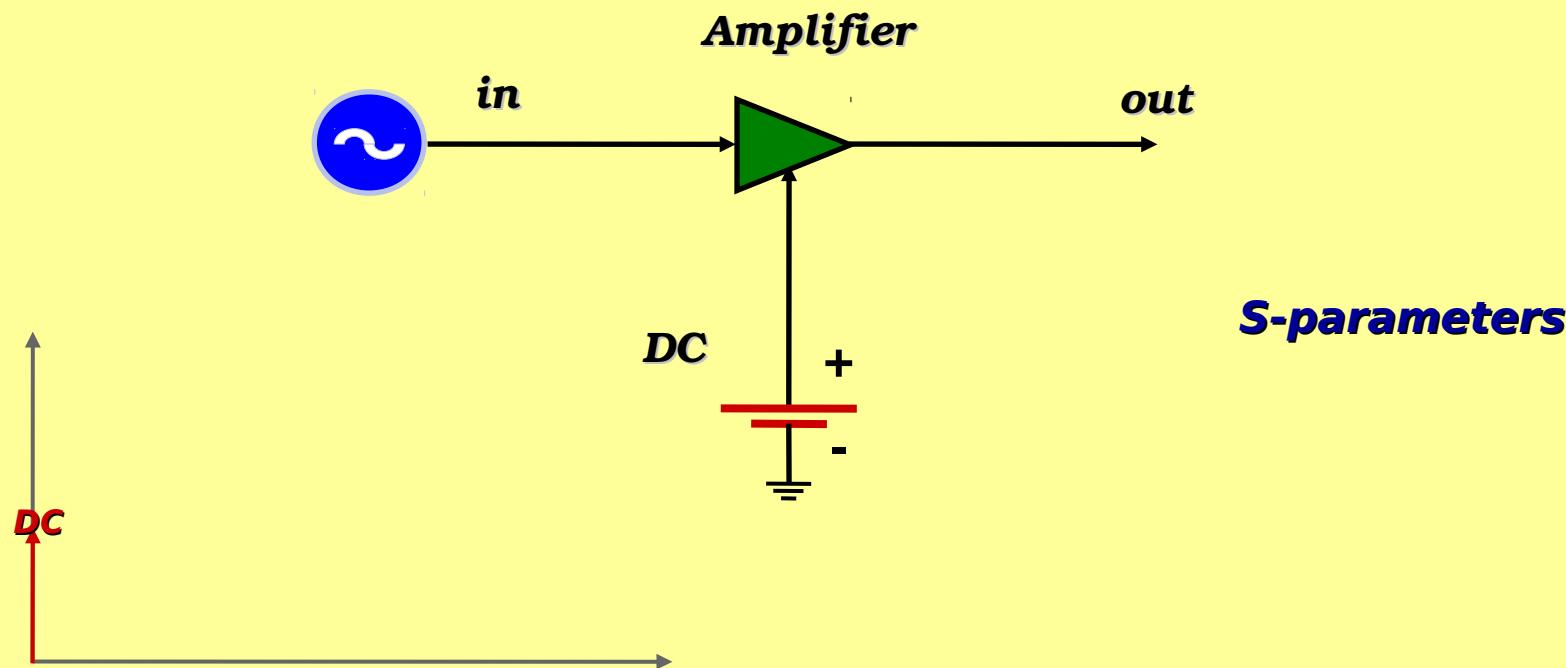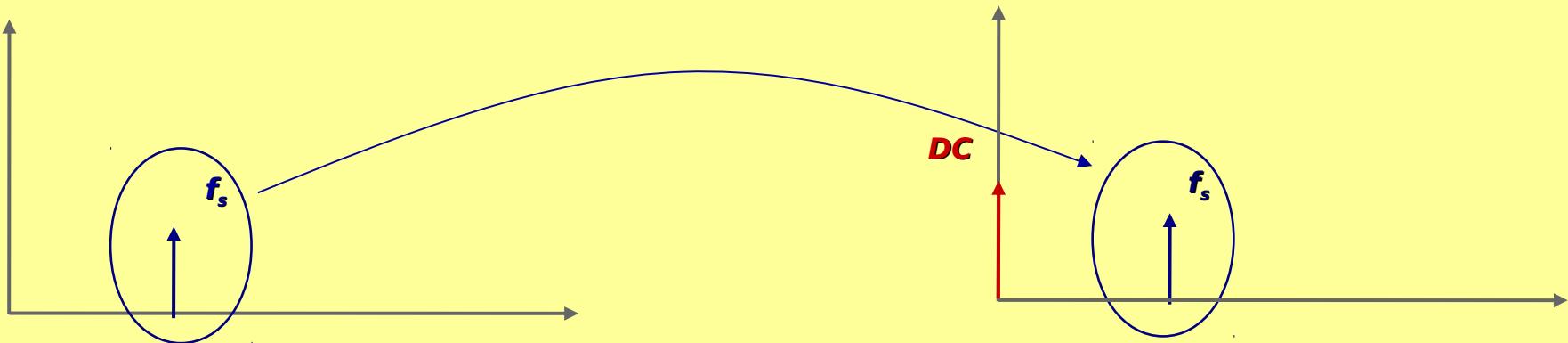**A large signal (DC) and a small signal in a linear amplifier:**





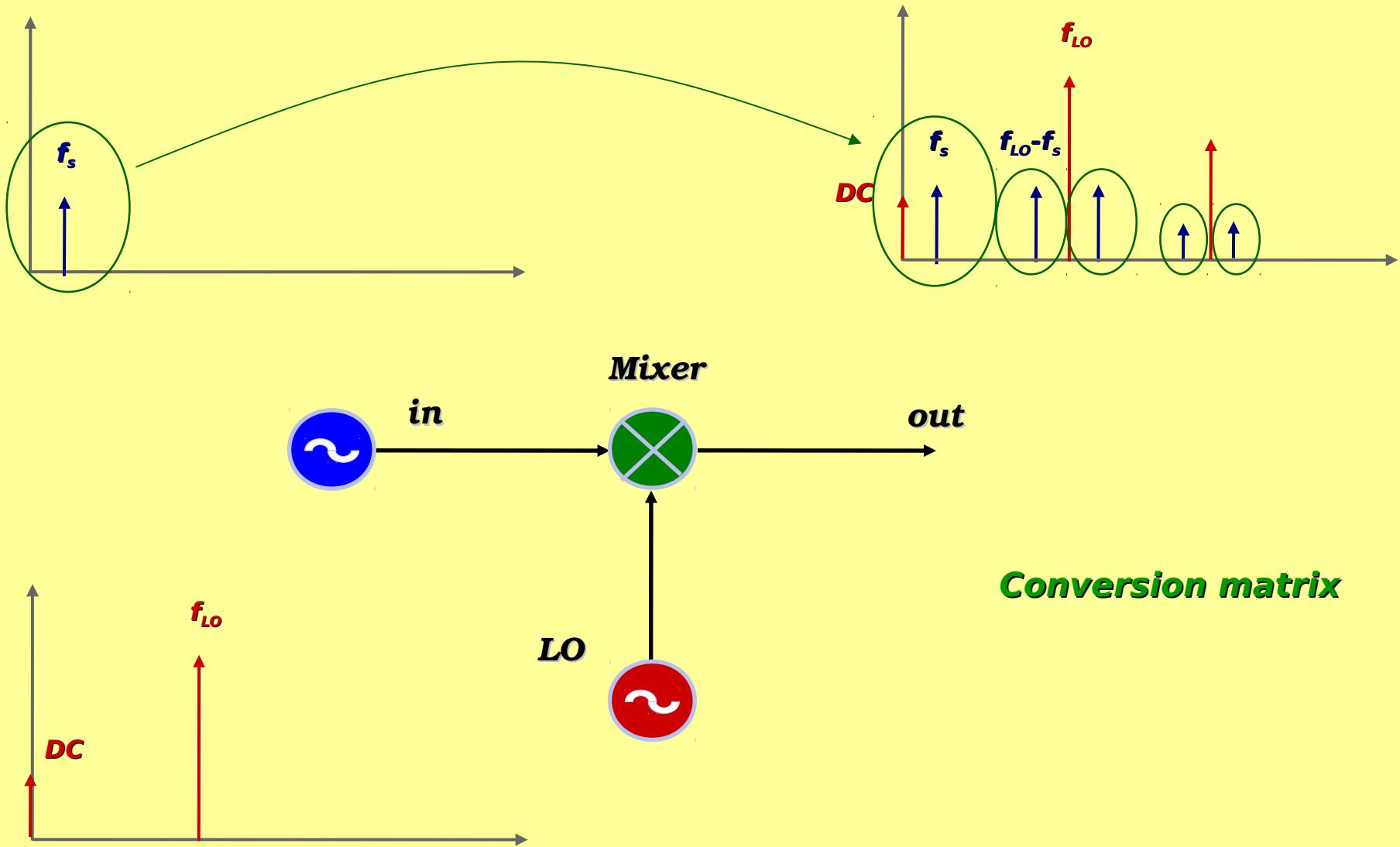
### A large signal (RF LO) and a small signal in a mixer:




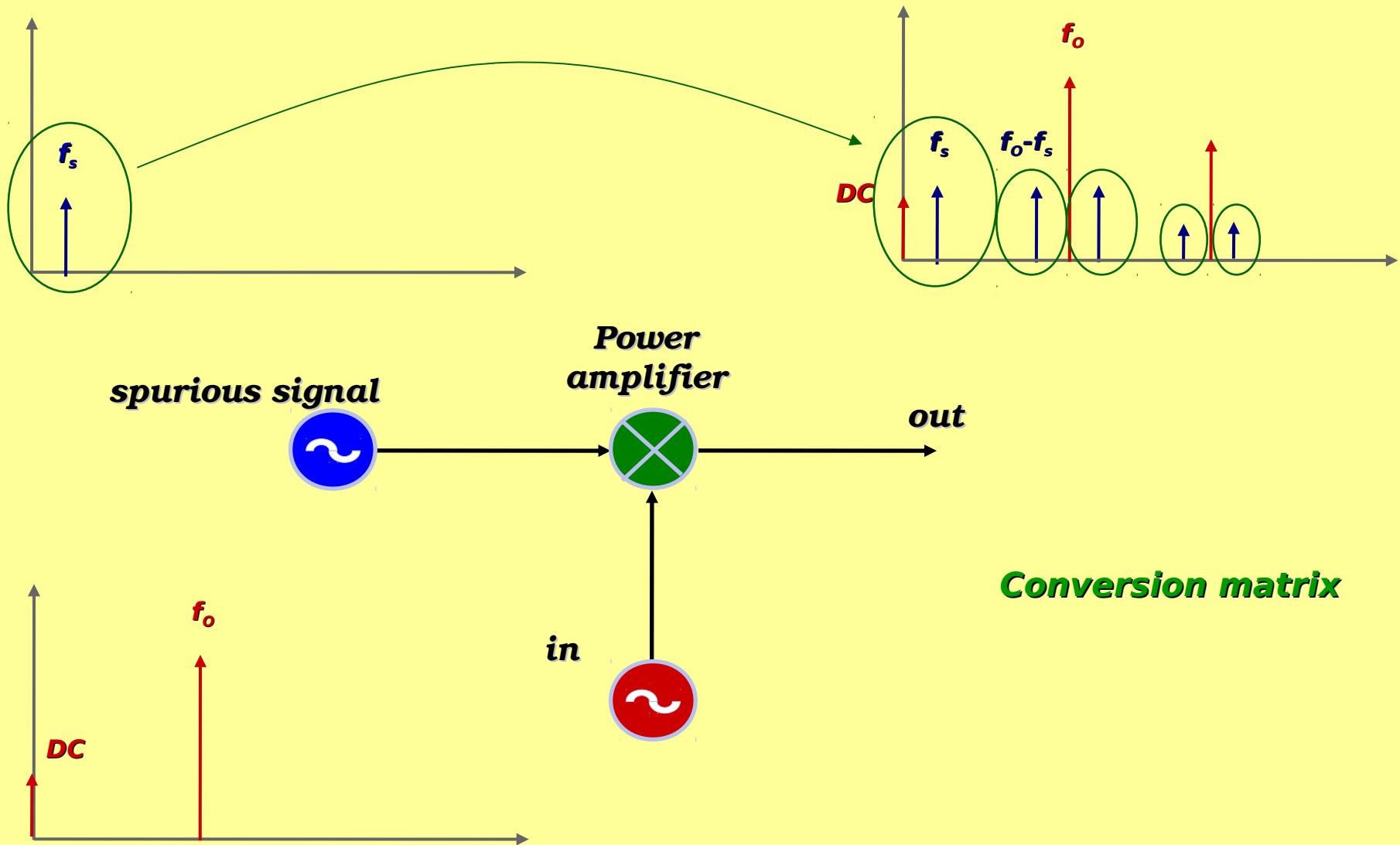
### A large signal (RF IN) and a small spurious signal in a power amplifier:





## Nonlinear computer-aided analysis methods:

***Direct time-domain integration:***

***SPICE***

***Shooting methods***

***Convolution approach***

***Series expansion:***

***Fourier series (Harmonic balance)***


***Volterra series***

***Mixed time-domain / Fourier series:***

***Transient envelope***



### Direct time-domain integration:

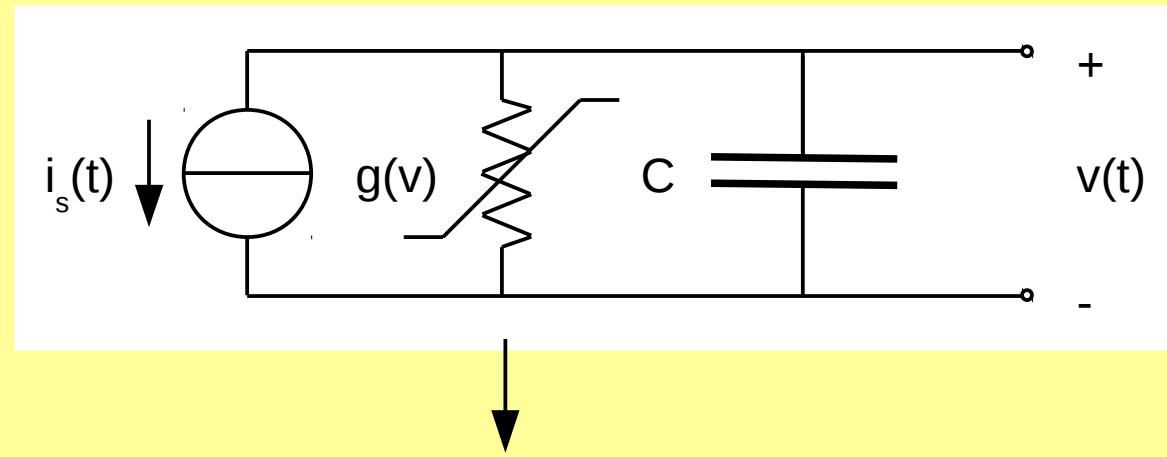


**KCL:**

$$i_s(t) + i_{max} \cdot \tanh\left(\frac{g \cdot v(t)}{i_{max}}\right) + C \cdot \left(\frac{dv(t)}{dt}\right) = 0$$


$$i_g = i_{max} \cdot \tanh\left(\frac{g \cdot v}{i_{max}}\right)$$

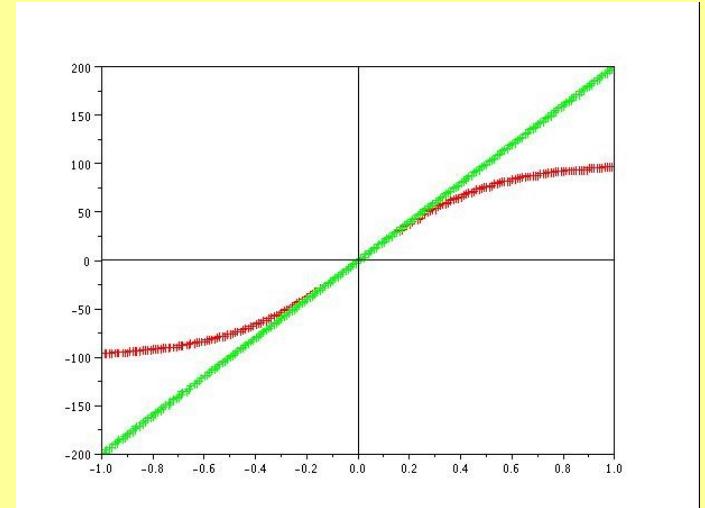**No analytical solution for the unknown function  $v(t)$**





### Direct time-domain integration:

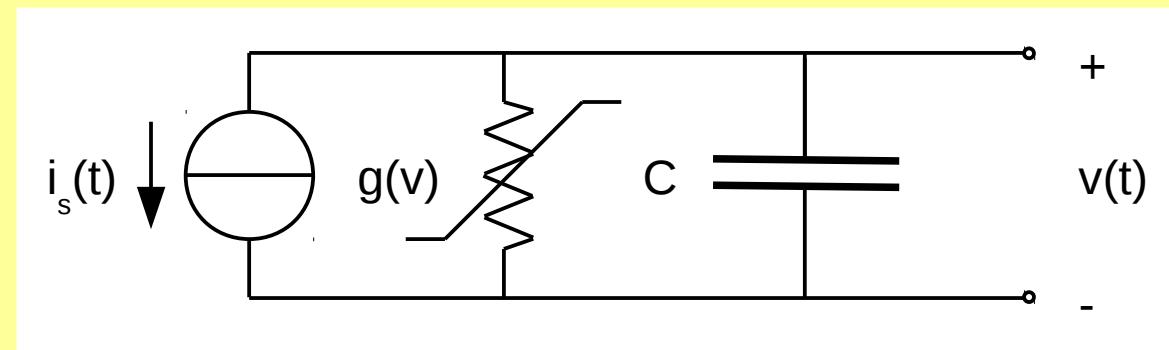

$$i_s(t) + i_{max} \cdot \tanh\left(\frac{g \cdot v(t)}{i_{max}}\right) + C \cdot \left(\frac{dv(t)}{dt}\right) = 0$$

$$t \Rightarrow t_k$$

$$i_{s,k}(t) + i_{max} \cdot \tanh\left(\frac{g \cdot v_k}{i_{max}}\right) + C \cdot \left(\frac{v_k - v_{k-1}}{t_k - t_{k-1}}\right) = 0$$

$$v(t) \Rightarrow v_k$$

$$k = 0, 1, 2, \dots$$



$$v(t_0) \Rightarrow v_0$$

Instead of an unknown function  $v(t)$  we look for discrete values  $v_k$


Numerical solution of the nonlinear equation in  $v_k$  at each time step  $t_k$  starting from  $v_0 = v(t_0)$



### Direct time-domain integration:

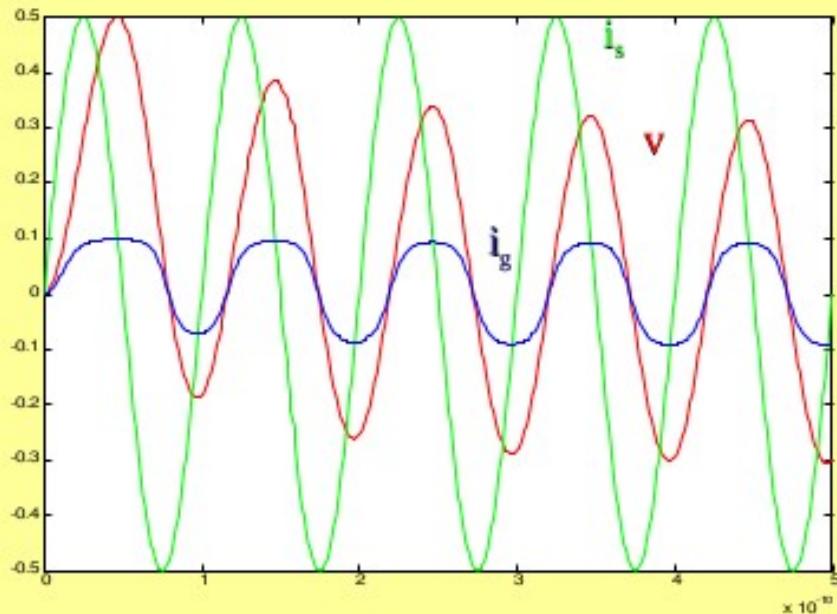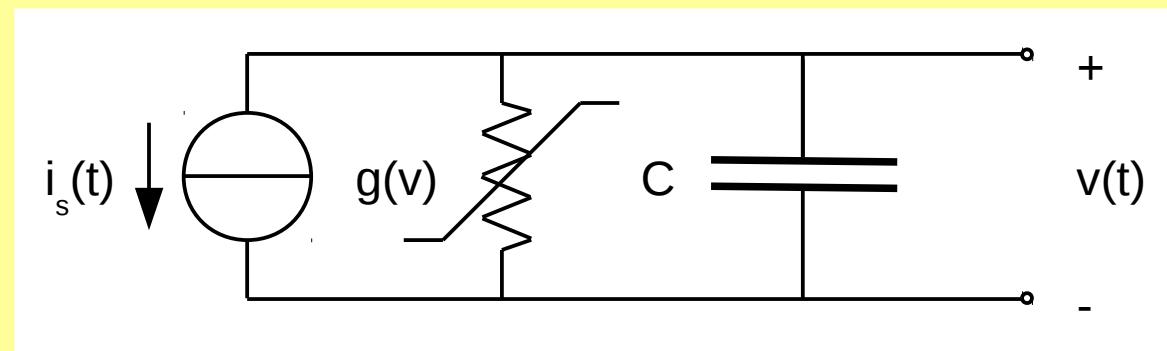


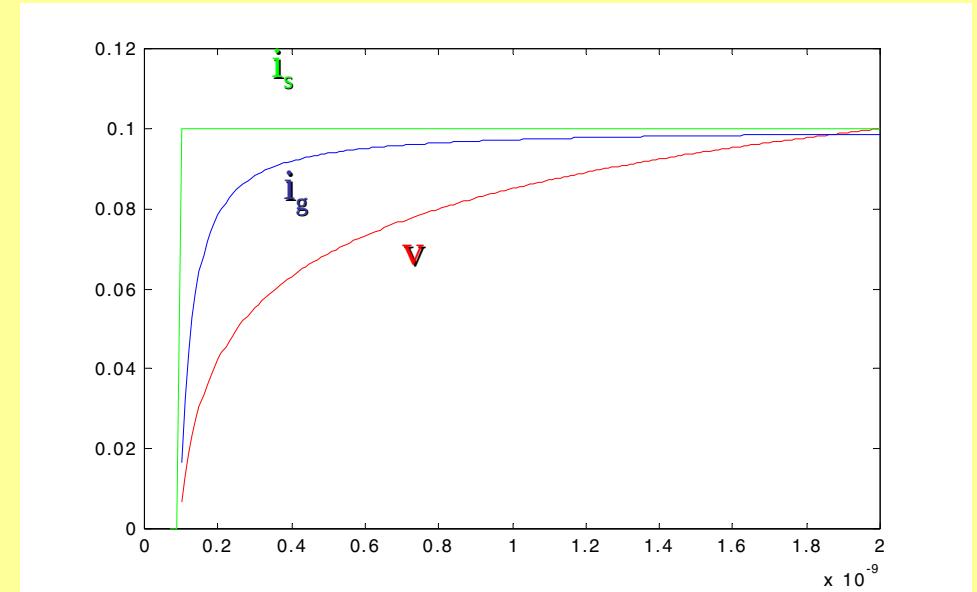
**Response to a sine wave (with transient)**



**Response to a step**



### Direct time-domain integration:

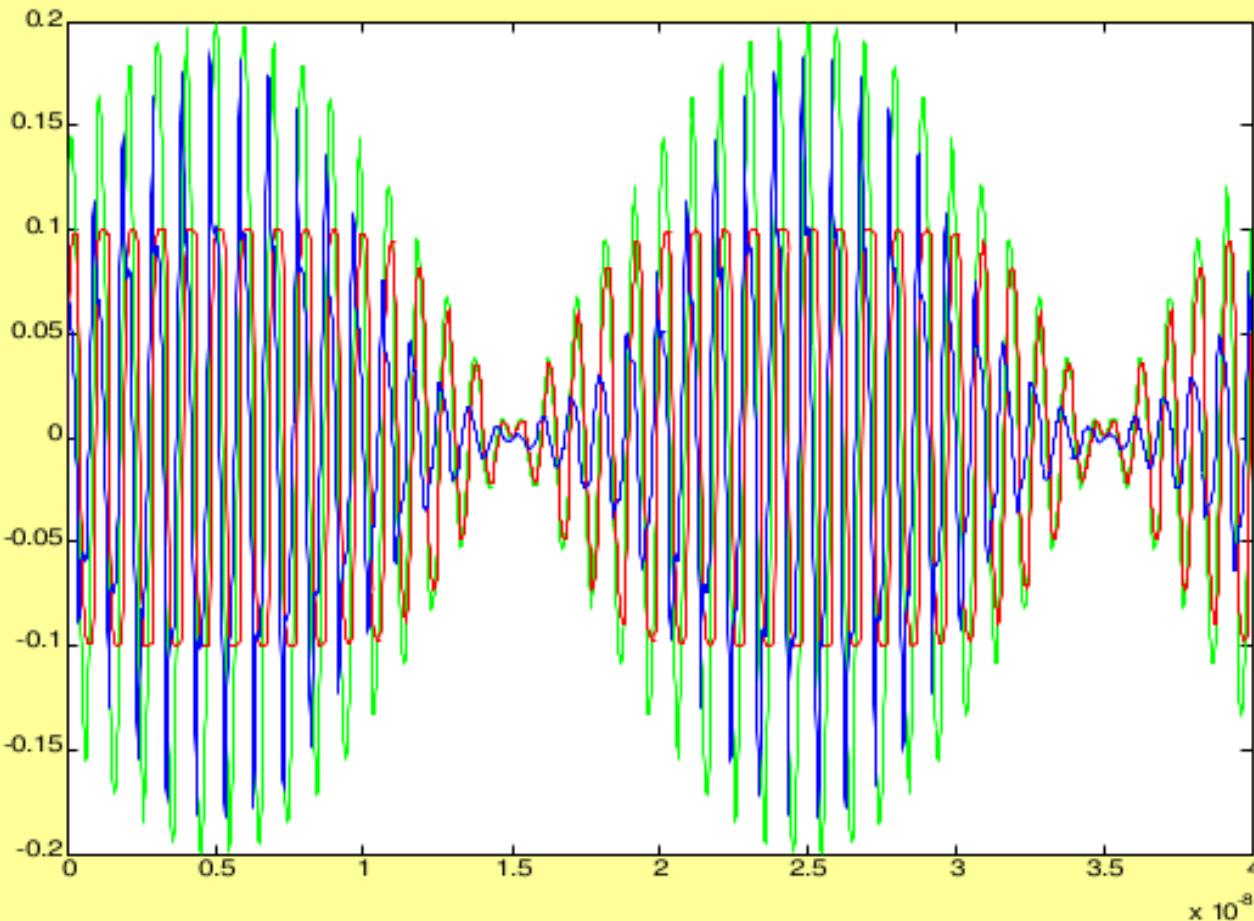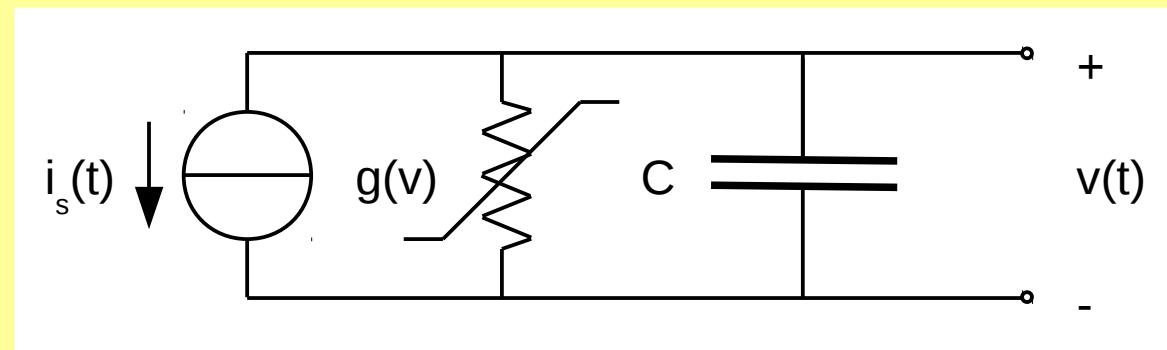

**Response to a two-tone  
quasi-sinusoidal signal**



**Time-domain solution:**

**General nonlinearities, even very strong**

**General solution**

**Shooting methods**


**Non efficient for steady state**

**Lumped elements only**

**Convolution method**



### Time-domain solution:

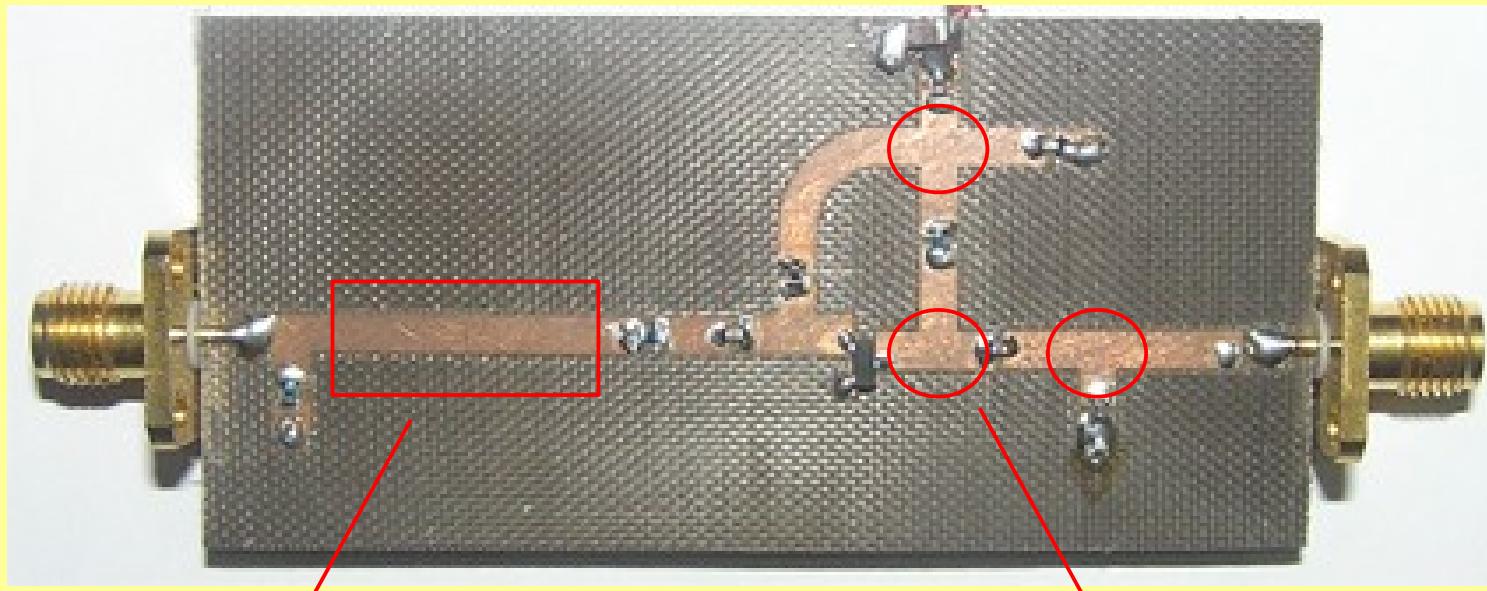


*Transmission lines*

*Discontinuities*

$$i(t) = f ?[v(t)]$$



## Convolution method:

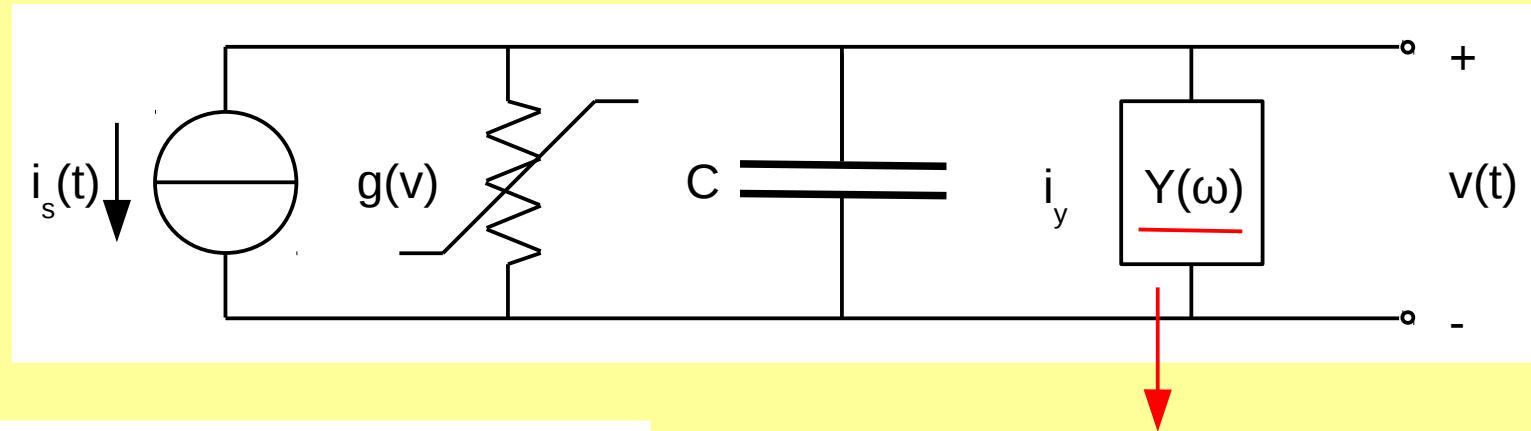

$$i_s(t) + i_{max} \cdot \tanh\left(\frac{g \cdot v(t)}{i_{max}}\right) + C \cdot \left(\frac{dv(t)}{dt}\right) + i_y(t) = 0$$

$$I_y(\omega) = Y(\omega) \cdot V(\omega)$$

$$y(t) = \frac{1}{\sqrt{2\pi}} \cdot \int Y(\omega) \cdot e^{j\omega t} \cdot d\omega$$

$$i_y(t) = i_y(t_0) + \int y(t-\tau) \cdot v(\tau) \cdot d\tau$$

$$i_{s,k}(t) + i_{max} \cdot \tanh\left(\frac{g \cdot v_k}{i_{max}}\right) + C \cdot \left(\frac{v_k - v_{k-1}}{t_k - t_{k-1}}\right) + \sum_{m=0}^M y_m \cdot v_{k-m} = 0$$



$$i_y(t_k) = \sum_{m=0}^M y_m \cdot v_{k-m}$$

Unfortunately does not work very well in practice!



## Solution by series expansion:


The unknown function is expanded in a suitable series of orthogonal functions  $v_n(t)$ :

$$v(t) = \sum_{n=-\infty}^{\infty} k_n \cdot v_n(t)$$

- The series is replaced into the 'difficult' equation
- The 'difficult' equation is splitted into infinite 'simpler' equations (using orthogonality)
- Only the first terms of the series (and thence the first equations) are retained
- The unknowns are the coefficients  $k_n$  of the series expansion


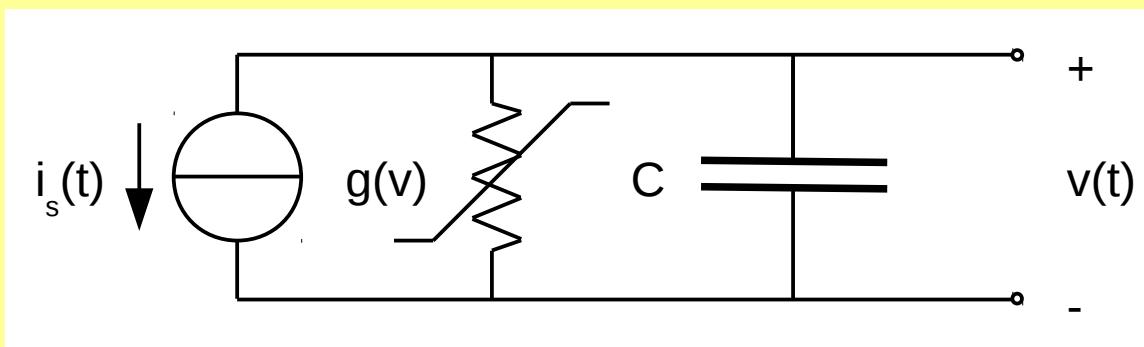
## Fourier series expansion (Harmonic balance):



$$i_s(t) + i_{max} \cdot \tanh\left(\frac{g \cdot v(t)}{i_{max}}\right) + C \cdot \left(\frac{dv(t)}{dt}\right) = 0$$

$$v(t) = \sum_{n=-\infty}^{\infty} V_n \cdot e^{jn\omega \cdot t}$$

$$\frac{dv(t)}{dt} = \sum_{n=-\infty}^{\infty} jn\omega C \cdot V_n \cdot e^{jn\omega \cdot t}$$


$$i_s(t) = \sum_{n=-\infty}^{\infty} I_{s,n} \cdot e^{jn\omega \cdot t}$$

$$\sum_{n=-\infty}^{\infty} I_{s,n} \cdot e^{jn\omega \cdot t} + i_{max} \cdot \tanh\left(\frac{g \cdot \sum_{n=-\infty}^{\infty} V_n \cdot e^{jn\omega \cdot t}}{i_{max}}\right) + \sum_{n=-\infty}^{\infty} jn\omega C \cdot V_n \cdot e^{jn\omega \cdot t} = 0$$

**The explicit expression of the Fourier series of the nonlinear current is not available**


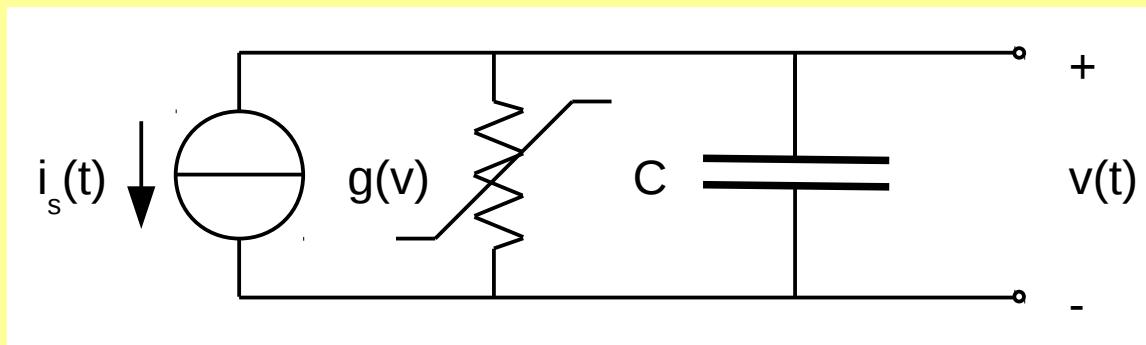
## Fourier series expansion (Harmonic balance):



$$i_{max} \cdot \tanh\left(\frac{g \cdot \sum_{n=-\infty}^{\infty} V_n \cdot e^{jn\omega \cdot t}}{i_{max}}\right)$$

↓  
Discrete Fourier Transform (DFT)

$$\sum_{n=-\infty}^{\infty} I_{g,n} \cdot e^{jn\omega \cdot t}$$

$$\sum_{n=-\infty}^{\infty} I_{s,n} \cdot e^{jn\omega \cdot t} + \boxed{g \cdot \sum_{n=-\infty}^{\infty} V_n \cdot e^{jn\omega \cdot t}} + \sum_{n=-\infty}^{\infty} jn\omega C \cdot V_n \cdot e^{jn\omega \cdot t} = 0$$

$$\sum_{n=-\infty}^{\infty} I_{s,n} \cdot e^{jn\omega \cdot t} + \boxed{\sum_{n=-\infty}^{\infty} I_{g,n} \cdot e^{jn\omega \cdot t}} + \sum_{n=-\infty}^{\infty} jn\omega C \cdot V_n \cdot e^{jn\omega \cdot t} = 0$$



**System of orthogonal nonlinear  
equations in the unknowns  $V_n$**

$$I_{s,n} + I_{g,n}(\vec{V}) + jn\omega C \cdot V_n = 0$$

$$n = -N \div N$$



## Harmonic balance:

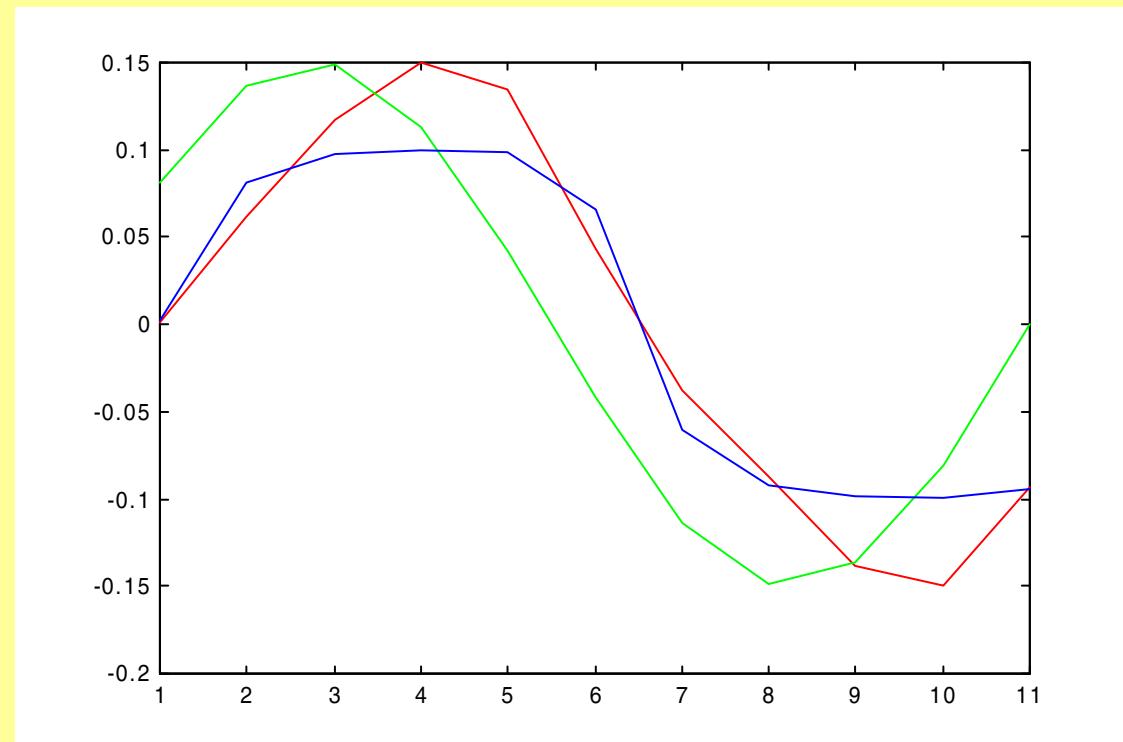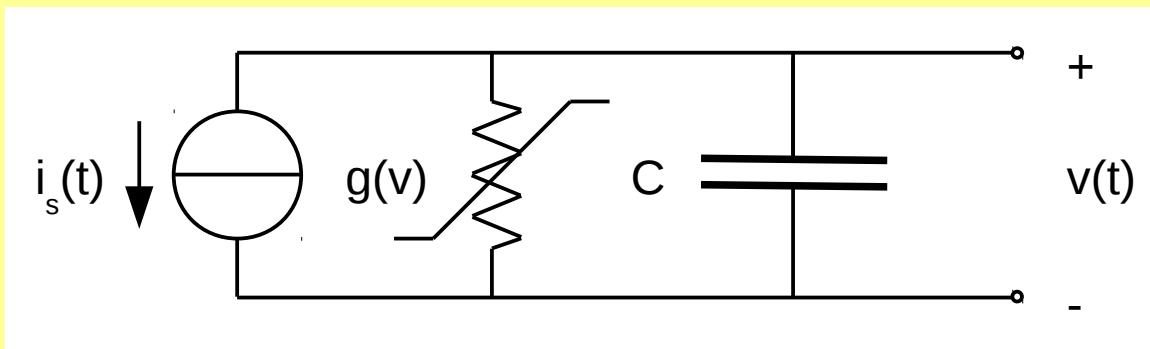



**Harmonic balance:**

**General nonlinearities, weak to moderately strong**

**Frequency domain linear subcircuits**

**Steady state only**

**Not efficient for multi-tone or complex modulation schemes**

**Envelope transient**


**Multi-dimensional Fourier transform**



## Transient envelope:

$$v(t) = \sum_{n=-\infty}^{\infty} V_n(t) \cdot e^{jn\omega \cdot t}$$

## **Slowly varying phasors**

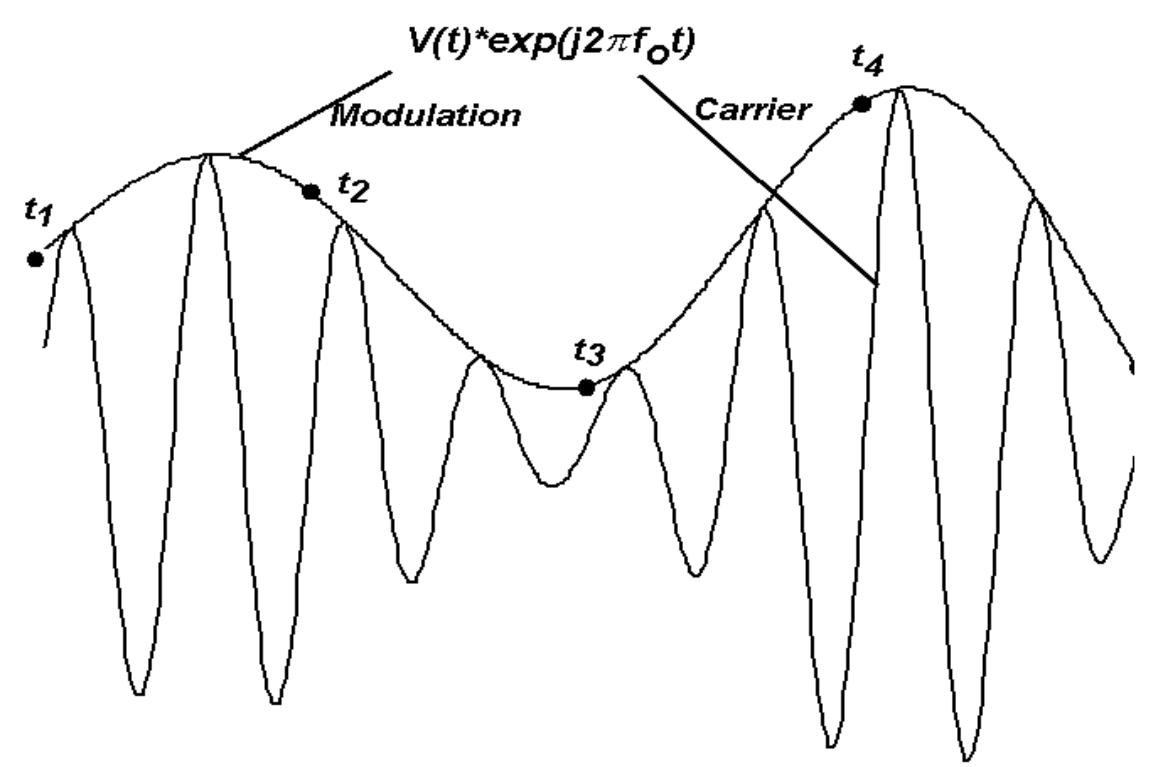

(narrowband modulation, start-up of oscillation, etc.)



$$\sum_{n=-\infty}^{\infty} I_{s,n}(t) \cdot e^{jn\omega \cdot t} + i_{max} \cdot \tanh\left(\frac{g \cdot \sum_{n=-\infty}^{\infty} V_n(t) \cdot e^{jn\omega \cdot t}}{i_{max}}\right) + C \frac{d\left(\sum_{n=-\infty}^{\infty} V_n(t) \cdot e^{jn\omega \cdot t}\right)}{dt} = 0$$

**Time-domain discretisation of the values of the slowly varying phasors**


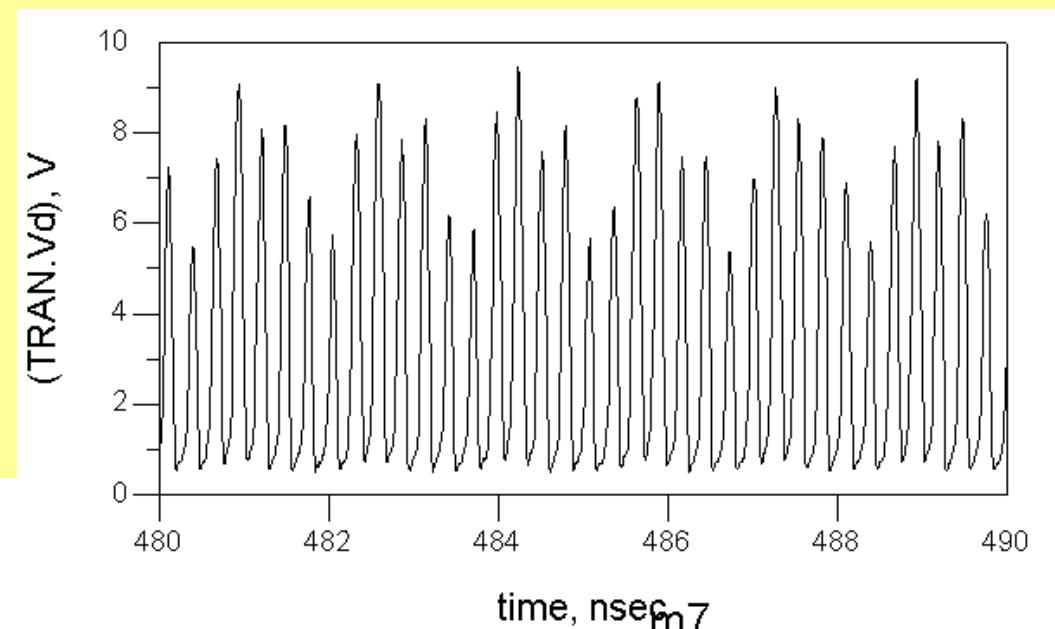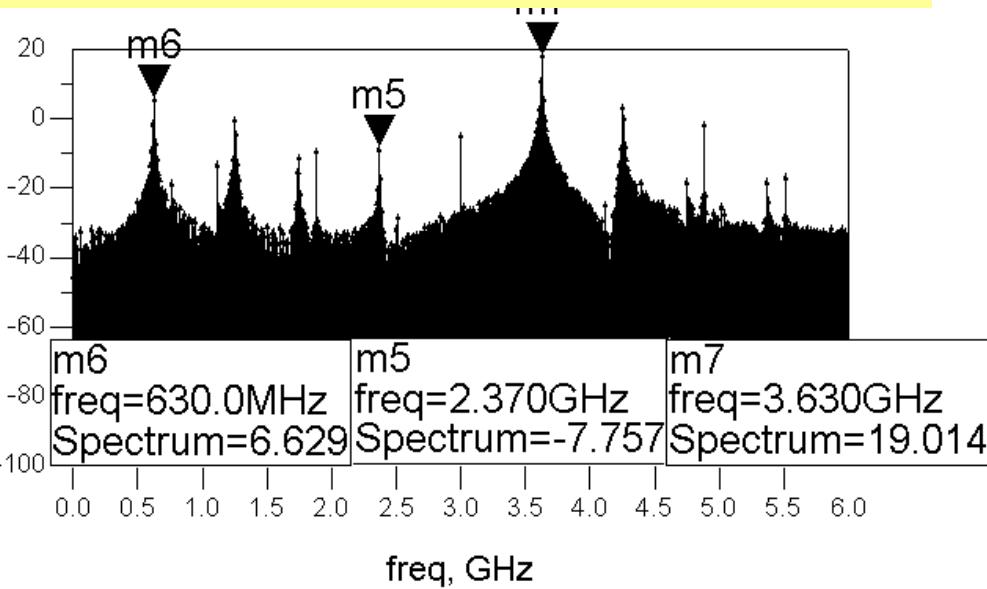
## CAD detection of instabilities:

Time-domain analysis detects spurious frequencies (instabilities)





### CAD detection of instabilities:

**Harmonic balance analysis does not detect spurious frequencies:**


$$v(t) = \sum_{n=-\infty}^{\infty} V_n \cdot e^{jn\omega \cdot t}$$

**unless included in the frequency list,**

**or detected by means of an auxiliary generator.**



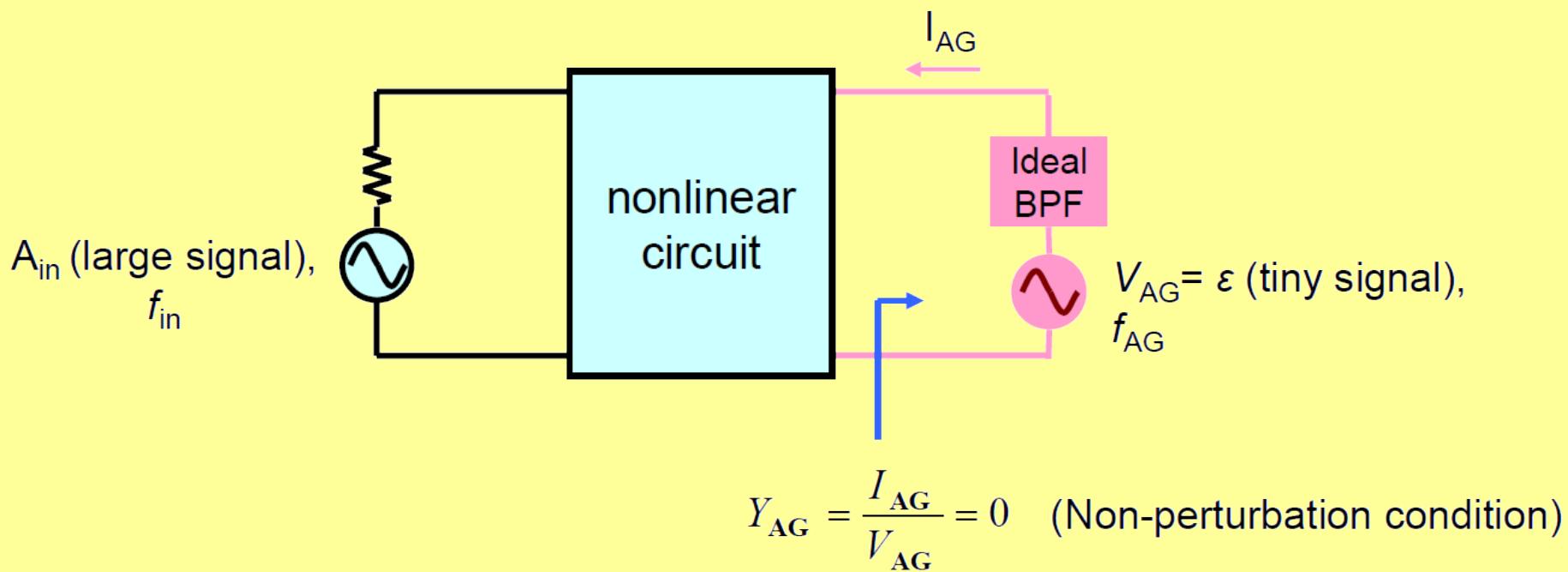
## Harmonic balance detection of instabilities: the auxiliary generator





**A probing voltage is applied at the spurious frequency, and an oscillation condition is looked for:**

**Frequency, phase and amplitude of the probing voltage  
are swept until the non-perturbation condition is found.**

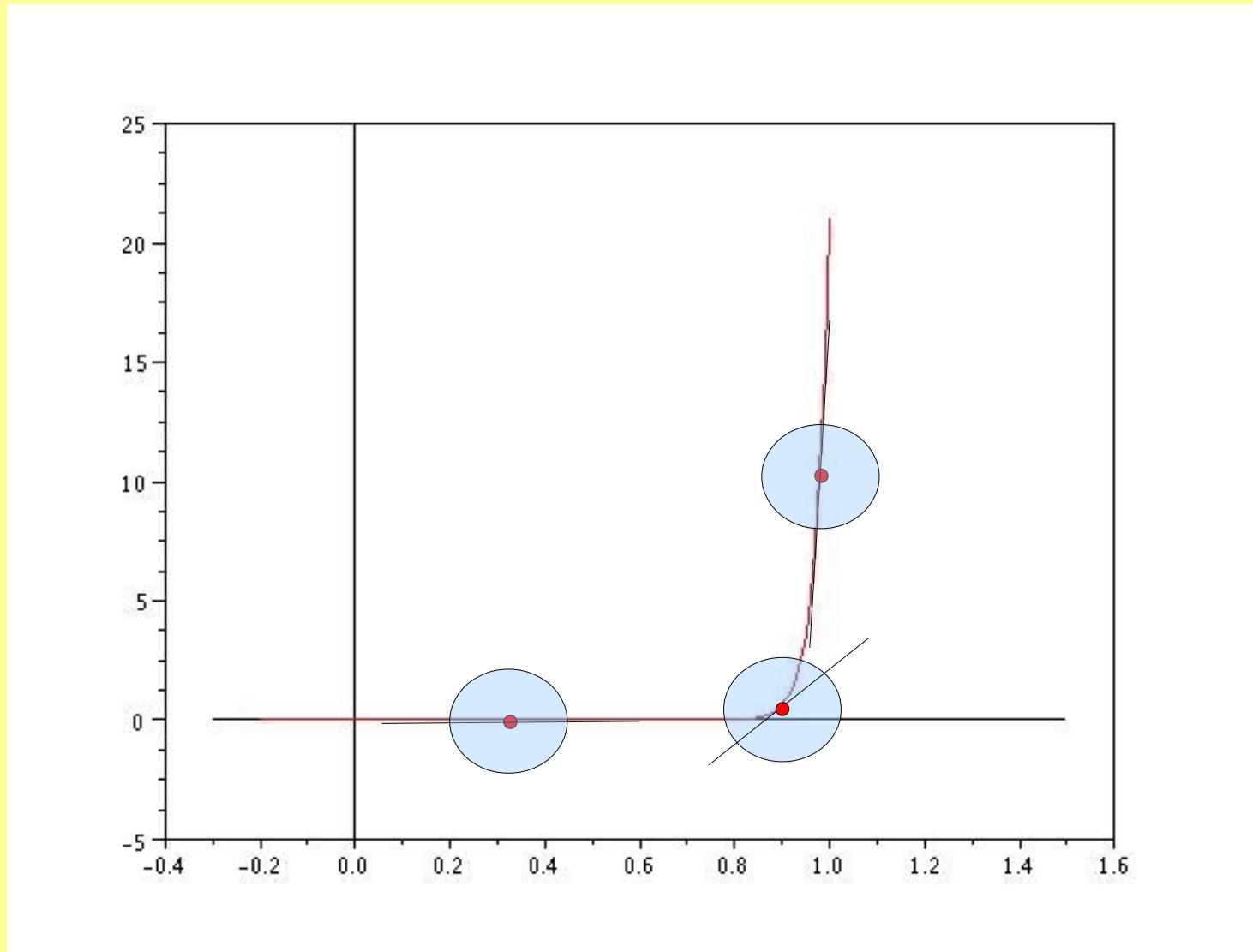The conversion matrix:**Linearisation around a static bias point****Linearisation around  
a dynamic bias point**

The conversion matrix:

Periodic switching: frequency conversion

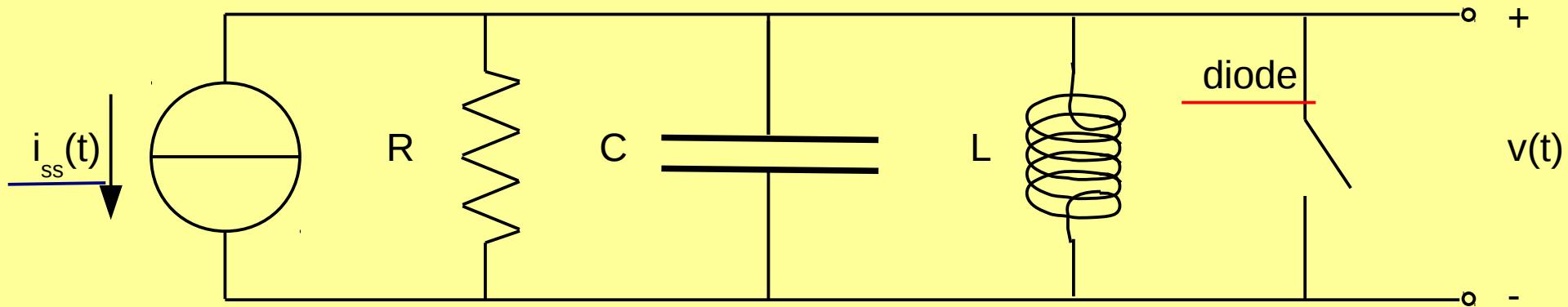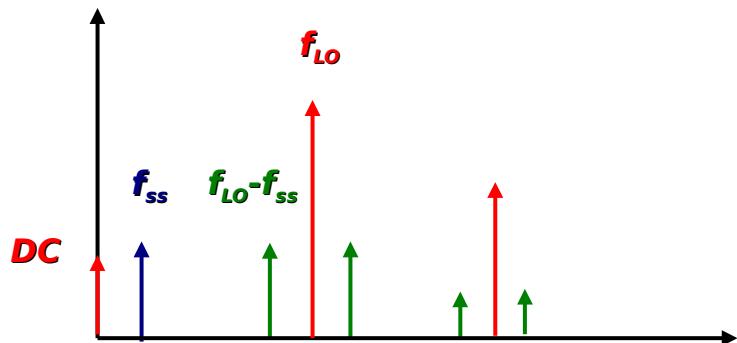

$$v(t) = I_{ss} \sin(\omega_{ss} t) \cdot \sum_{n=-\infty}^{\infty} G_n \cdot e^{-jn\omega_{LO} \cdot t} = \sum_{n=-\infty}^{\infty} [I_{ss} G_n \cdot e^{-jn(\omega_{LO} - \omega_{ss}) \cdot t} + I_{ss} G_n \cdot e^{-jn(\omega_{LO} + \omega_{ss}) \cdot t}]$$

---

*in*

---


*diode*

---



*LSB*

---

*USB*

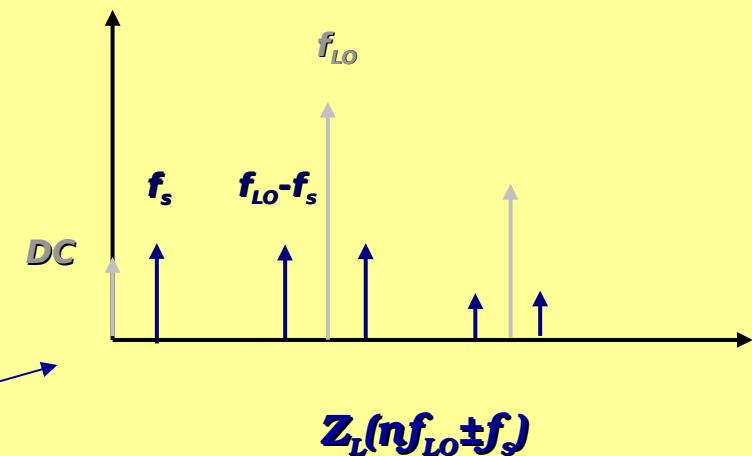The conversion matrix:

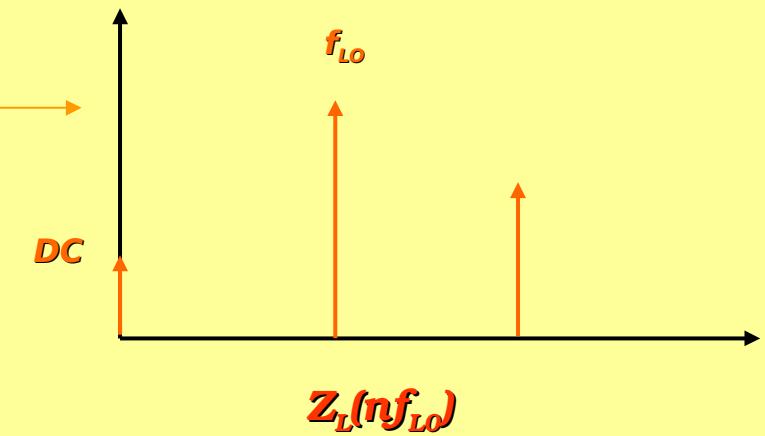
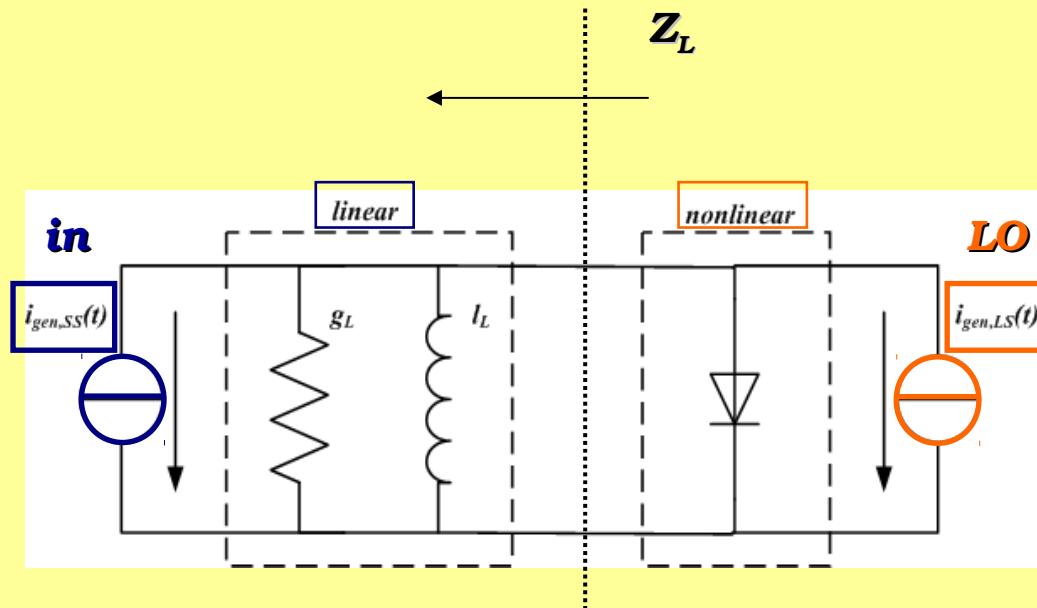
**Small-signal (in) behaviour: converted frequencies**



**Large-signal (LO) behaviour: fundamental frequency (and harmonics) loads**




### The conversion matrix:

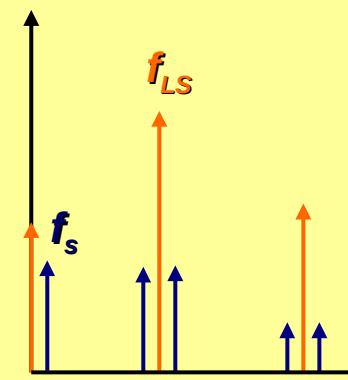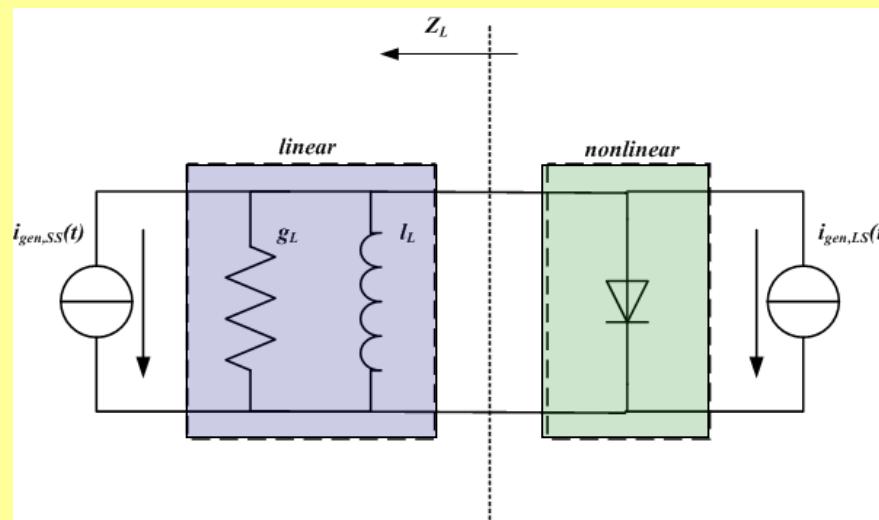

### **Small-signal operations:**


**frequency-converting linear network**

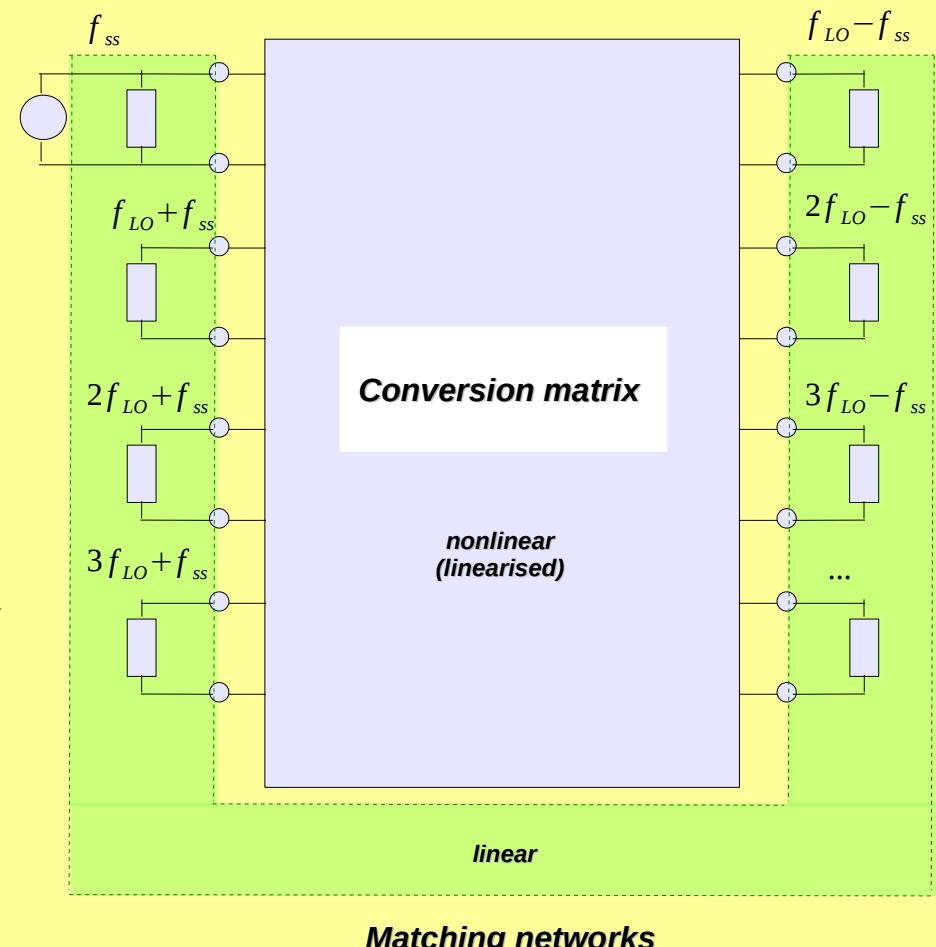




### The conversion matrix:

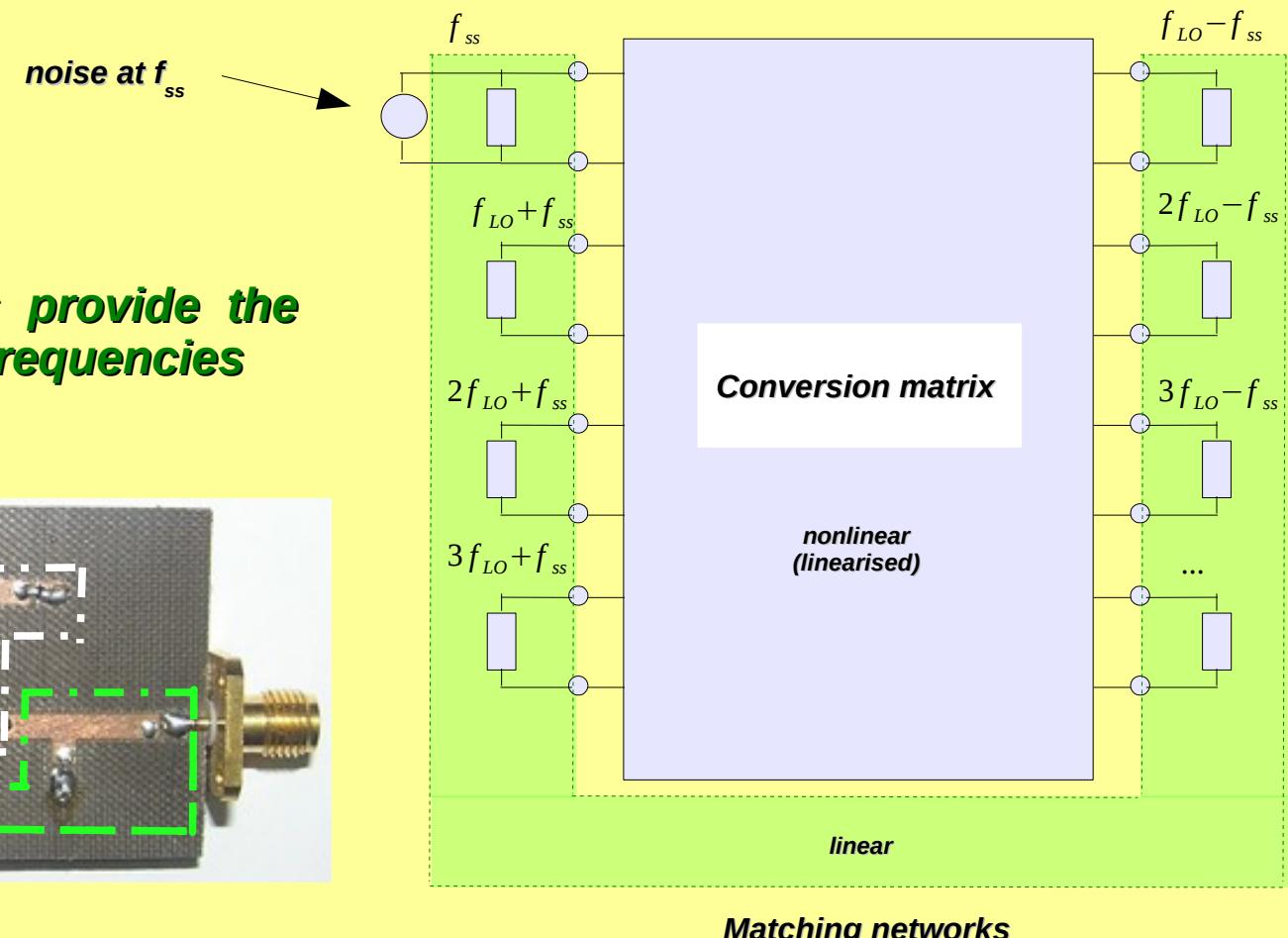**Active device (+ bias networks) linearised by means of the conversion matrix**



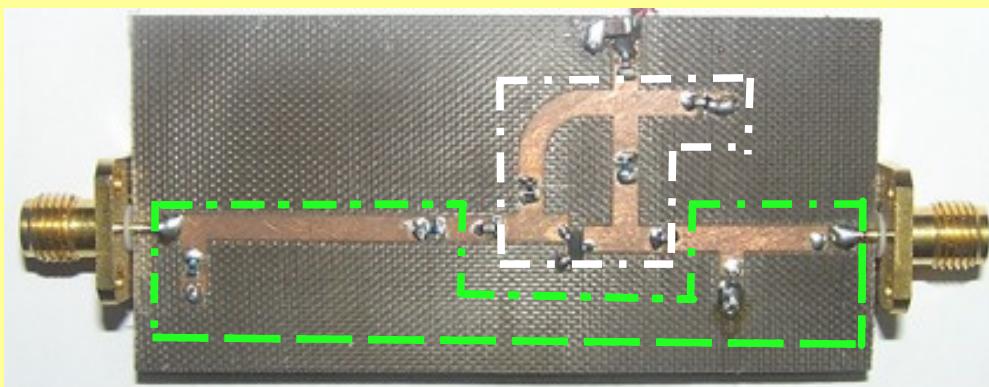
**Passive matching networks provide the external loads at converted frequencies**




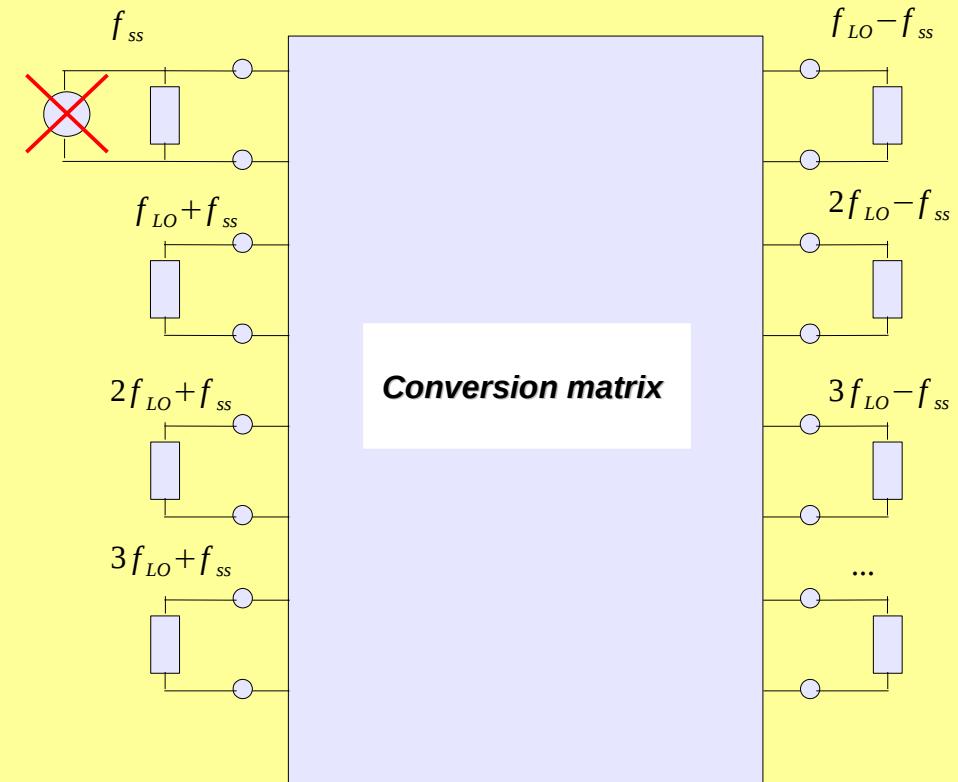
## Stability (Rizzoli, 1985):

- Removal of the small-signal excitation
- Linear, homogeneous equations system
- Determinant of the system = 0 ?



**Non-trivial solution at small-signal frequency: oscillation -> instability**

**(provided that the Rollett proviso is fulfilled)**




## Stability (Rizzoli, 1985):

**The determinant is a function of the small-signal frequency  $\omega_{ss}$**

**Onset of oscillation:**

**complex frequency**

$$\sigma = \alpha_{ss} + j \omega_{ss}$$

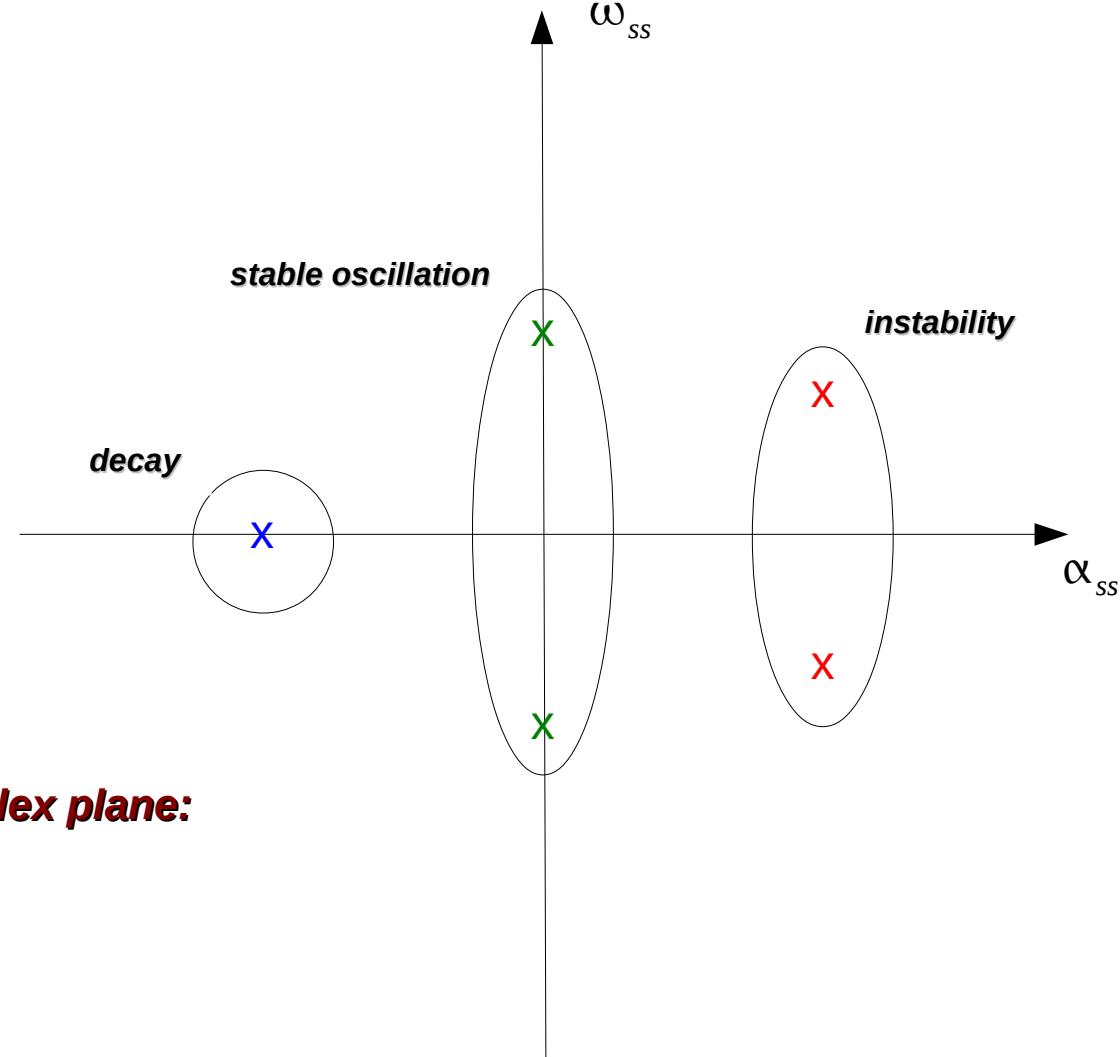

**The zeros of the determinant in the complex plane:**




## Stability (Rizzoli, 1985):

**Calculation of the determinant in the Laplace domain**

$$\sigma = \alpha_{ss} + j \omega_{ss}$$

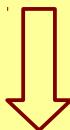**Not possible with currently available CAD programs!**




**Calculation along the imaginary axis**

$$\sigma = j \omega_{ss}$$



**Encirclements of the origin**  
=

**Zeros in the RHS half-plane**

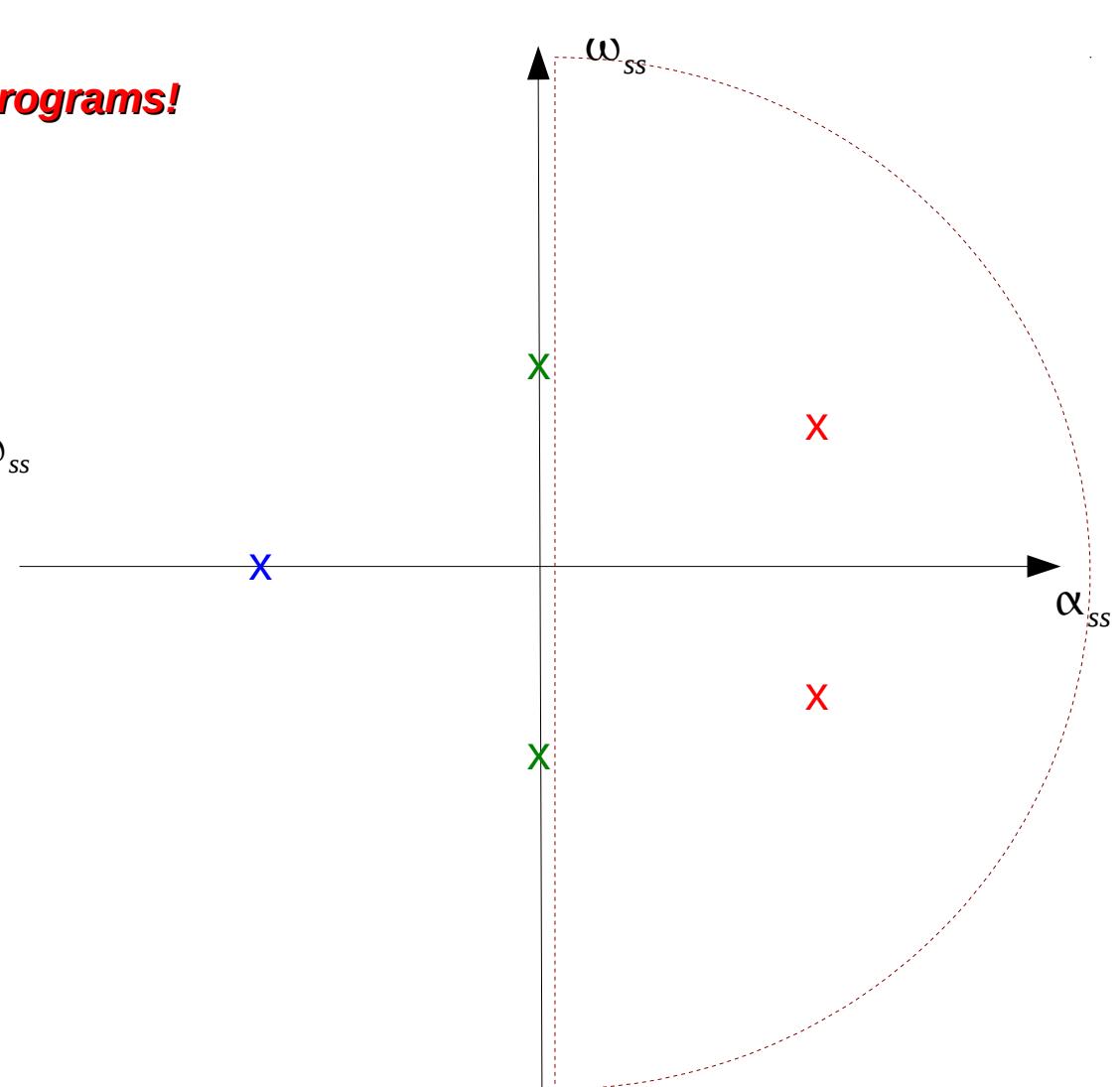

Stability (Rizzoli, 1985):

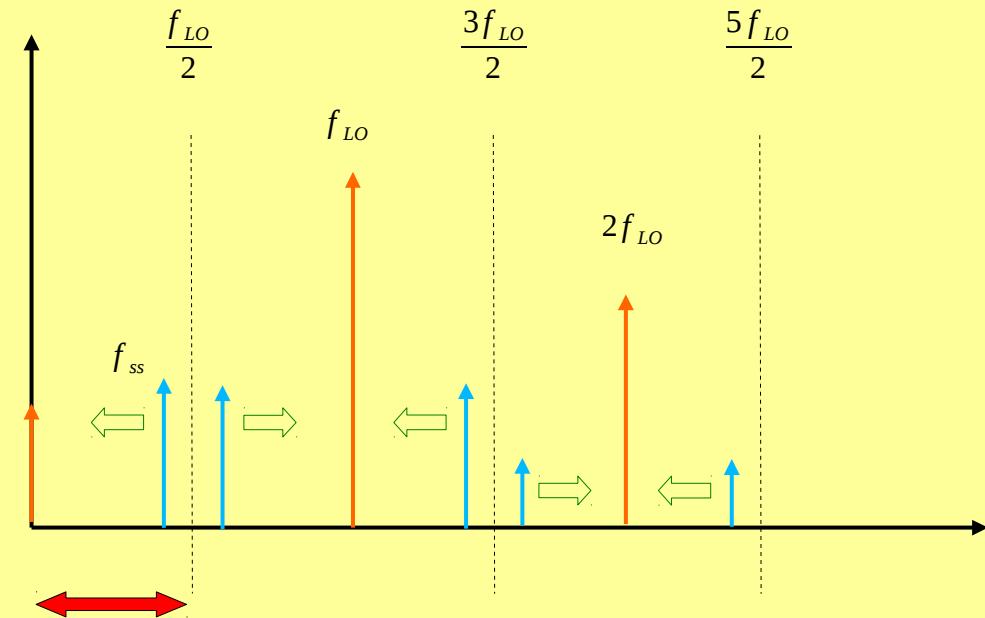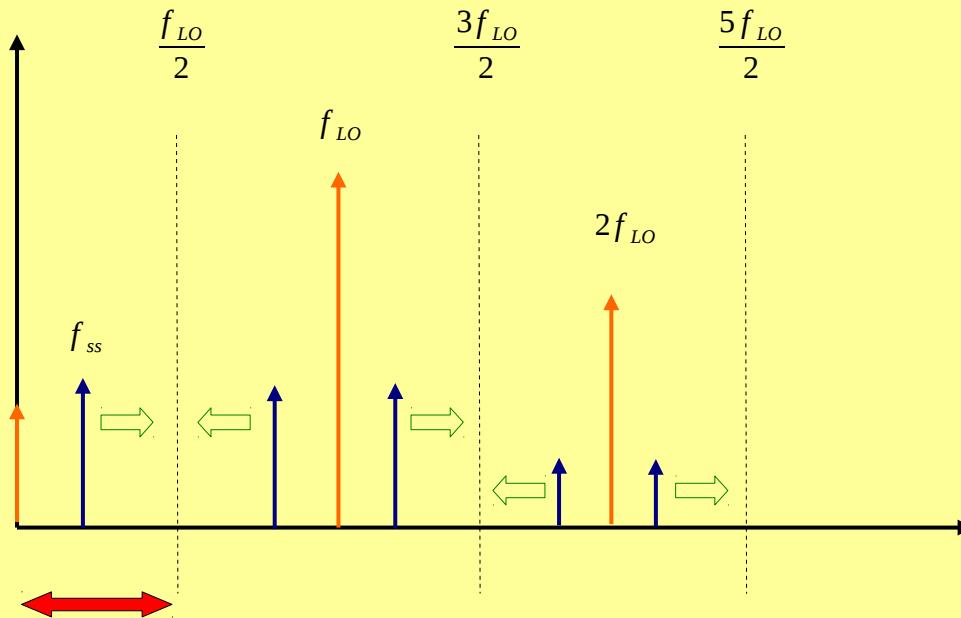**The conversion matrix is periodic as a function of frequency:**



and symmetric with respect to  $\frac{f_{LO}}{2}$



Calculation in the range:

$$0 \div \left(\frac{f_{LO}}{2}\right)$$

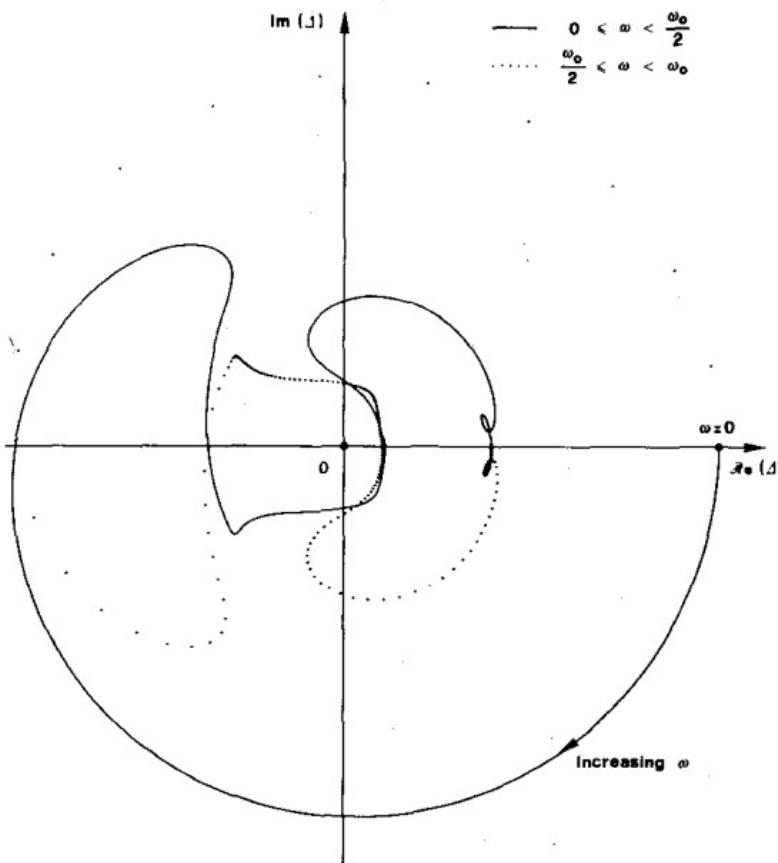
Stability (Rizzoli, 1985):Example – frequency divider  
(Rizzoli, 1985)

Fig. 5. Nyquist plot for a stable equilibrium condition of the frequency divider (nominal operating regime).


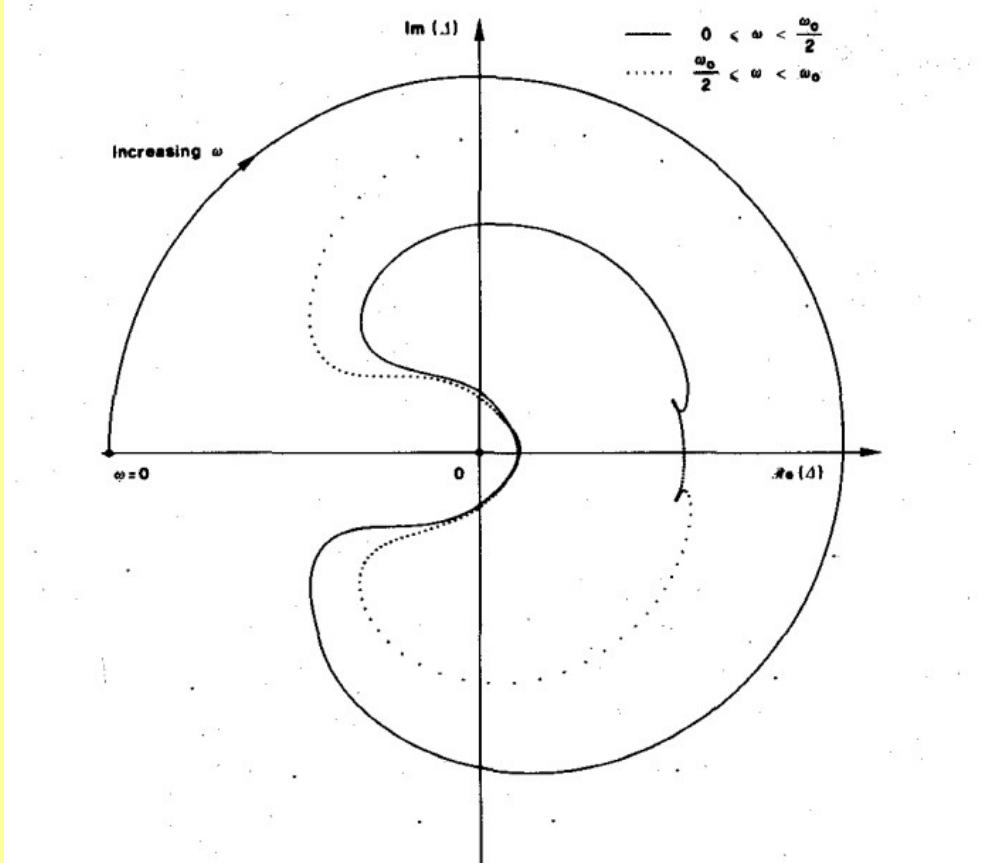
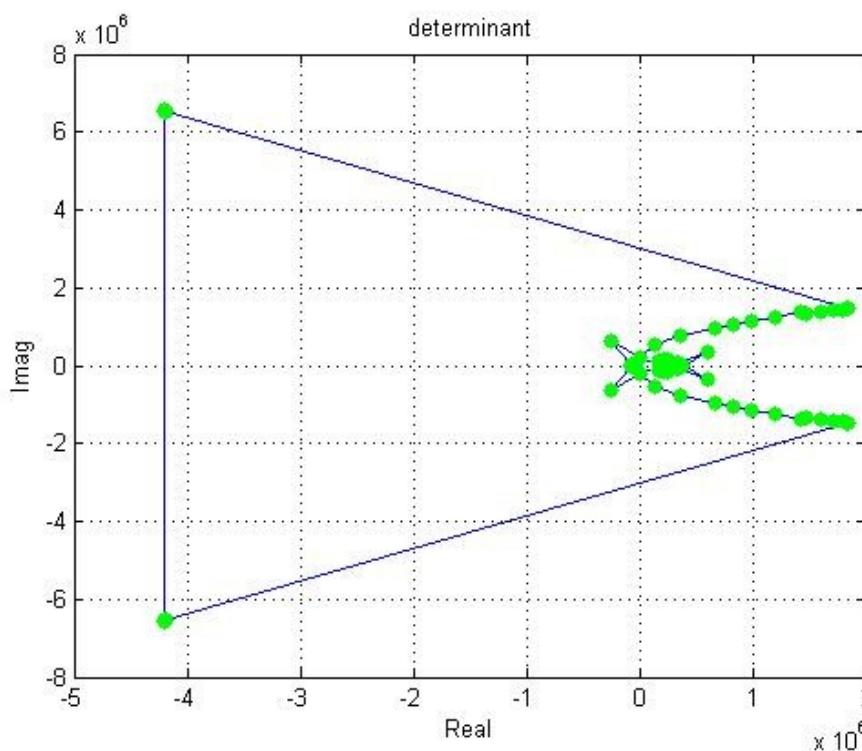



Fig. 6. Nyquist plot for an intrinsically unstable equilibrium condition of the frequency divider (hysteresis region).

Stability (Rizzoli, 1985):**stable**Example – frequency divider  
(Leuzzi, Pantoli, 2009)**unstable**

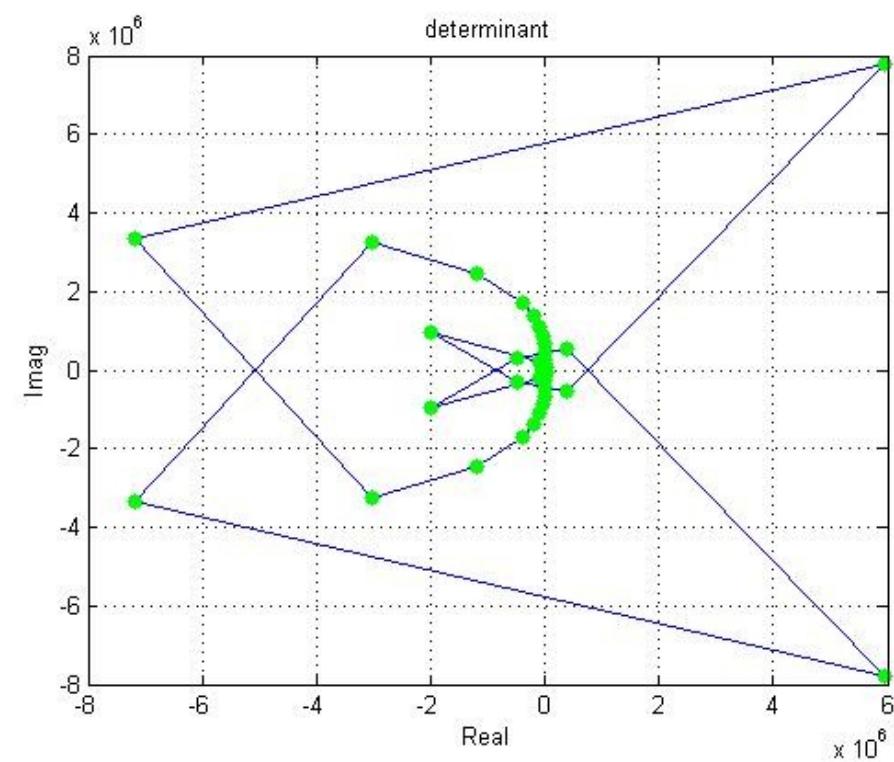**Not practical: results are often confusing and unstable**



### Stability (Collantes, 2001):

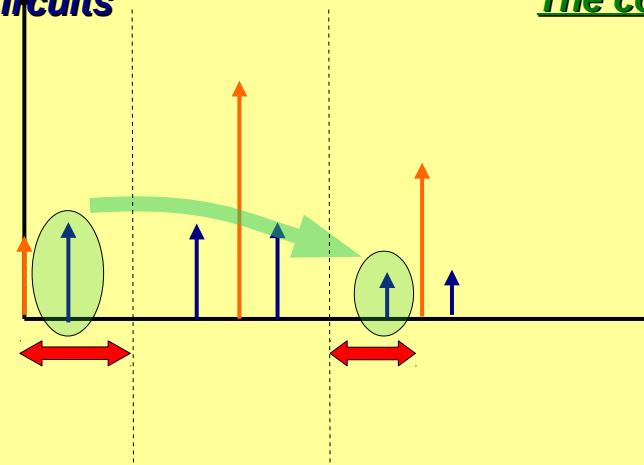



- Conversion gain between two ports

- Frequency sweep in the range

$$0 \div \left( \frac{f_{LO}}{2} \right)$$

- Fit to a polynomial function of the frequency
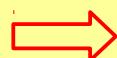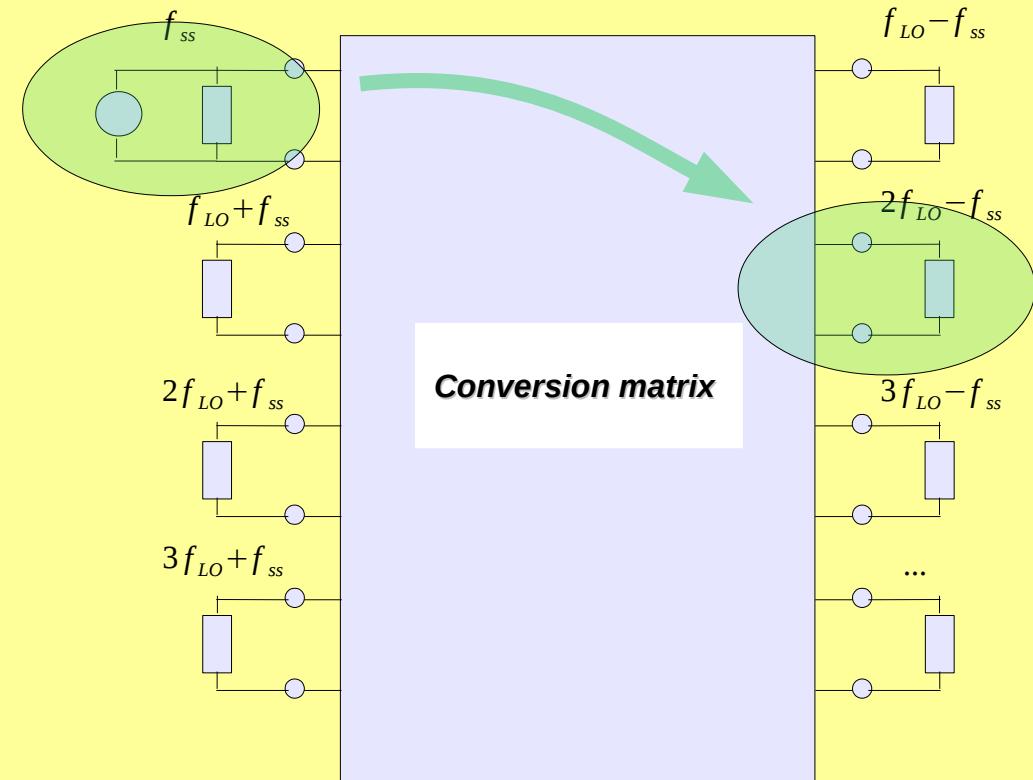
$$CG(j\omega_{ss}) = \frac{k \cdot (\omega_{ss} - z_1) \cdot (\omega_{ss} - z_2) \cdot \dots}{(\omega_{ss} - p_1) \cdot (\omega_{ss} - p_2) \cdot \dots}$$



Identification of the (complex) poles of the conversion gain function




## Stability (Collantes, 2001):

**Poles position may change with input power**


**Increasing input power**



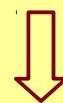**Increasing conversion gain of the nonlinear device**



**Increasing potential instability**

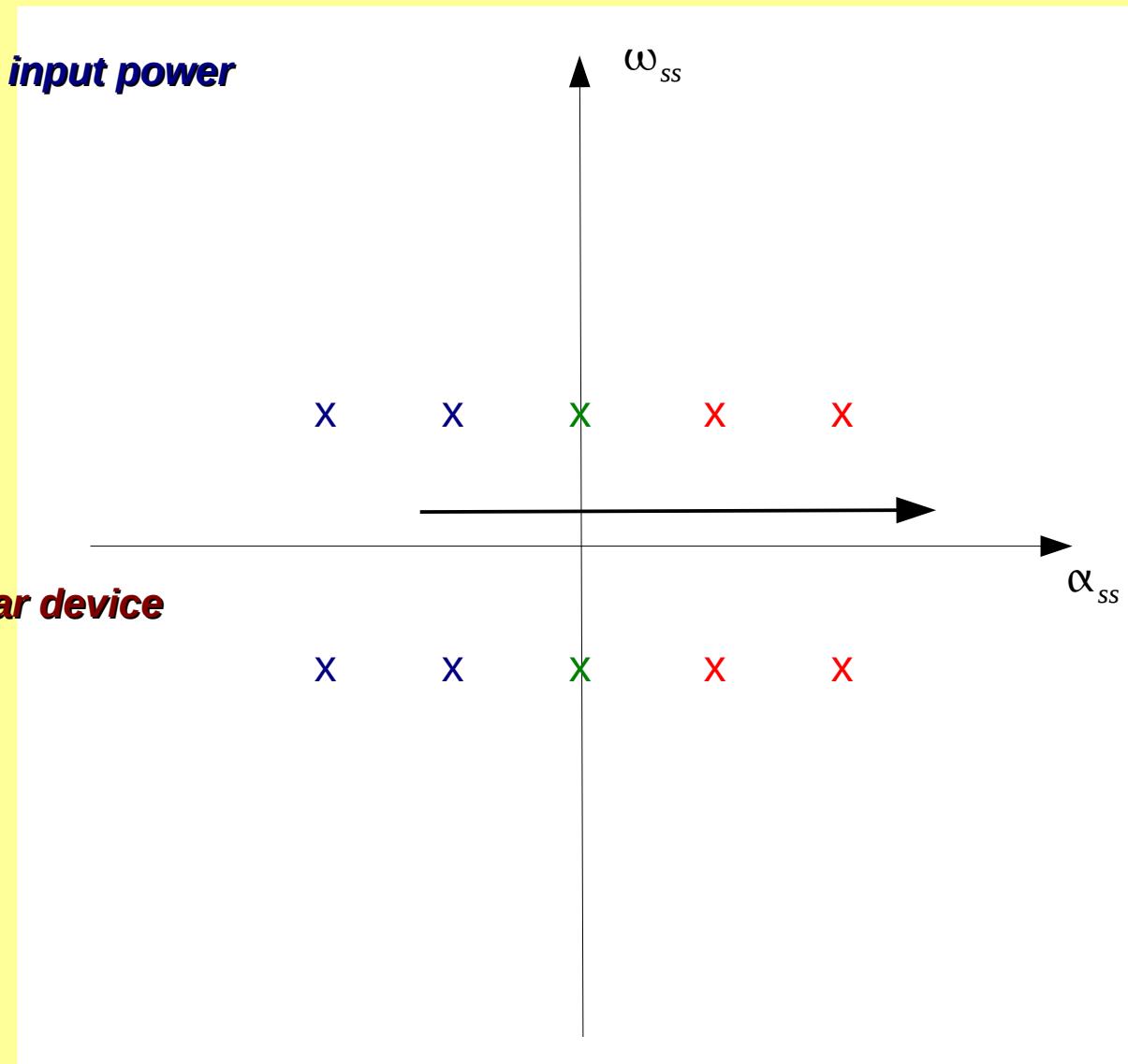




## Stability (Collantes, 2001):

**Poles position may be moved by redesign of the circuit:**

- Component values can be optimised

- No explicit design condition



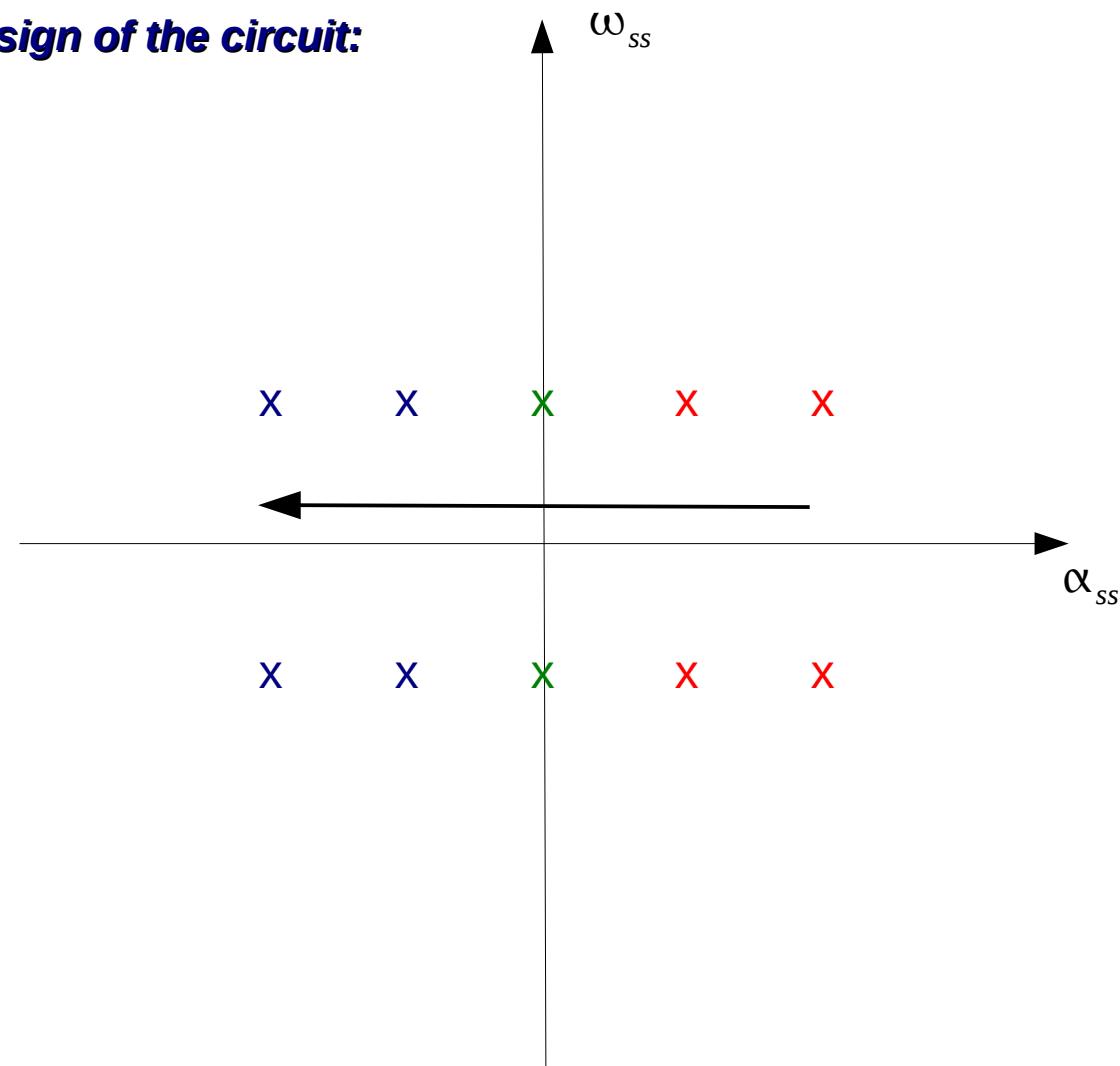




## Stability (Collantes, 2001):

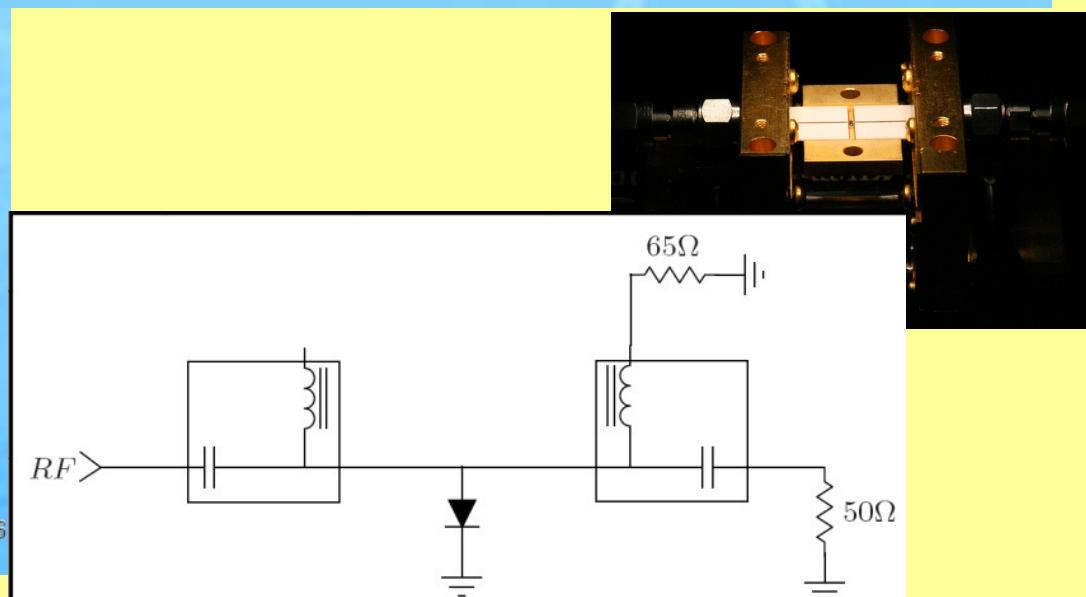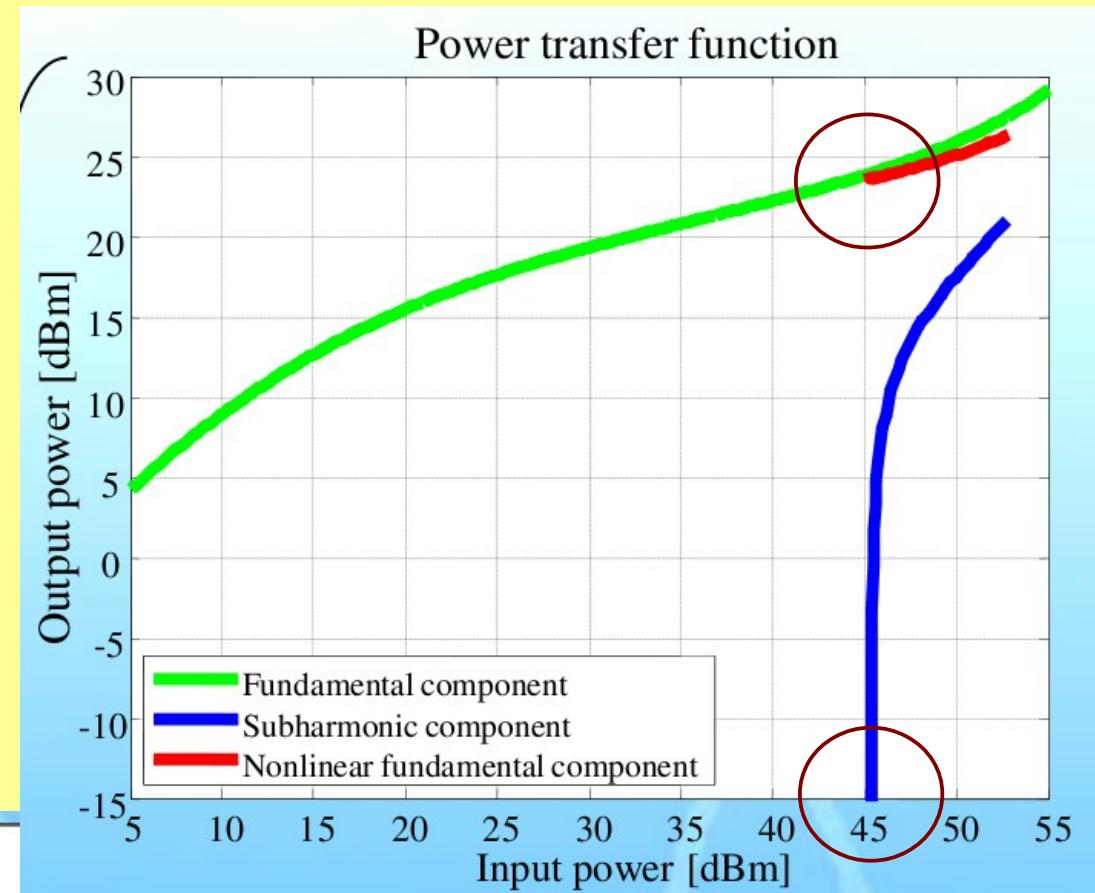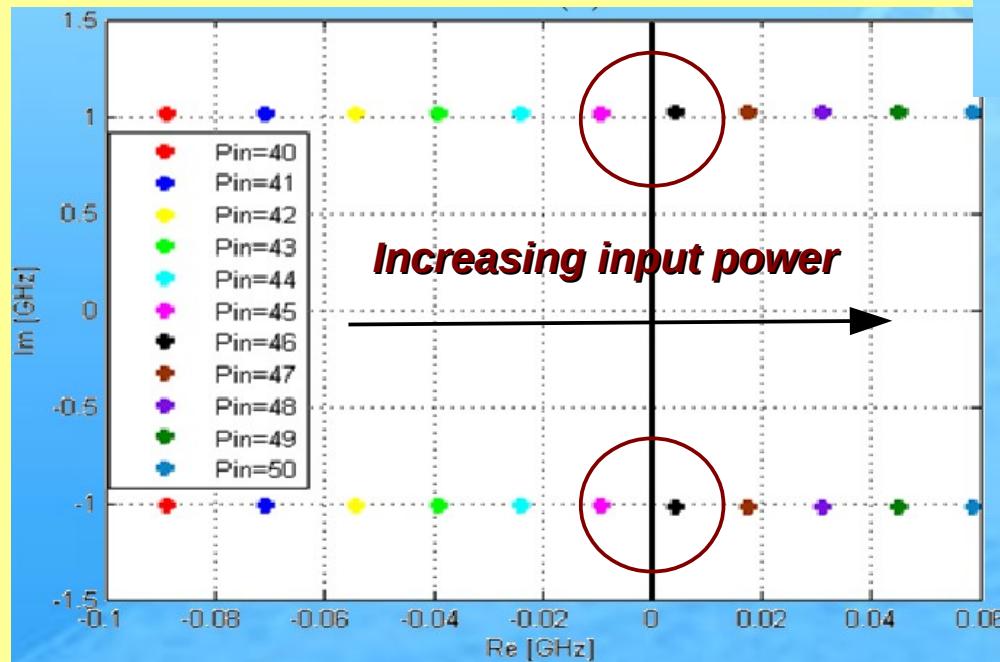**Example – Pin-diode limiter  
(Gatard, 2006; Pantoli, 2009)**



**Poles cross the y-axis when a  
spurious subharmonic signal appears**






## Stability (Collantes, 2001):

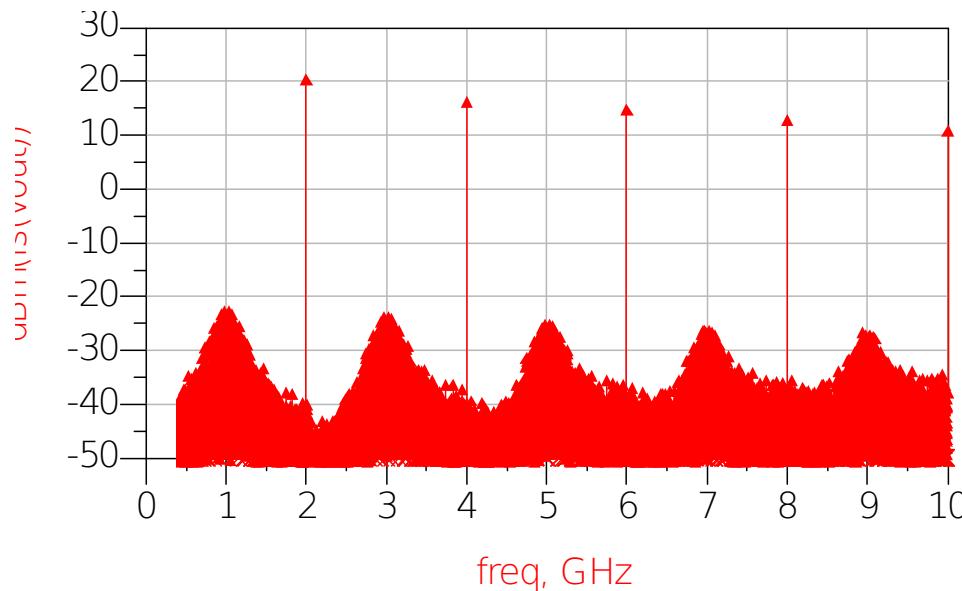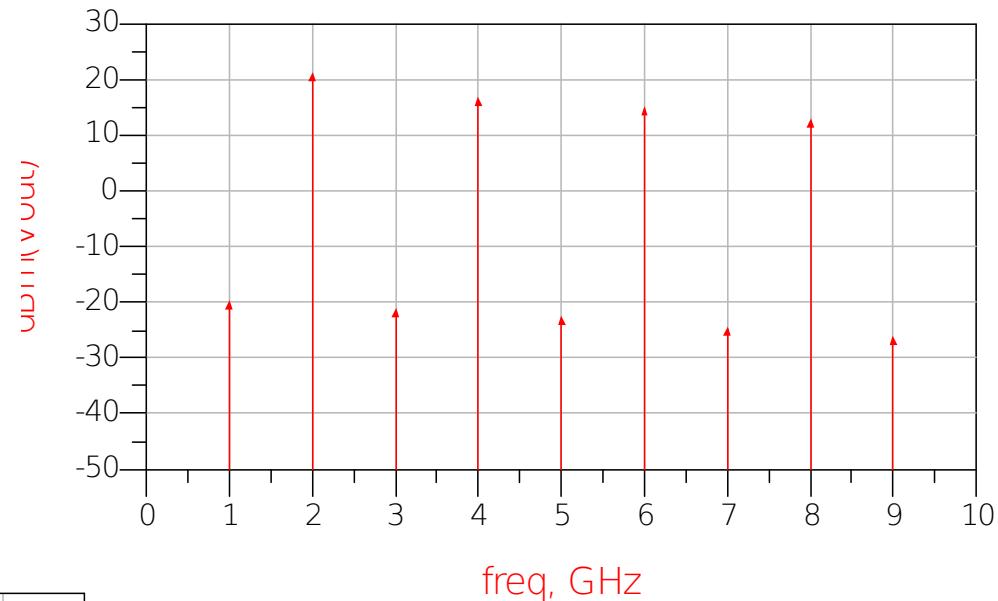Example – Pin-diode limiter  
(Gatard, 2006; Pantoli, 2009)







## Time-domain analysis
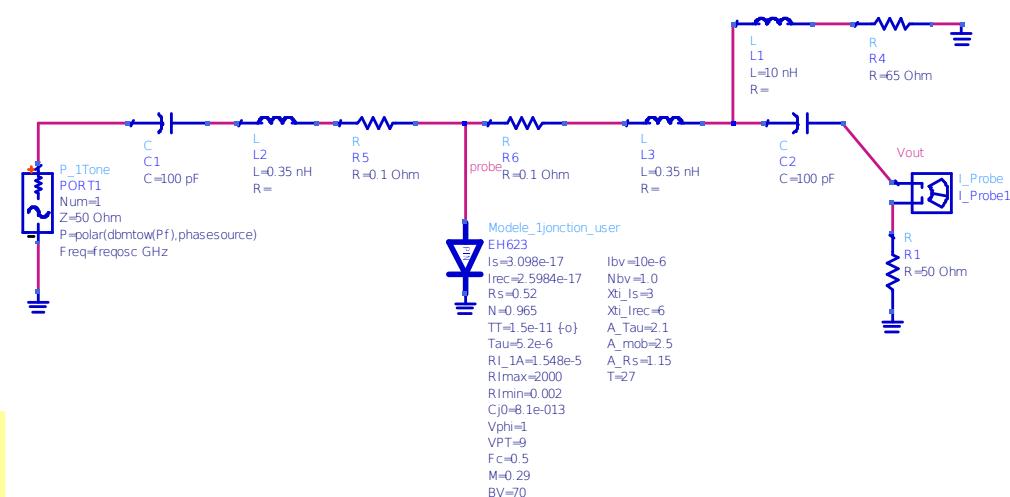
## Harmonic balance with auxiliary generator



Stability (Di Paolo, 2002):

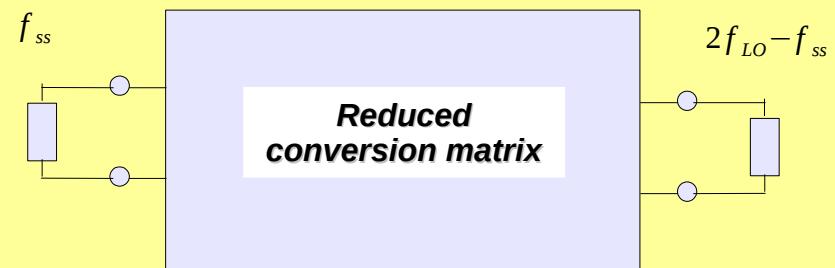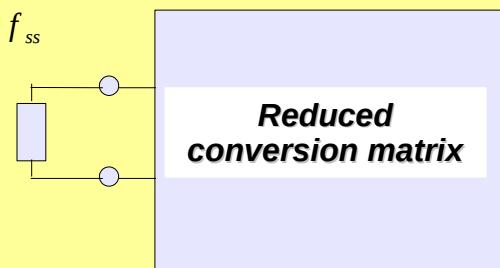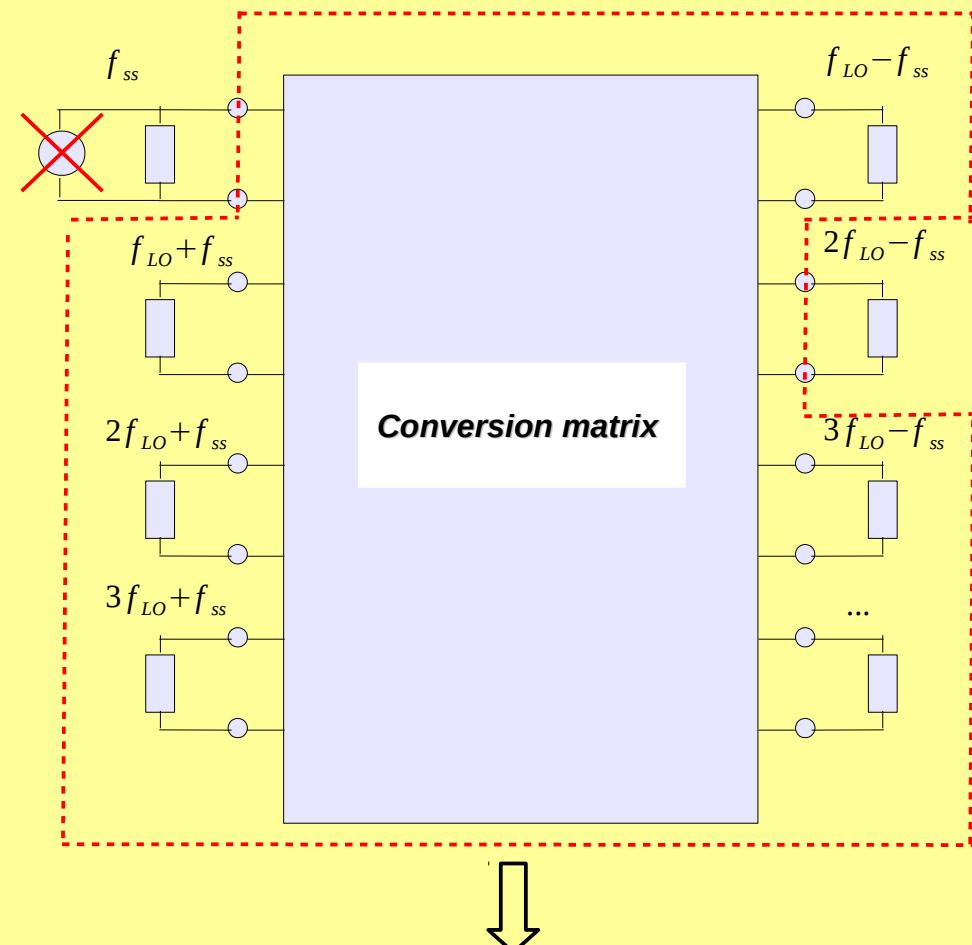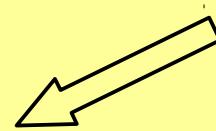- Removal of the small-signal excitation
- Reduction to a one-port or two-port network
- Linear stability design



Stability (Di Paolo, 2002):**Linear stability design (one port):****Stability**



$$|\Gamma_i(\omega_{ss})| < 1$$

**Potential instability**

$$|\Gamma_i(\omega_{ss})| > 1$$


**Oscillation**

$$\Gamma_L(\omega_{ss}) \cdot \Gamma_i(\omega_{ss}) = 1$$

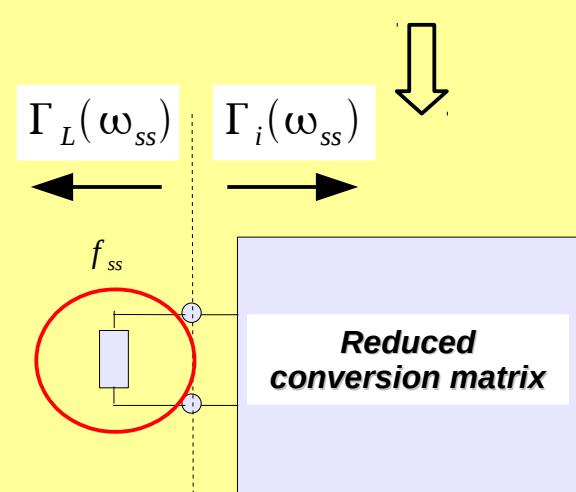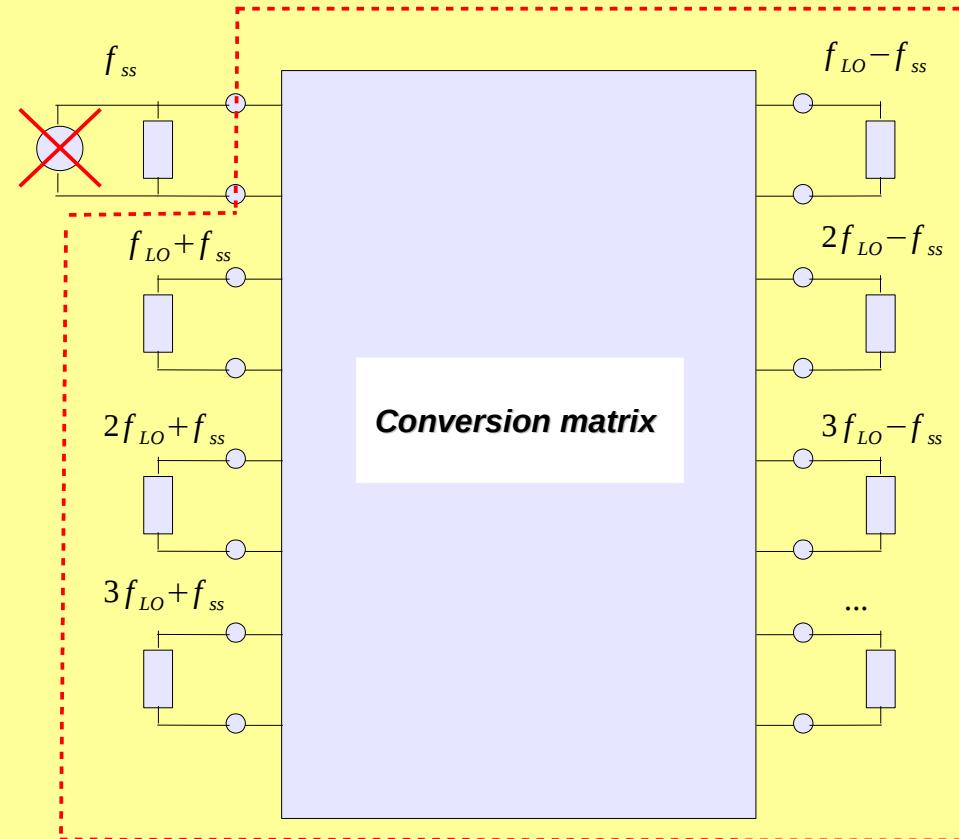**Redesign of  $\Gamma_L(\omega_{ss})$  for stability**

Stability (Di Paolo, 2002):

Redesign of the linear networks:

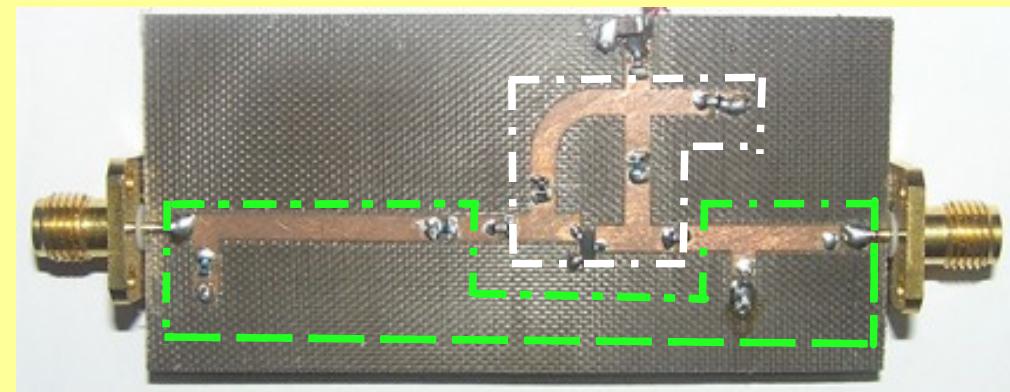


Impedance adjustment  
at converted frequencies

$$Z_L(nf_{LO} \pm f_s)$$

No impedance change at large-signal  
fundamental and harmonic frequencies

$$Z_L(nf_{LO})$$

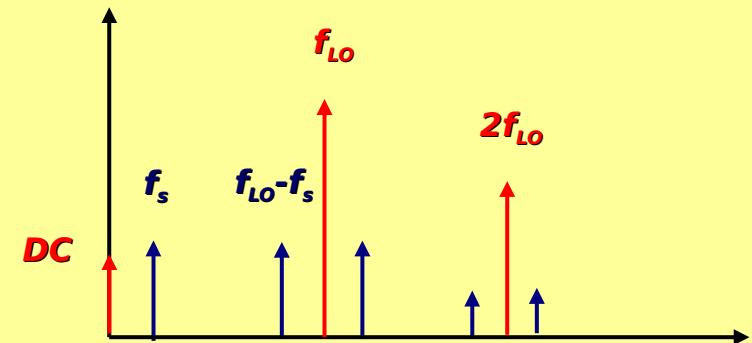


Otherwise the conversion matrix must be recomputed,  
and the large-signal performances change



Special case:



$$f_{ss} = \frac{f_0}{2}$$

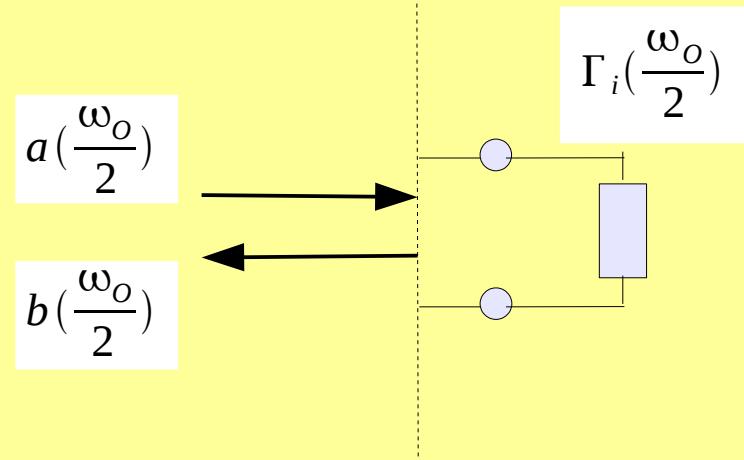

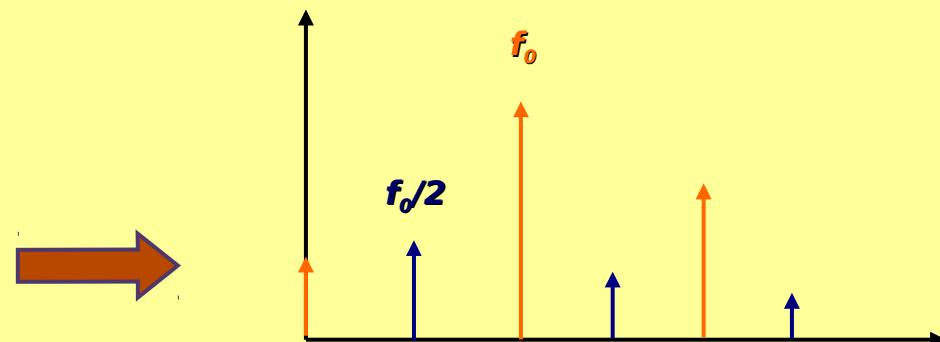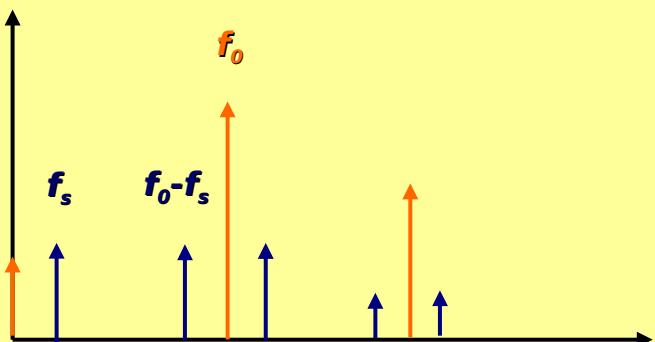**The conversion matrix assumes a different formalism**

$$\begin{bmatrix} b_r \\ b_i \end{bmatrix} = \begin{bmatrix} \Gamma_{11} & \Gamma_{12} \\ \Gamma_{21} & \Gamma_{22} \end{bmatrix} \cdot \begin{bmatrix} a_r \\ a_i \end{bmatrix}$$

$$\begin{aligned} a &= a_r + j a_i \\ b &= b_r + j b_i \end{aligned}$$



**Special case:**

$$f_{ss} = \frac{f_0}{2}$$

***The reflection coefficient depends on the phase of the incident wave***




$$\begin{bmatrix} b_r \\ b_i \end{bmatrix} = \begin{bmatrix} \Gamma_{11} & \Gamma_{12} \\ \Gamma_{21} & \Gamma_{22} \end{bmatrix} \cdot \begin{bmatrix} a_r \\ a_i \end{bmatrix}$$

$$a = a_r + j a_i$$

$$b = b_r + j b_i$$

$$a\left(\frac{\omega_o}{2}\right)$$

$$b\left(\frac{\omega_o}{2}\right)$$

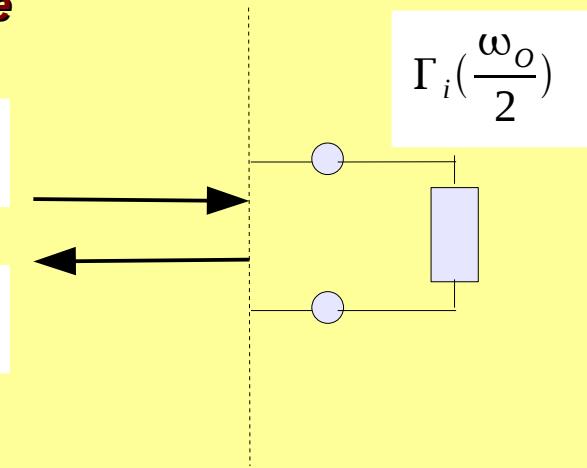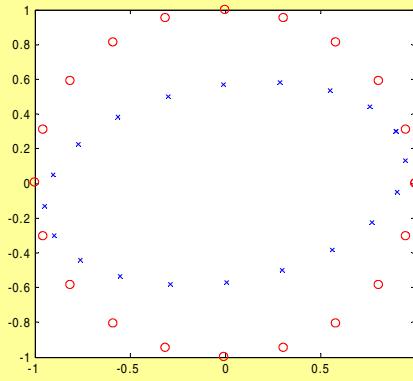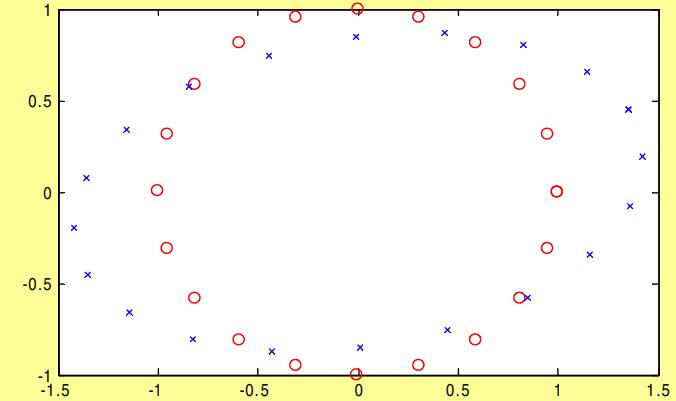 **$|b| < |a|$**  **$|b| > |a|$** ***The phase reference is the phase of the large signal at  $f_0$*** 

(Measurements by D.Schreurs)



**Special case:**

$$f_{ss} = \frac{f_0}{2}$$


***The oscillation condition becomes:***

$$\Gamma_s = \frac{1}{\Gamma_i}$$



$$\det \left( \begin{bmatrix} \Gamma_{s,r} & -\Gamma_{s,i} \\ \Gamma_{s,i} & \Gamma_{s,r} \end{bmatrix} + \begin{bmatrix} \Gamma_{in11} & \Gamma_{in12} \\ \Gamma_{in21} & \Gamma_{in22} \end{bmatrix} \right) = 0$$

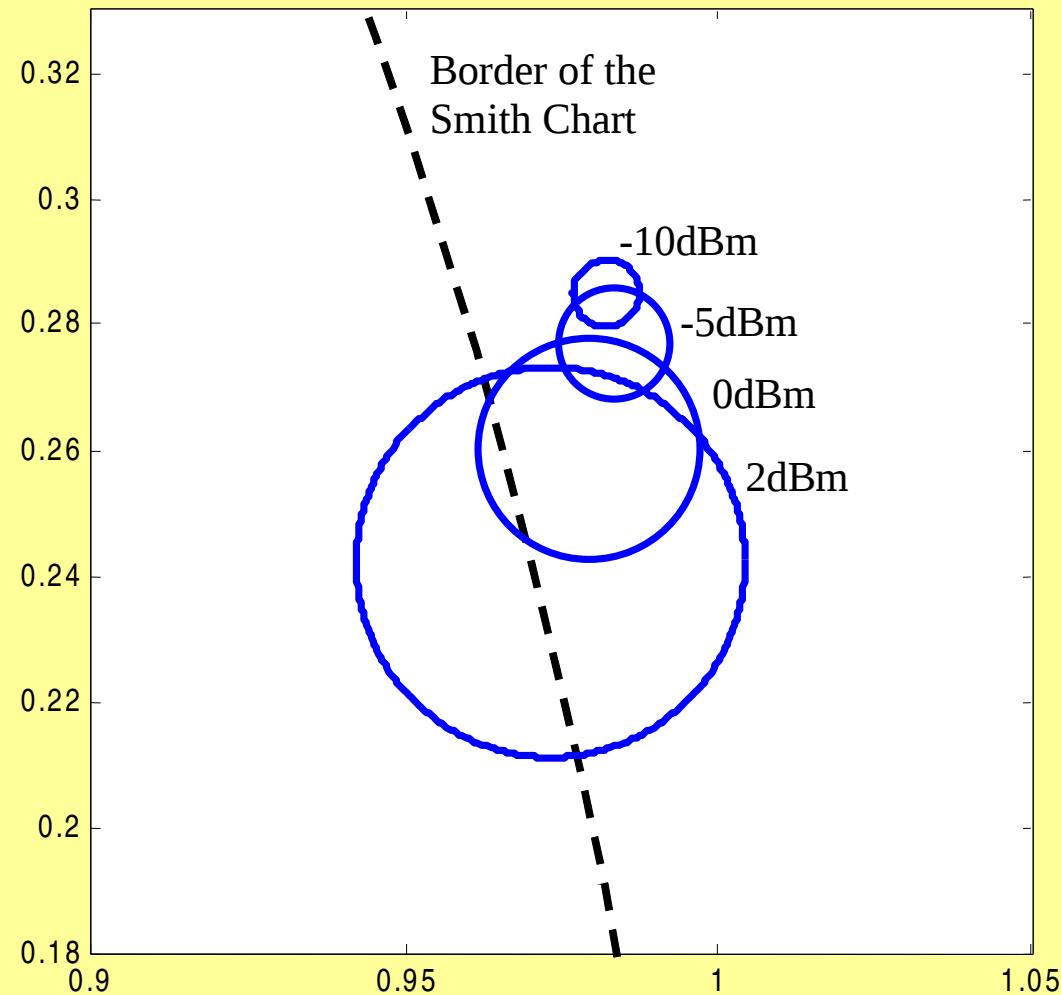
***The loads giving oscillation form a circle***






## Applications: medium-power amplifier



### **First design: stable amplifier**

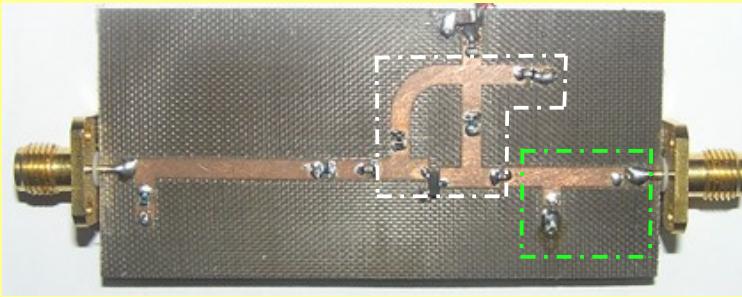
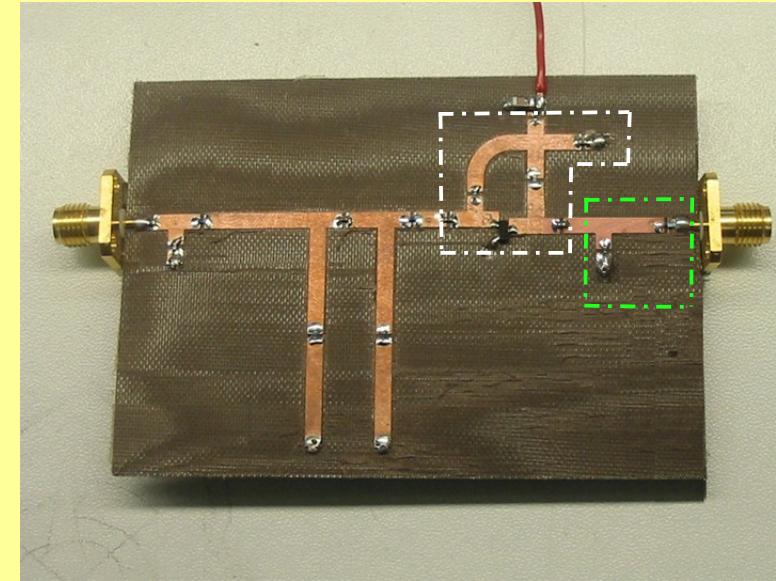
### **Second design: modified, unstable amplifier**



- **Same biased transistor**
- **Same output matching network**
- **Modified input matching network**

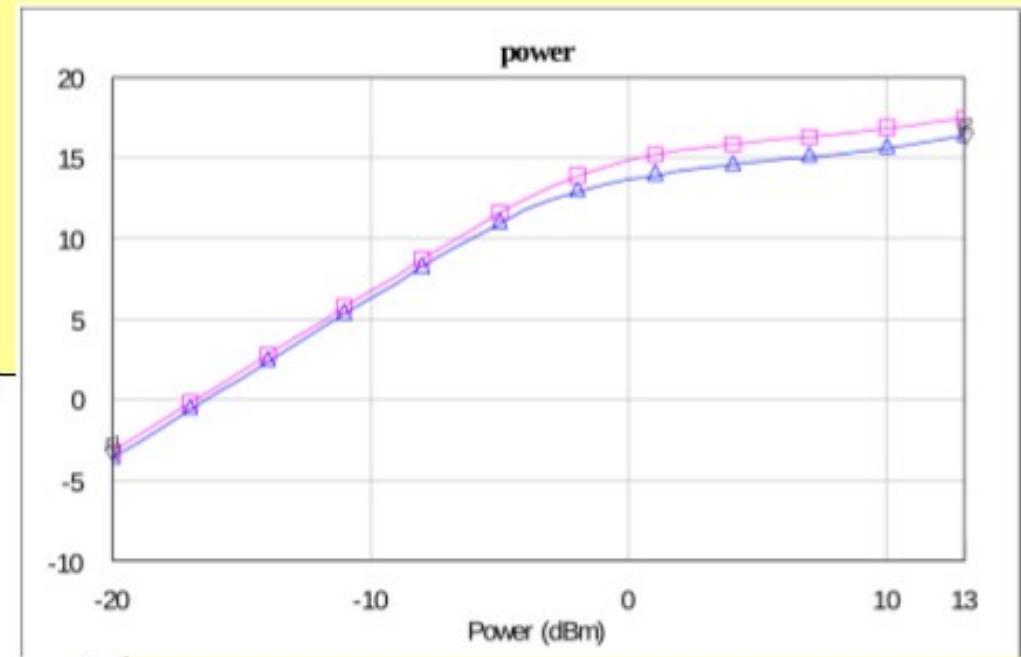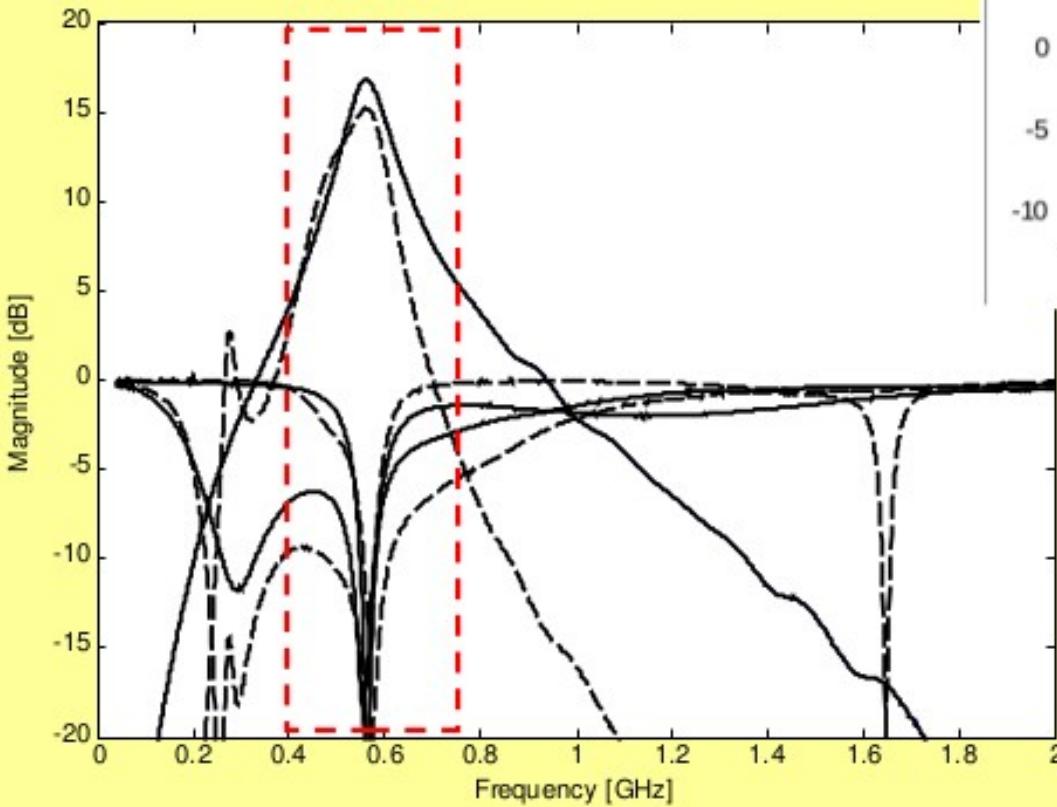Applications: medium-power amplifier


**Harmonic balance simulations**

**Measured S-parameters**




## The stable amplifier

**Output power**

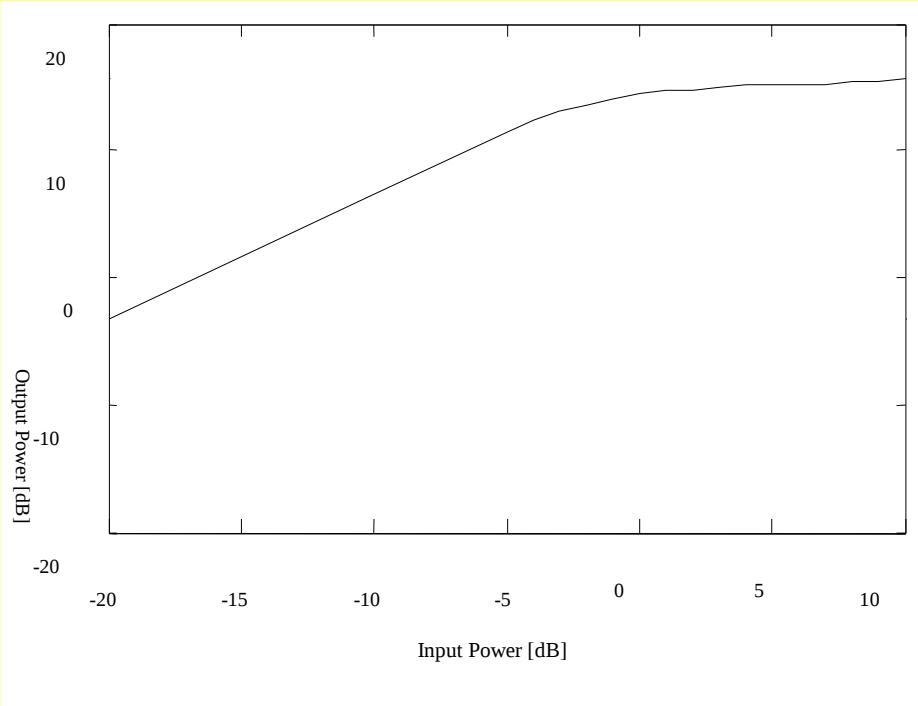


**Output power spectrum**

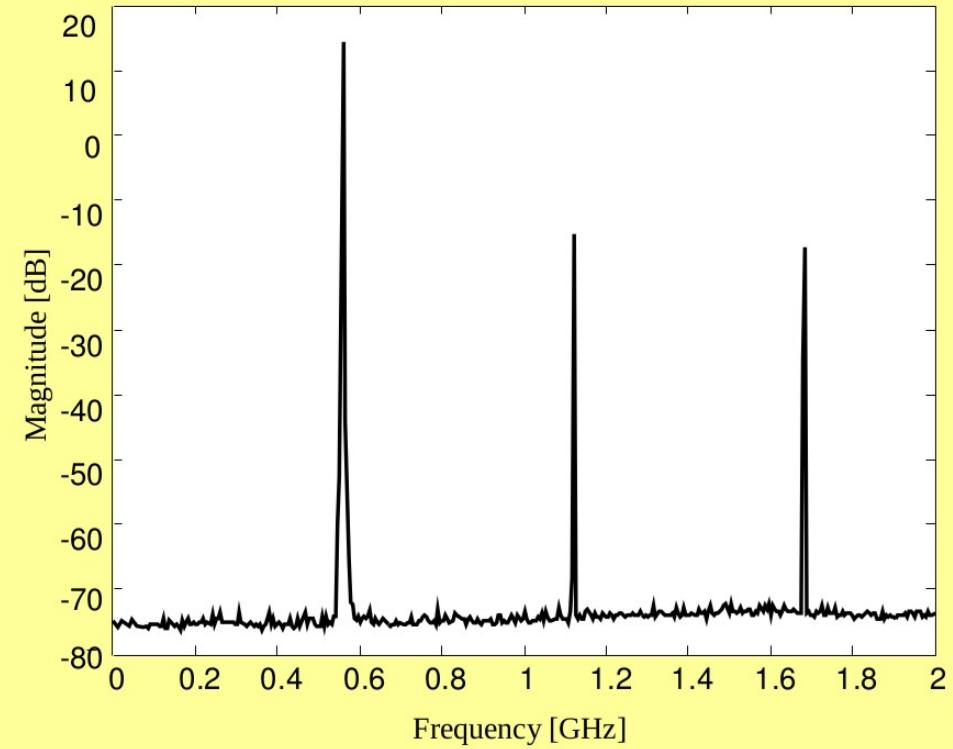



## Stability check of the amplifier

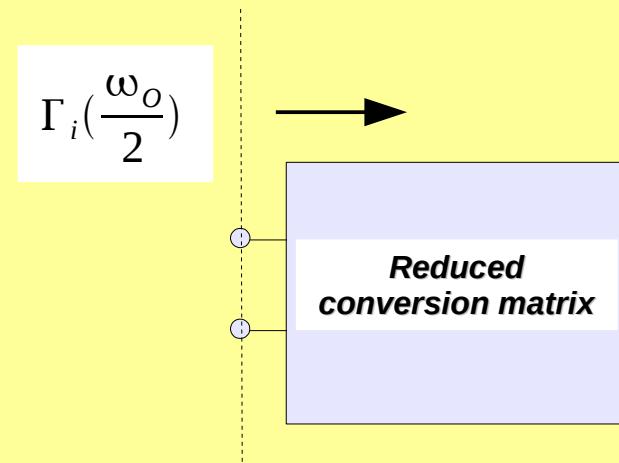


**Conversion matrix**

↓  
**Reflection coefficient at  $f_o/2$**

↓  
**Potential instability**

**Stable amplifier**

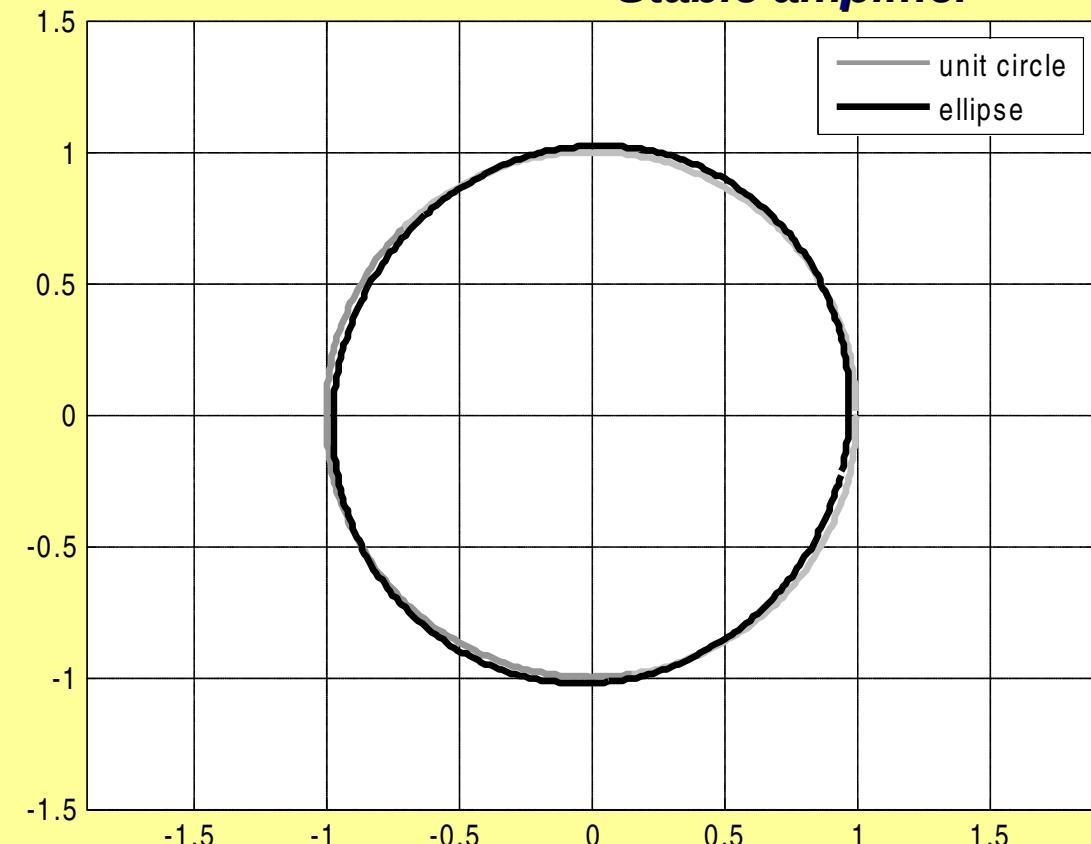




## Redesign of the amplifier for instability at

$$f_{ss} = \frac{f_0}{2}$$

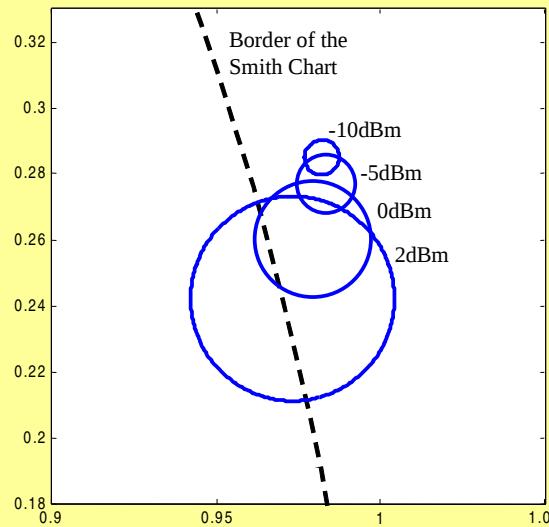
**Unstable region at  $f_0/2$  at input**



**Only one load at input has been changed**

**The output matching network is unchanged**

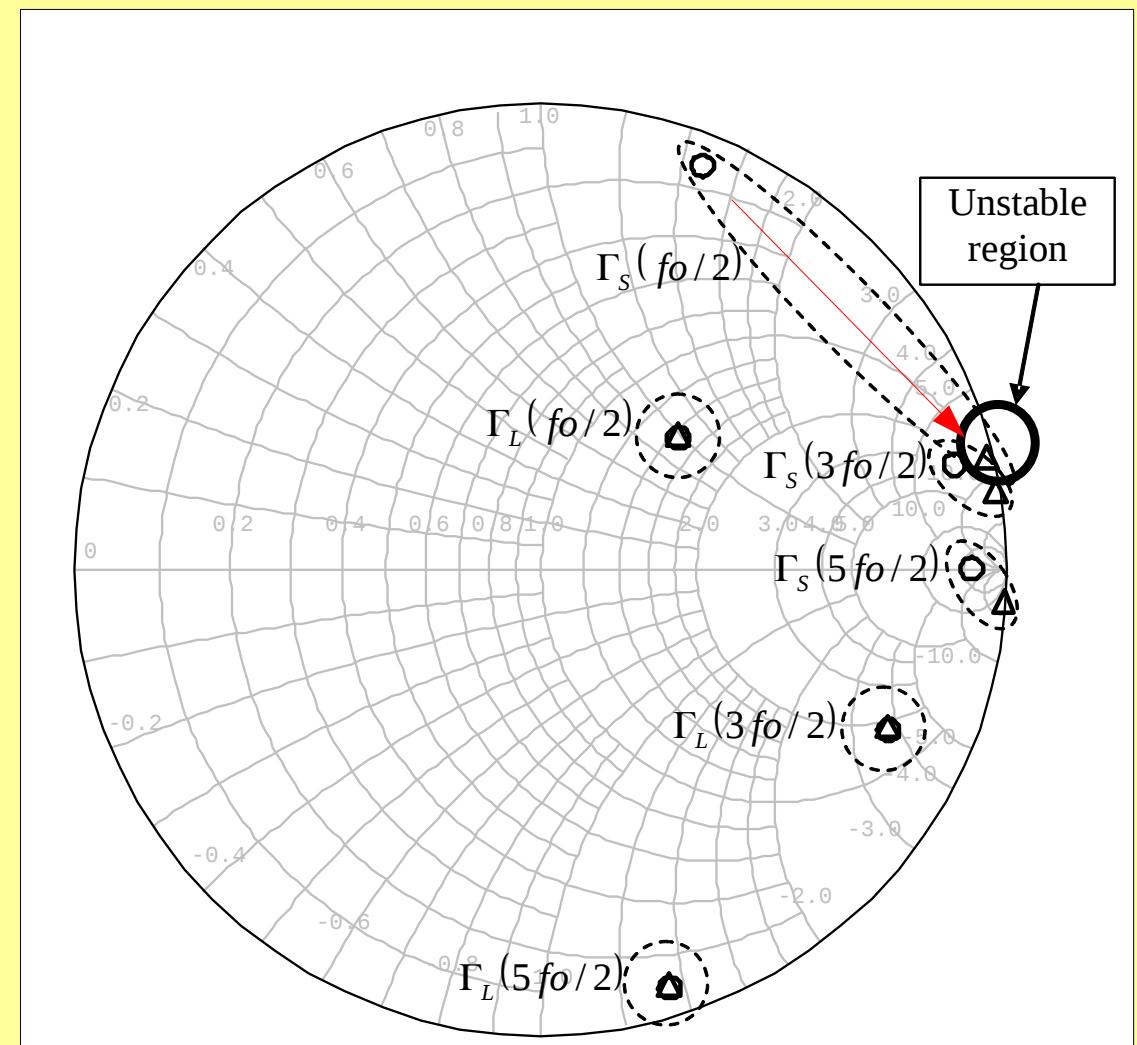**Modified loads at fractional frequencies**






**Redesign of the amplifier for instability at**

$$f_{ss} = \frac{f_0}{2}$$


**Loads at fundamental frequency and harmonics are unchanged**

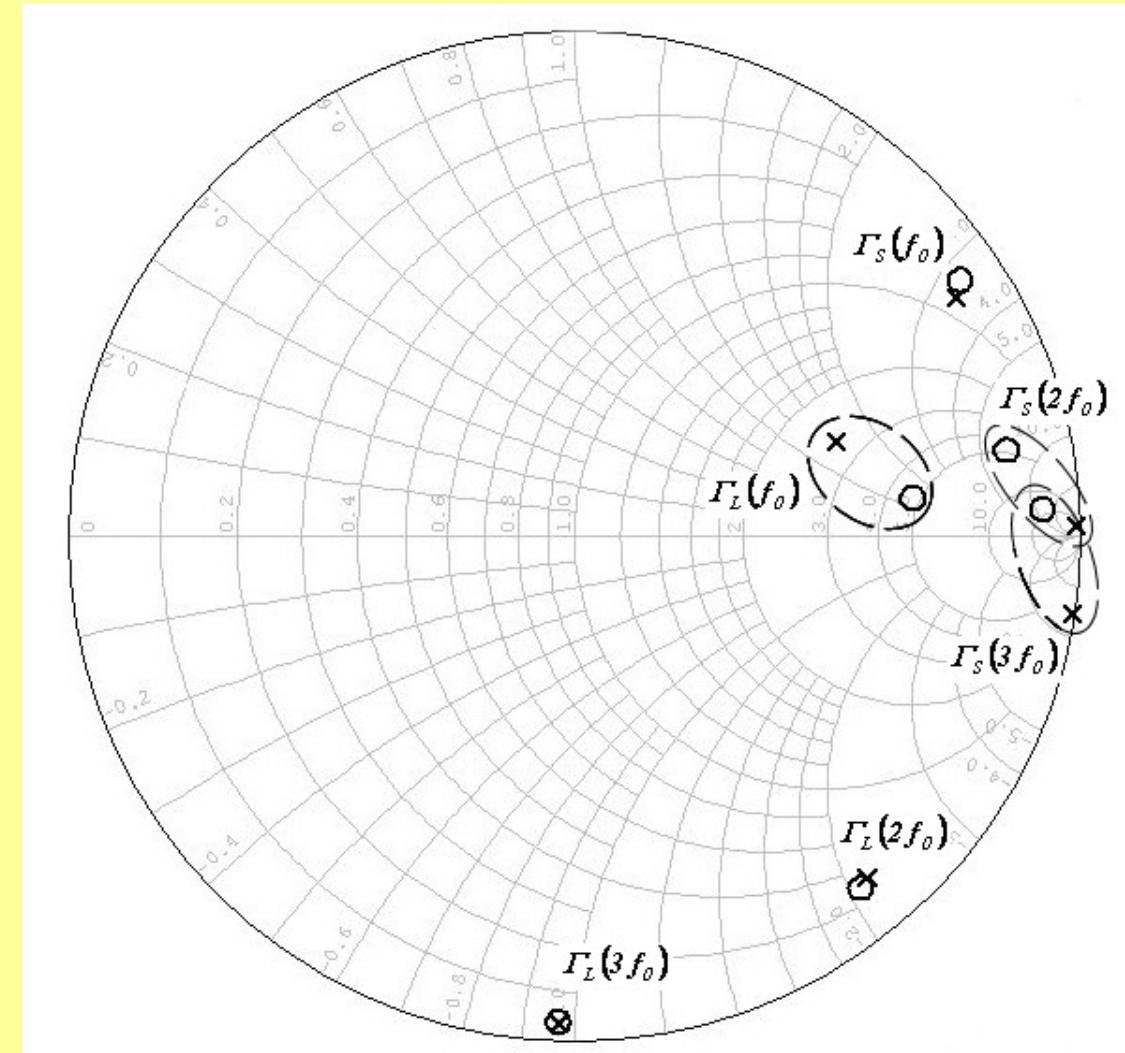**The conversion matrix remains the same**






## Redesigned amplifier - unstable

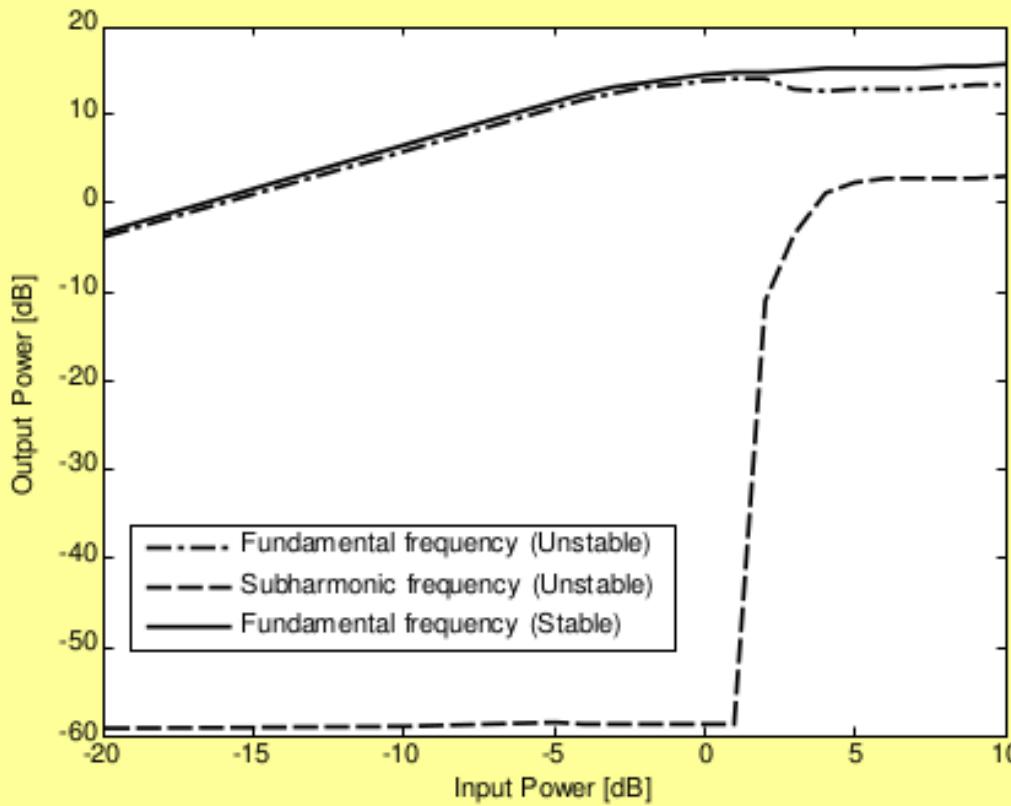


**Output power spectrum**

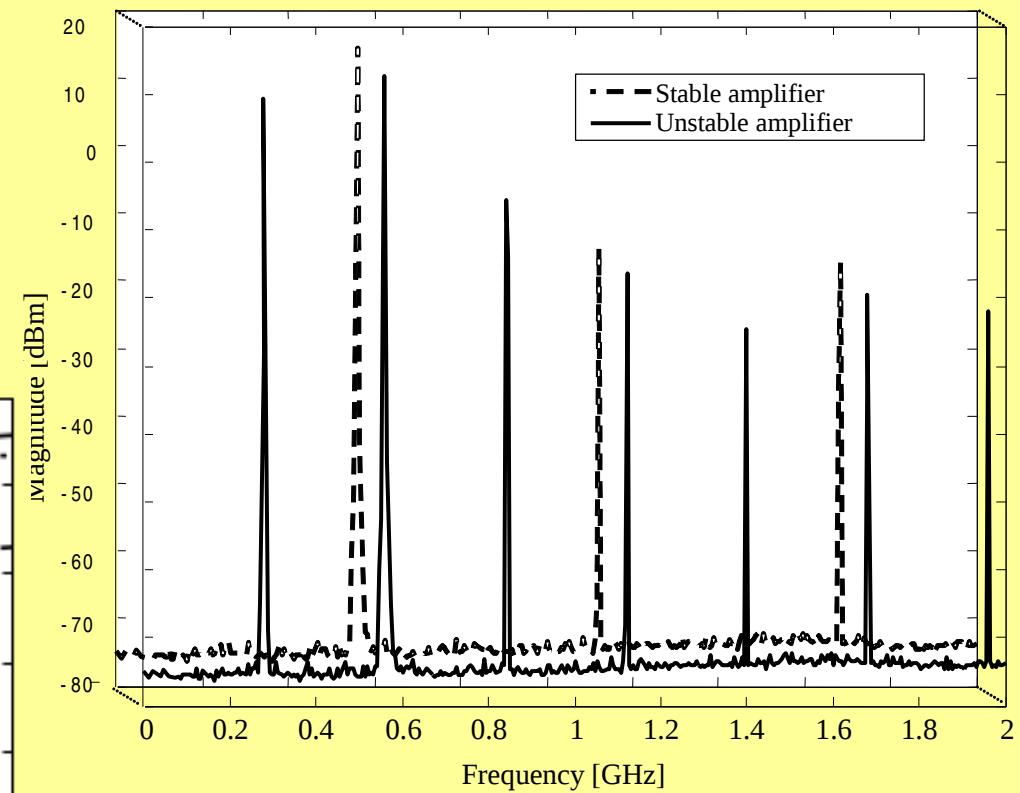


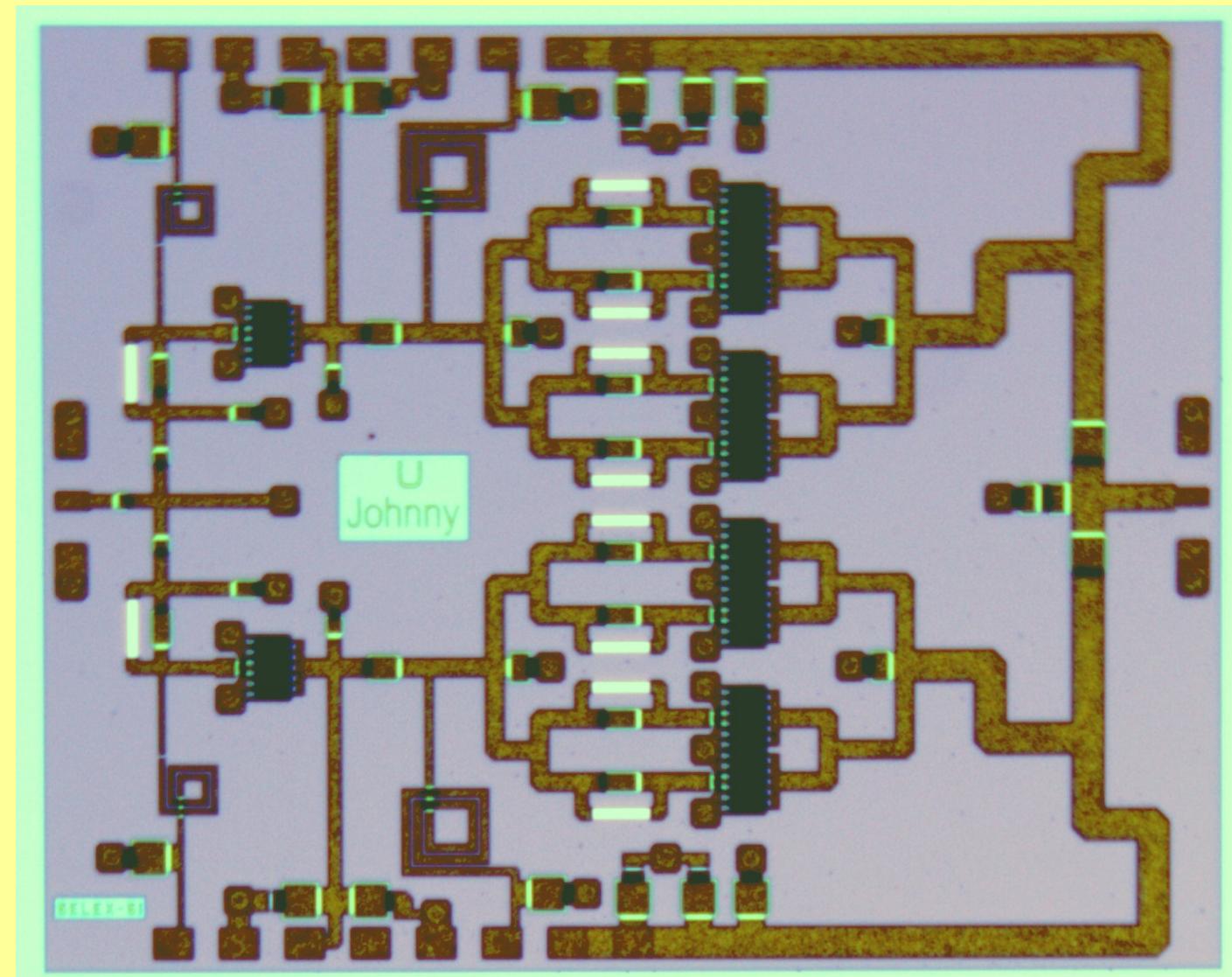
## Special case: parallel power amplifier





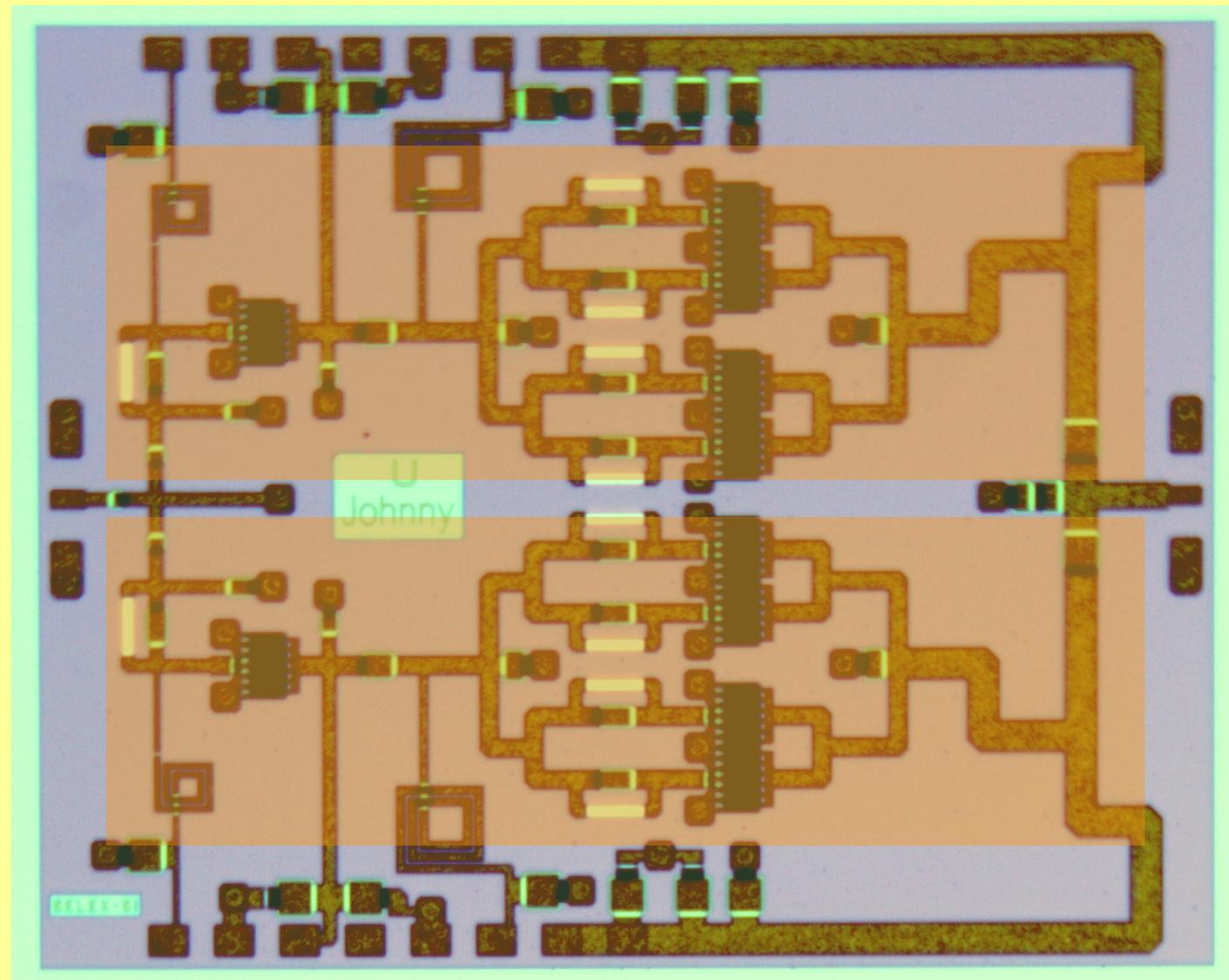
## Single-transistor approach:

*The symmetry of the amplifier is exploited*

*The amplifier must be symmetric wrt a longitudinal axis*






## Single-transistor approach:

*The symmetry of the amplifier is exploited*

*The amplifier must be symmetric wrt a longitudinal axis*

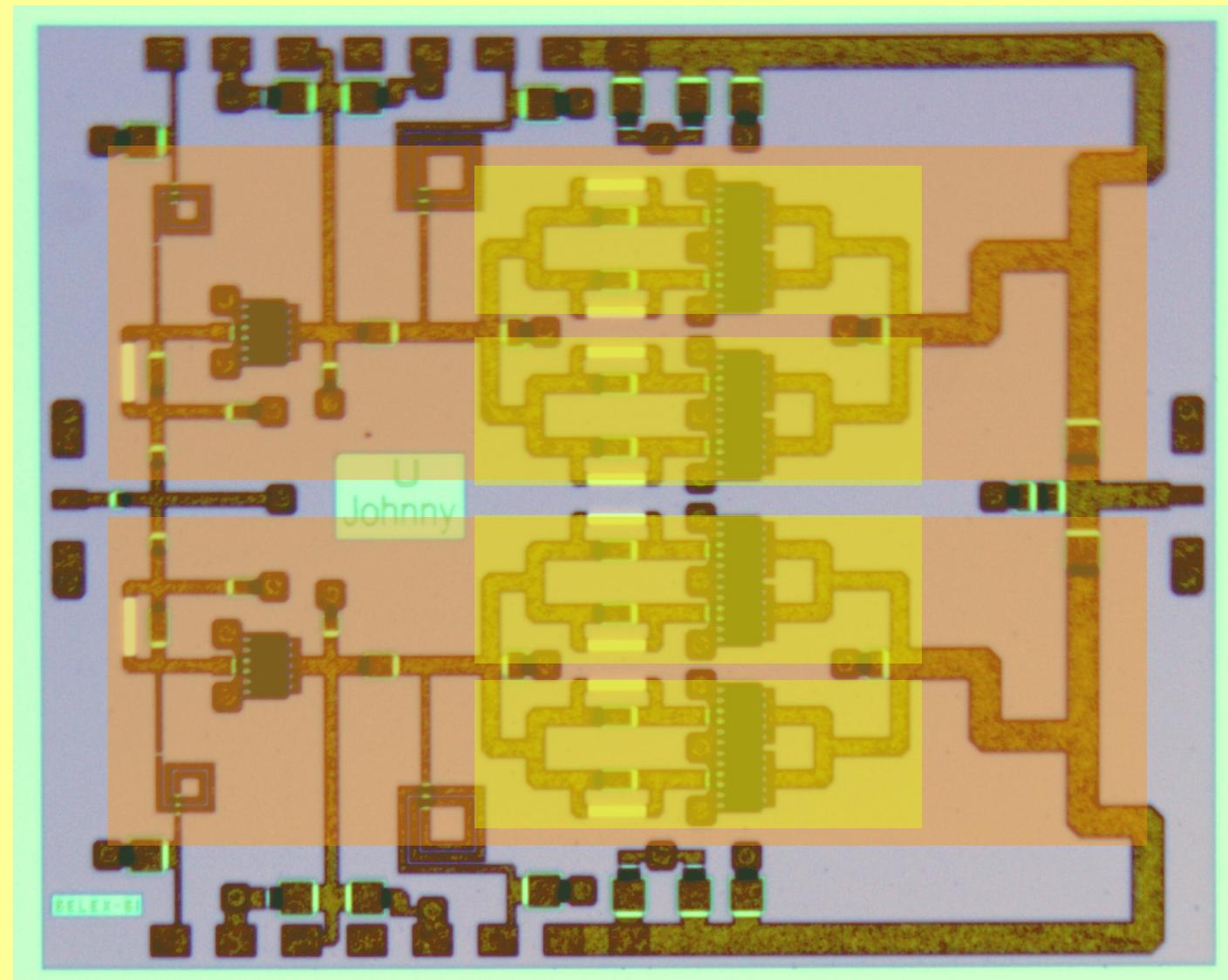*Each half must in turn be symmetric wrt its longitudinal axis*






## Single-transistor approach:

*The symmetry of the amplifier is exploited*

*The amplifier must be symmetric wrt a longitudinal axis*

*Each half must in turn be symmetric wrt its longitudinal axis*

*...and so on.*

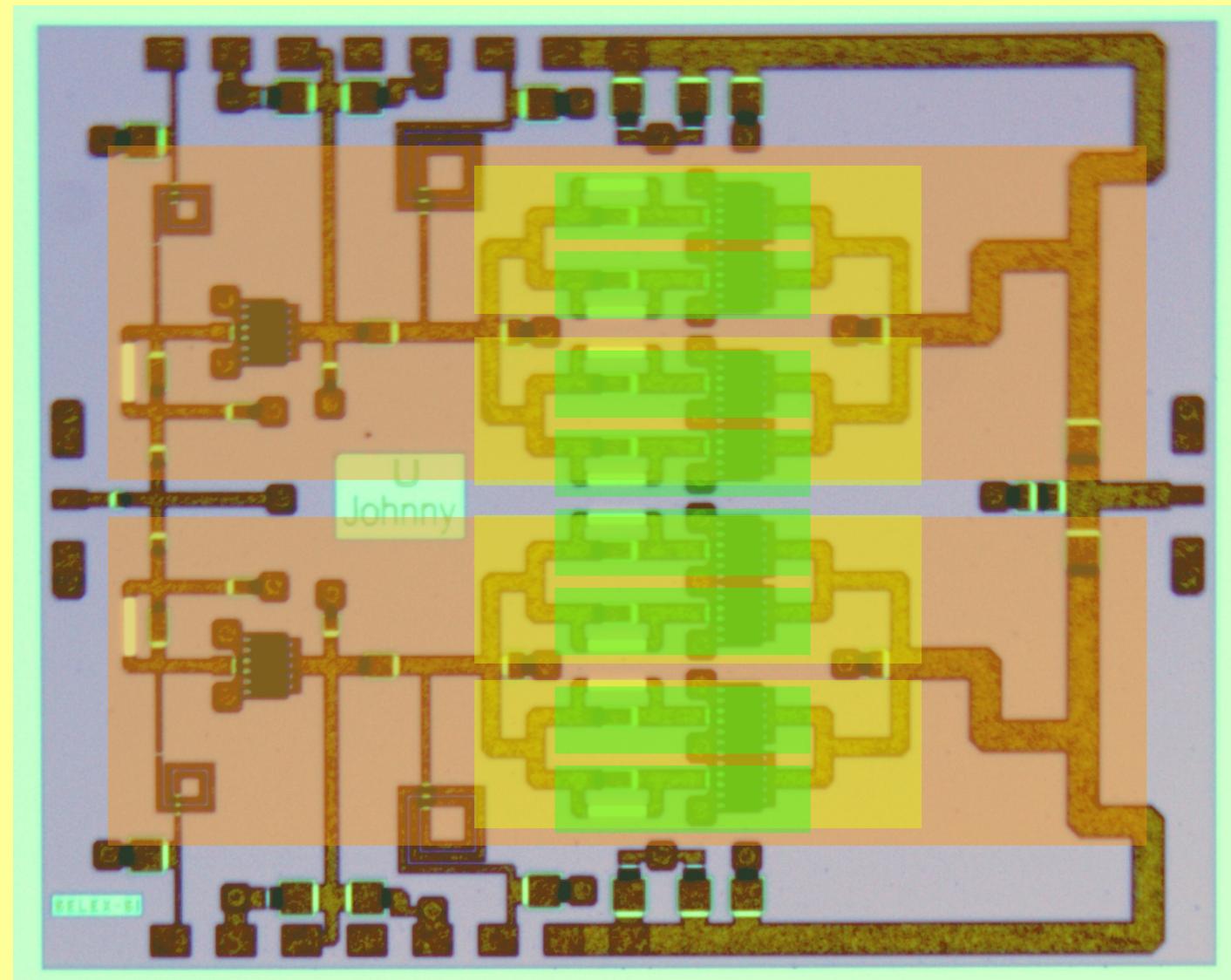




## Single-transistor approach:

***Identification of the symmetry modes***

***Example: a 4-transistor amplifier***





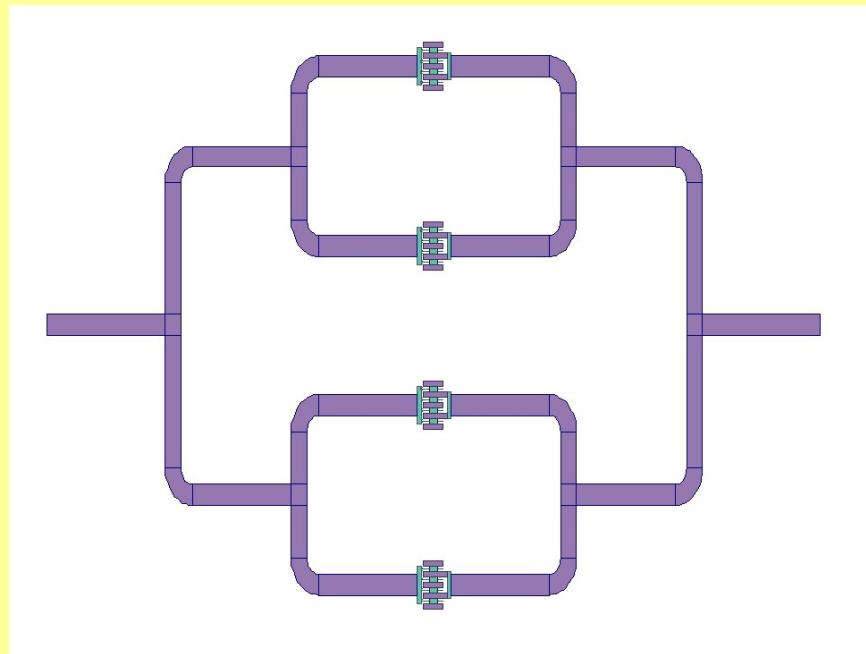




## Single-transistor approach:

**Identification of the symmetry modes**

**Example: a 4-transistor amplifier**

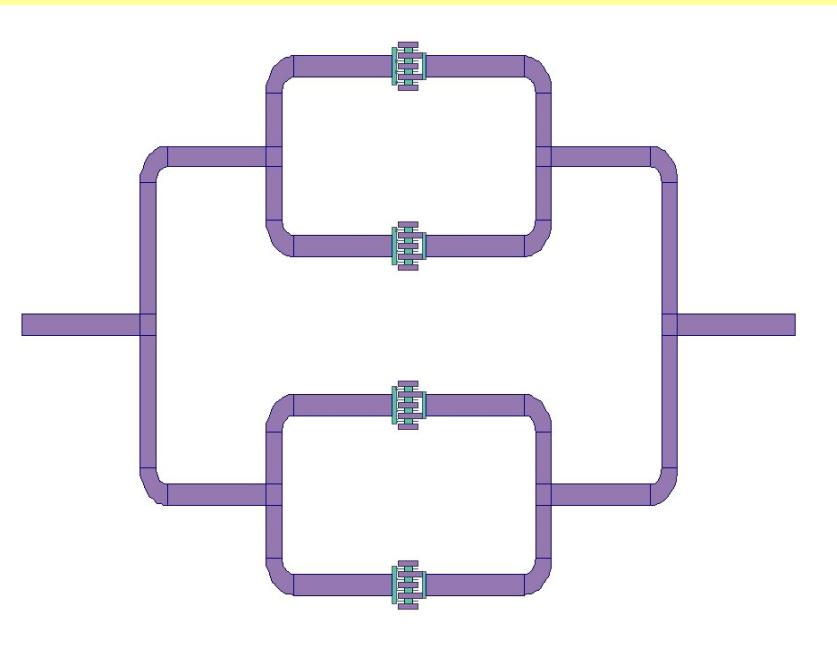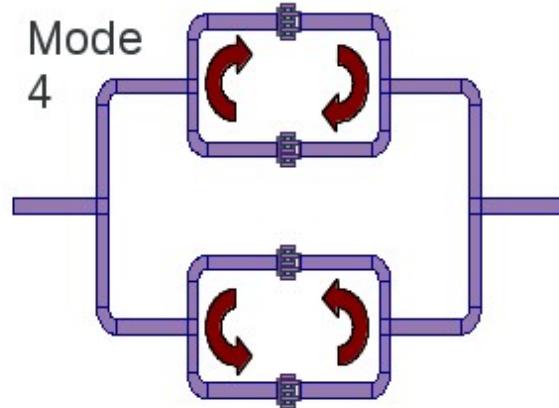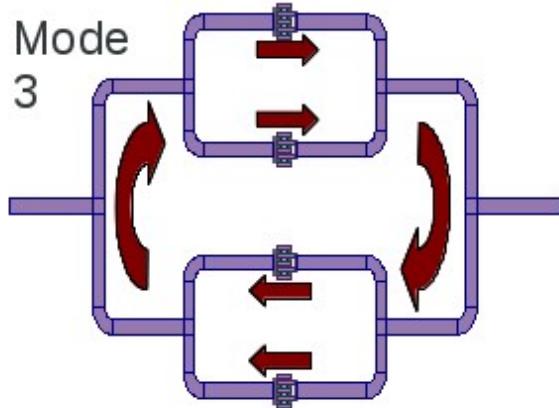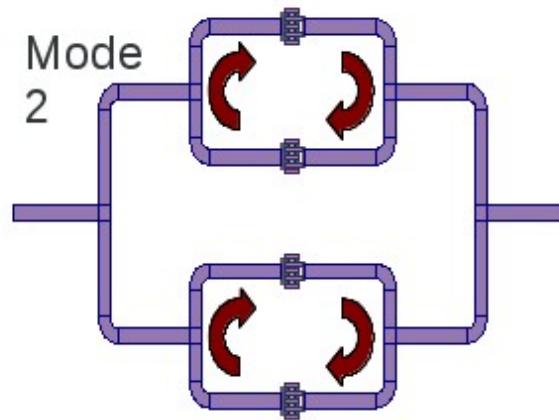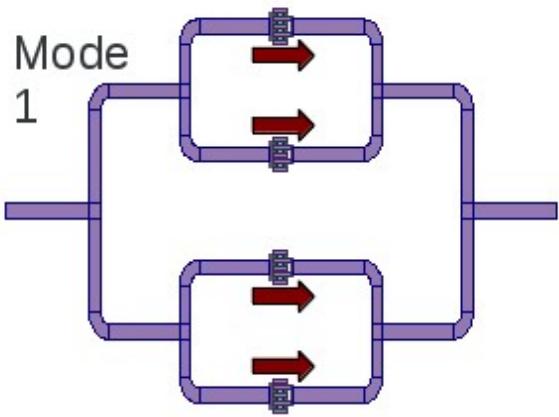






**Four modes are found**



## Single-transistor approach:

**Identification of the symmetry modes**

**Example: a 4-transistor amplifier**

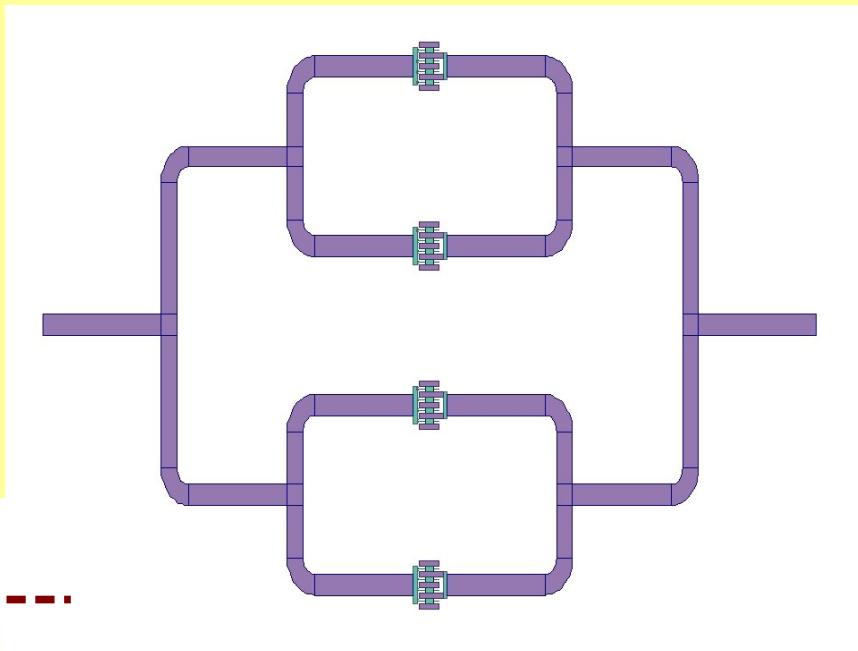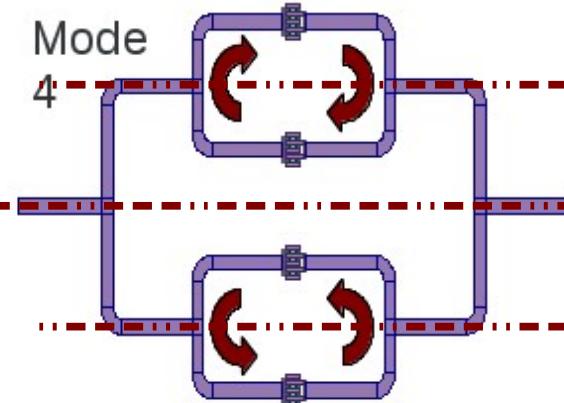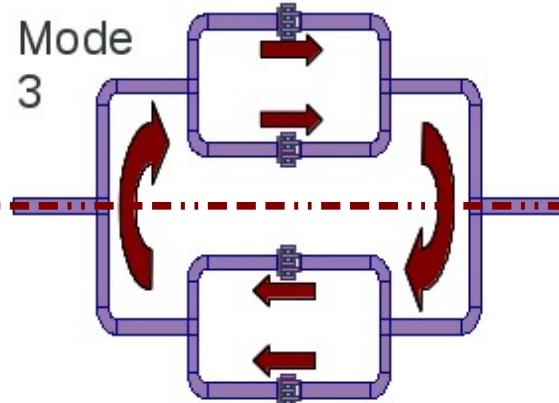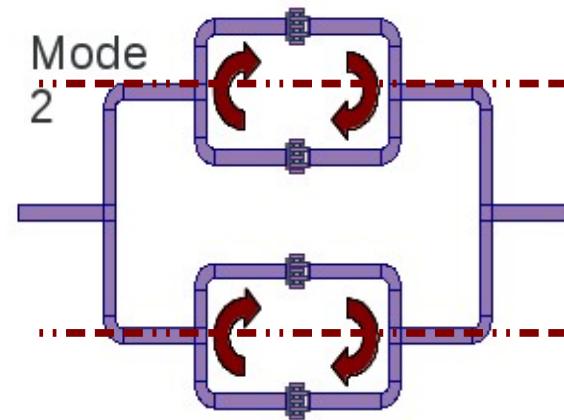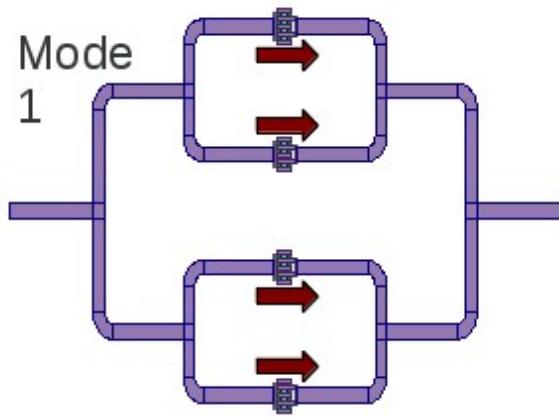

**Four modes are found**

**Symmetry axes for each mode**




### Single-transistor approach:
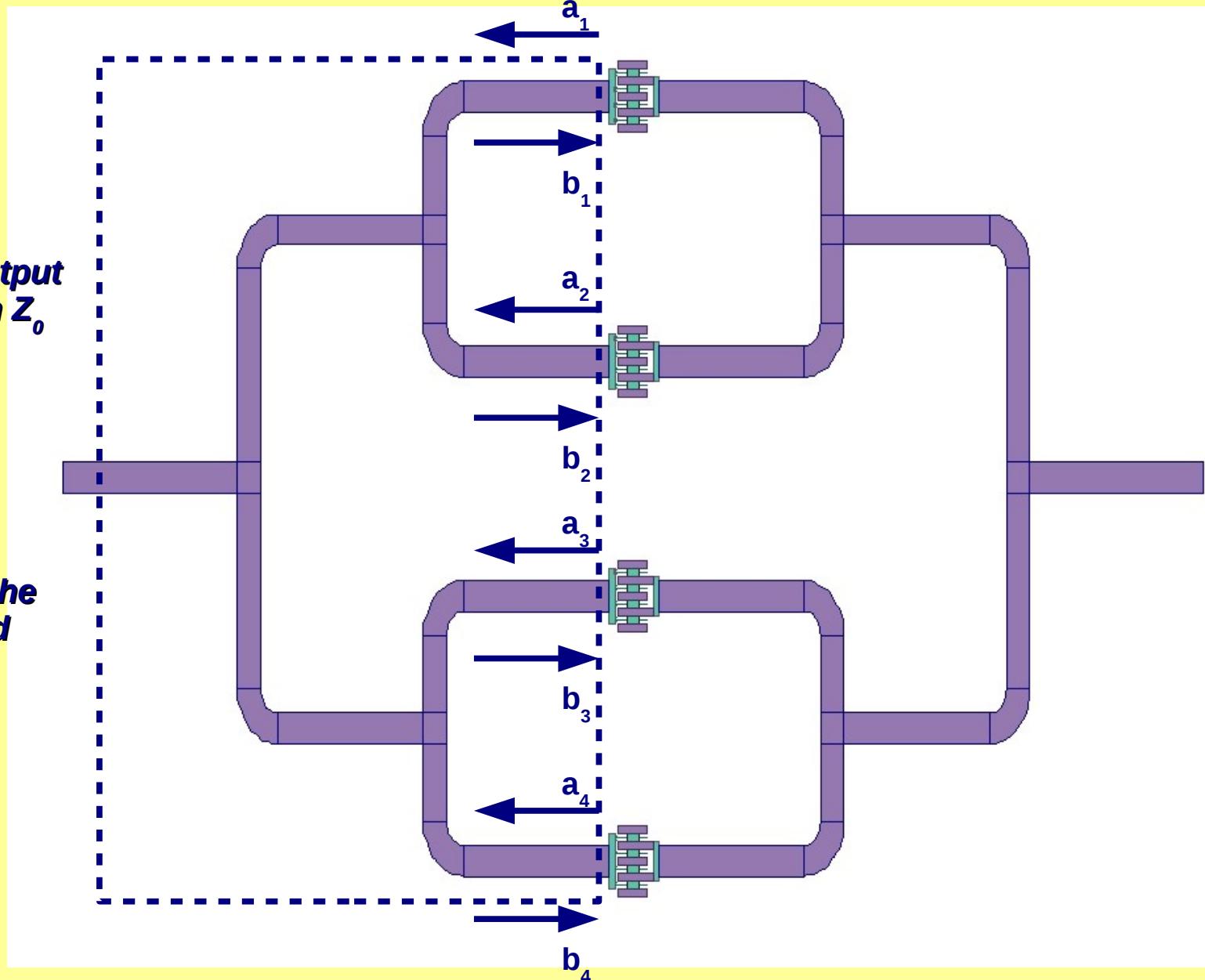
### **S-parameters of the matching networks**

The input and output ports are loaded with  $Z_0$

The symmetry of the networks is exploited





## Single-transistor approach:

$$S_{11} = S_{22} = S_{33} = S_{44} = \boxed{S_R}$$

$$S_{12} = S_{21} = S_{34} = S_{43} = \boxed{S_{MN}}$$

$$S_{13} = S_{14} = S_{23} = S_{24} = S_{31} = S_{32} = S_{41} = S_{42} = \boxed{S_{MF}}$$


$$b_1 = S_R \cdot a_1 + S_{MN} \cdot a_2 + \boxed{S_{MF} \cdot a_3 + S_{MF} \cdot a_4}$$

$$b_2 = S_{MN} \cdot a_1 + S_R \cdot a_2 + \boxed{S_{MF} \cdot a_3 + S_{MF} \cdot a_4}$$

$$b_3 = S_{MF} \cdot a_1 + S_{MF} \cdot a_2 + \boxed{S_R \cdot a_3 + S_{MN} \cdot a_4}$$

$$b_4 = S_{MF} \cdot a_1 + S_{MF} \cdot a_2 + \boxed{S_{MN} \cdot a_3 + S_R \cdot a_4}$$

## Modes identified from S-parameters

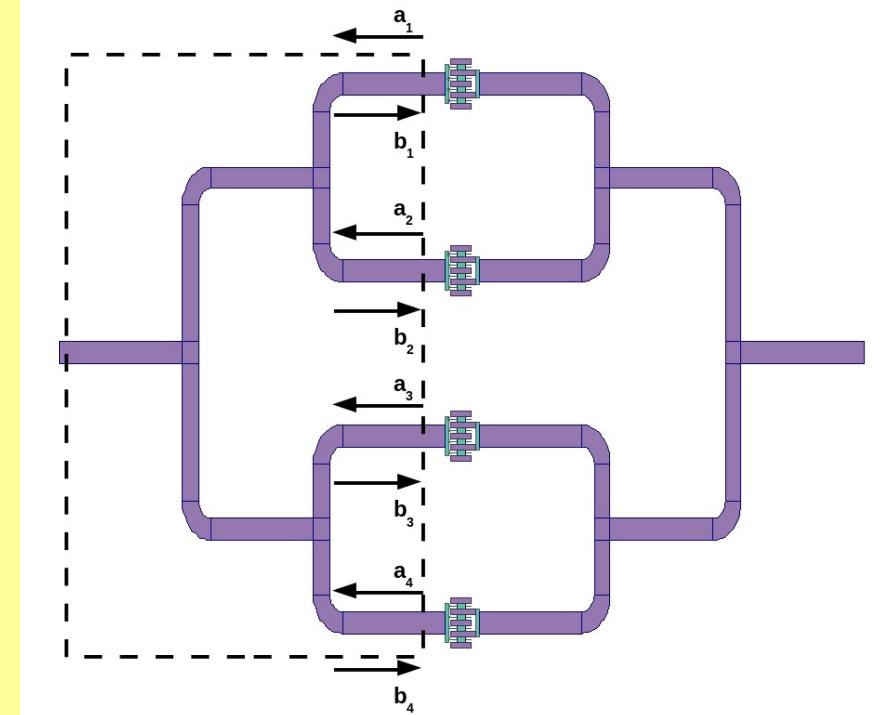

**Four modes:**

$$m_1 = [1, 1, 1, 1]$$

$$m_2 = [1, -1, 1, -1]$$

$$m_3 = [1, 1, -1, -1]$$

$$m_4 = [1, -1, -1, 1]$$

**E.g. - mode 3 :**

$$b_1 = b_2 = -b_3 = -b_4 = \boxed{b}$$

$$a_1 = a_2 = -a_3 = -a_4 = \boxed{a}$$

$$b = (S_R + S_{MN} - 2S_{MF}) \cdot a = \Gamma_3 \cdot a$$



## The stabilisation approach:

## Rizzoli's (Nyquist) method

Example – GaN power amplifier (Selex S.I.)


A high number of harmonics and frequency points are required

Results are sometimes confusing and unstable

Example: 10 harmonics of the large signal

22-port conversion matrix

47 frequency points

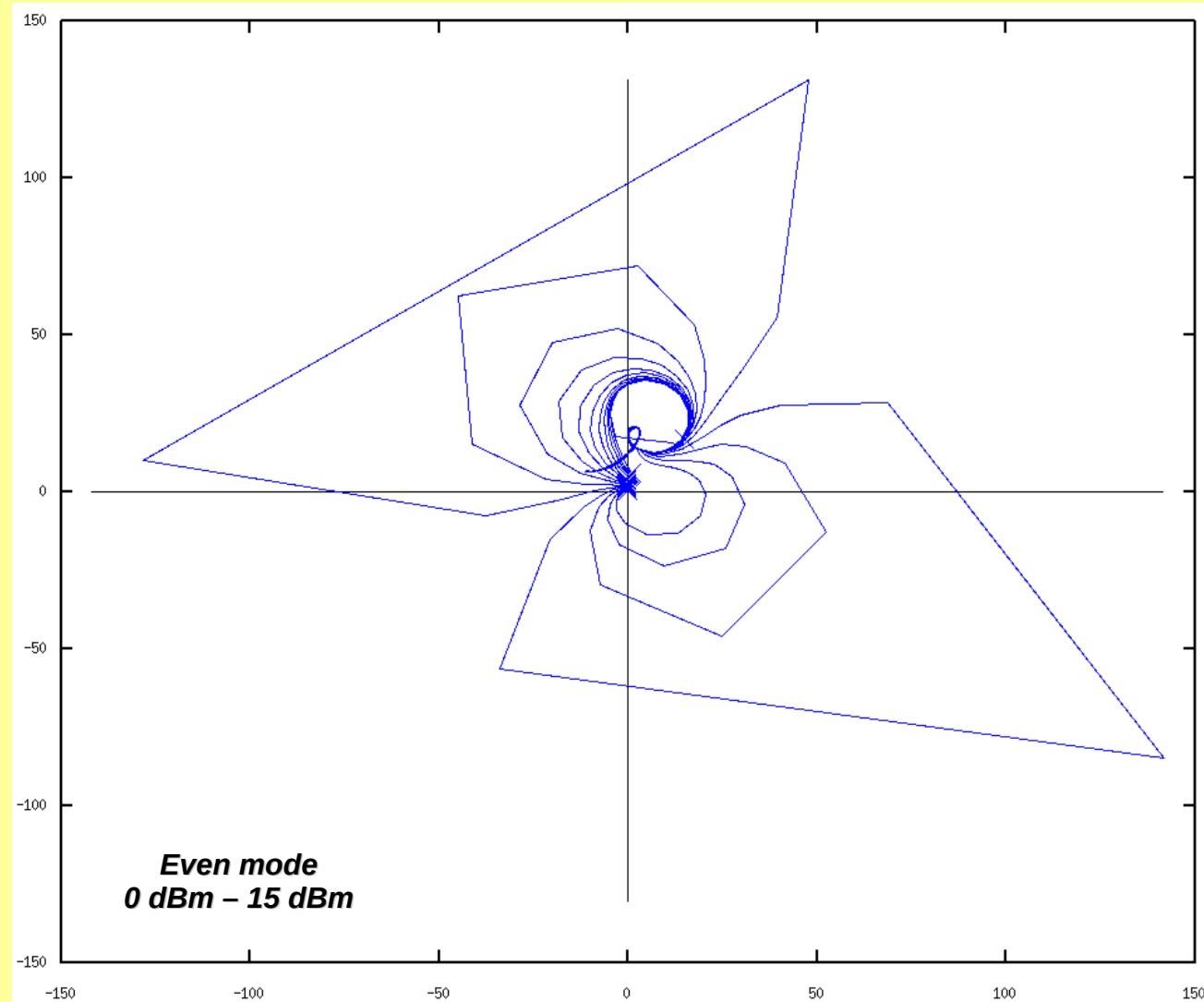




## The stabilisation approach:



## Rizzoli's (Nyquist) method

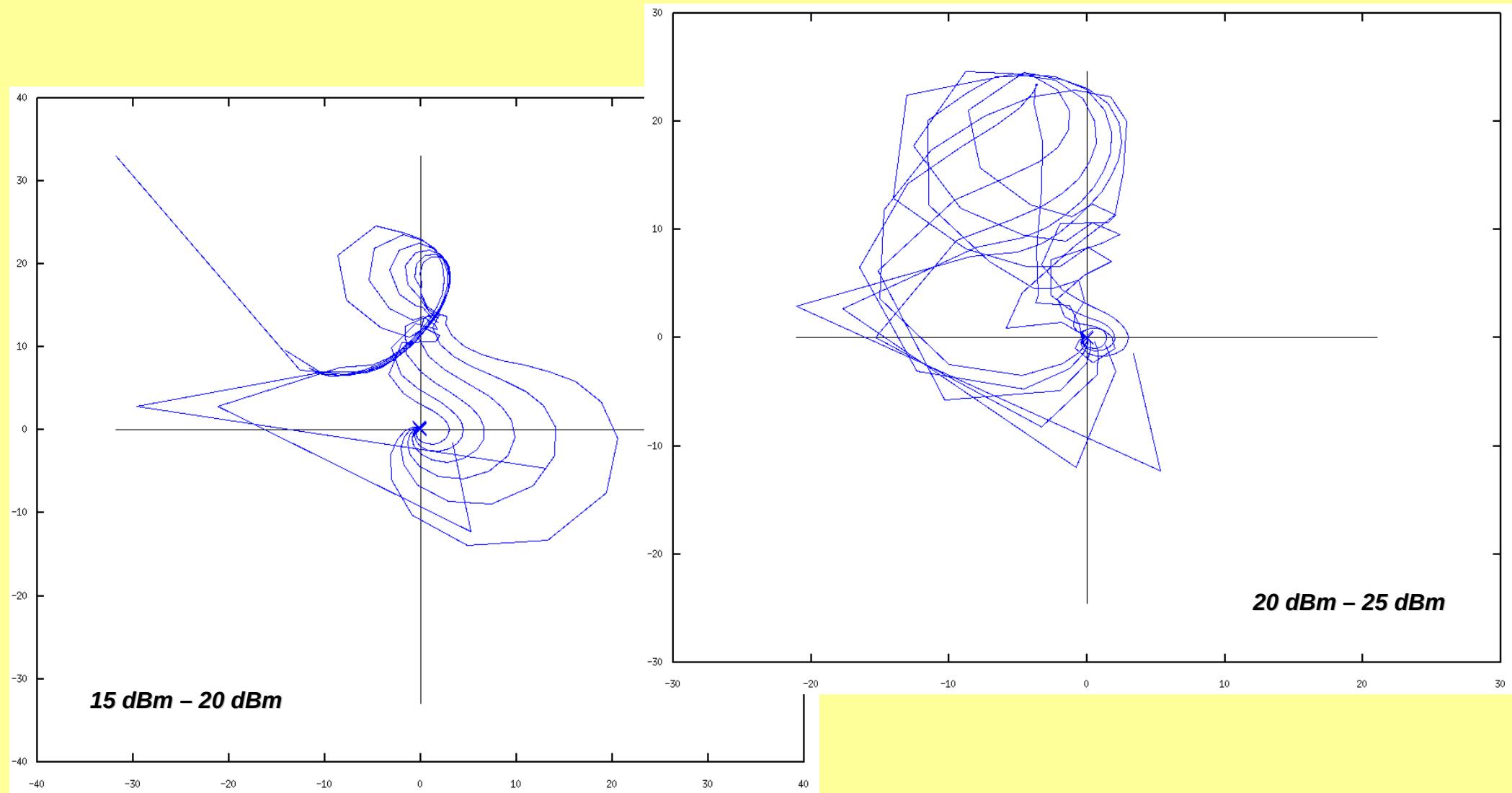Example – GaN power amplifier (Selex S.I.)



The stabilisation approach:**Collantes' (pole-zero identification) method**

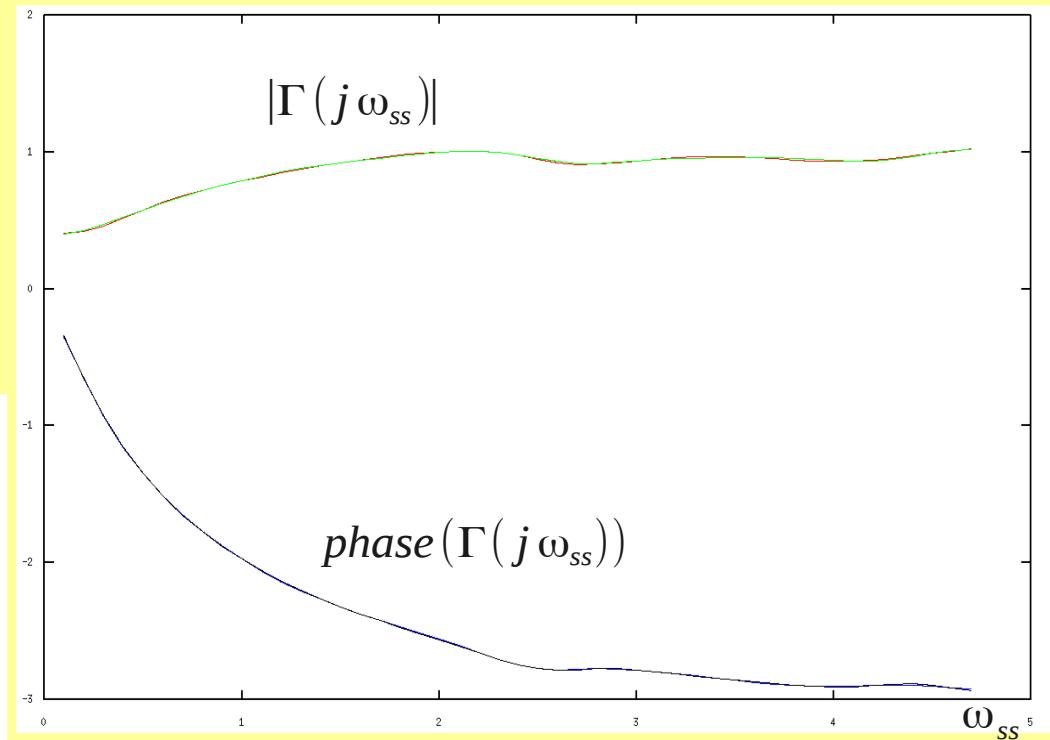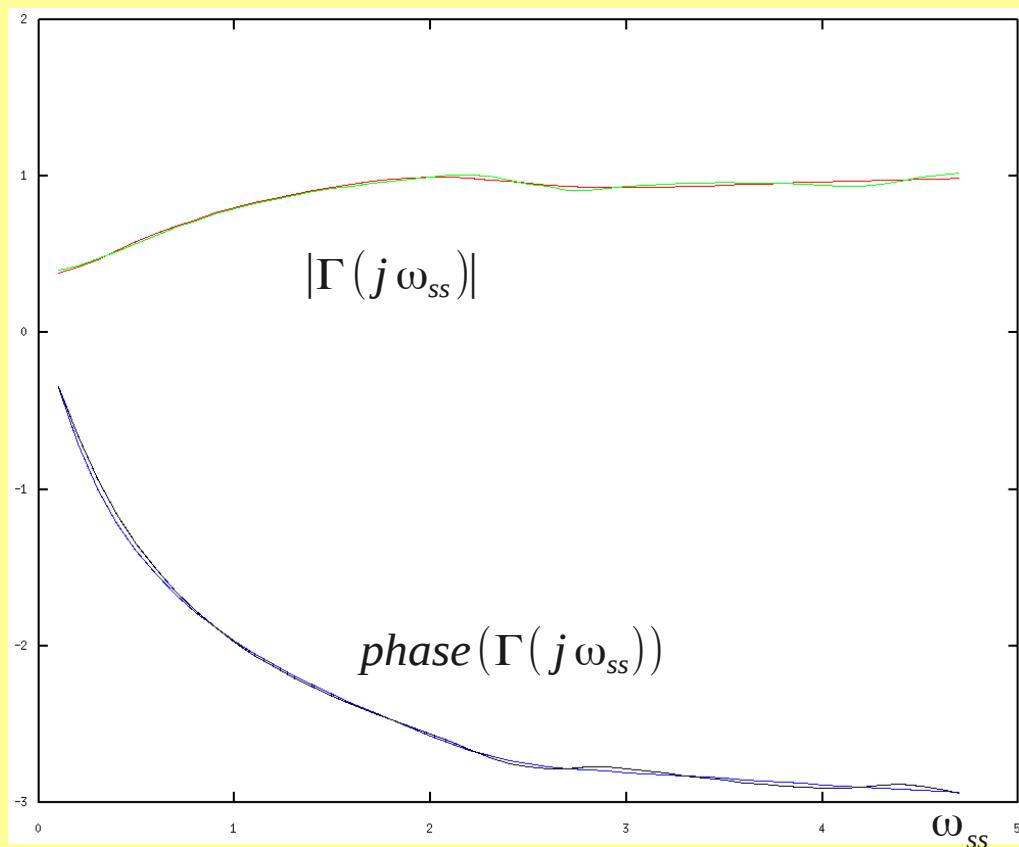Rational-function identification not unique



**10<sup>th</sup>-order**


**3<sup>rd</sup>-order**



The stabilisation approach:

**Collantes' (pole-zero identification) method**

**Pole-zero cancellation**

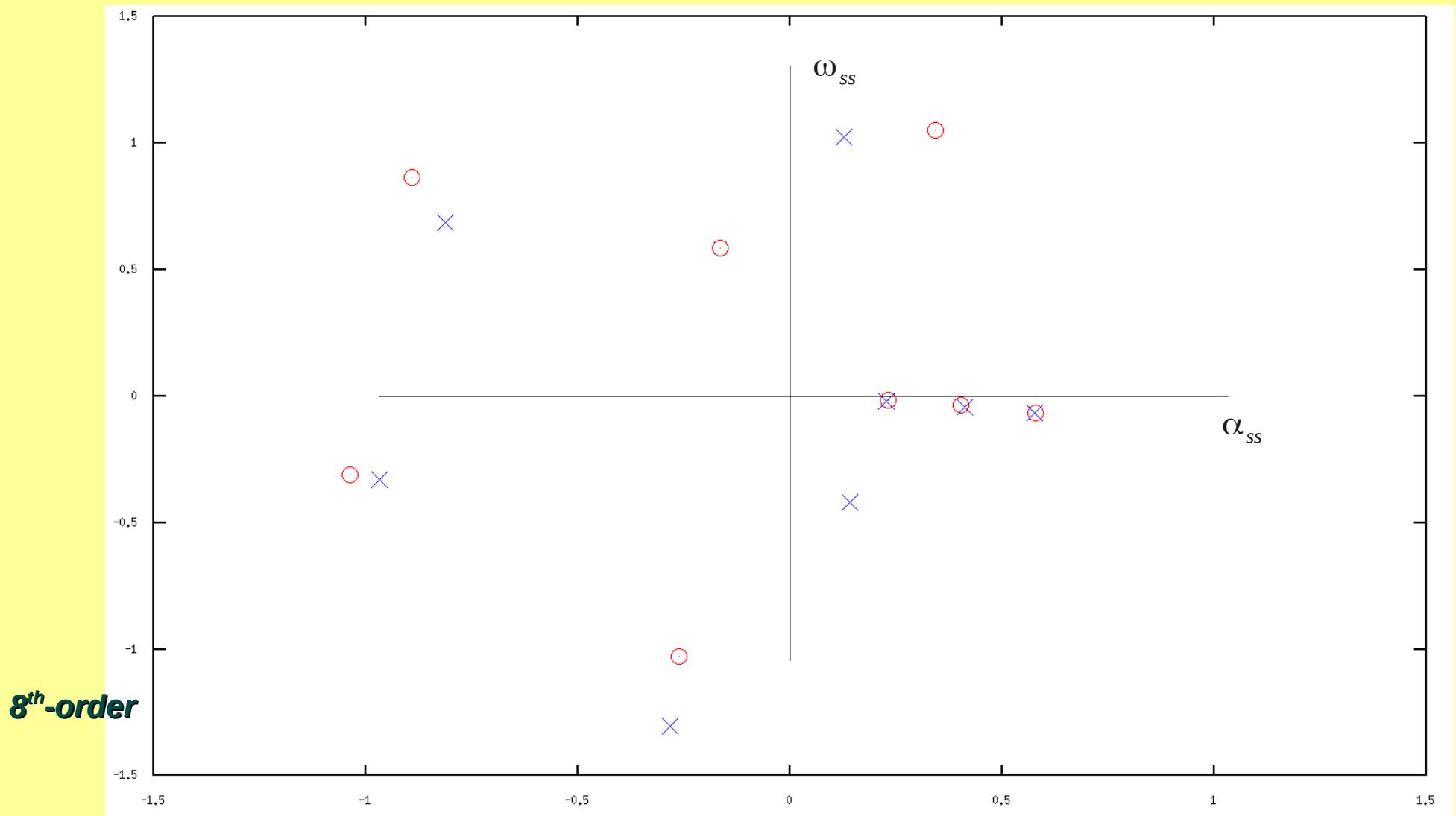



## Examples:

### **8-FET monolithic power amplifier**


**Two-stage, 9-GHz power amplifier from Selex S.I.**

**12 mm total periphery  
0.4- $\mu$ m GaAs HEMT**

**34 dBm output power at 1dB gain compression  
16 dB linear gain**

**Divider-by-two  
2-FET driver  
Two dividers-by-four  
8-FET power stage  
Combiner-by-eight**

**Driver stage linear**

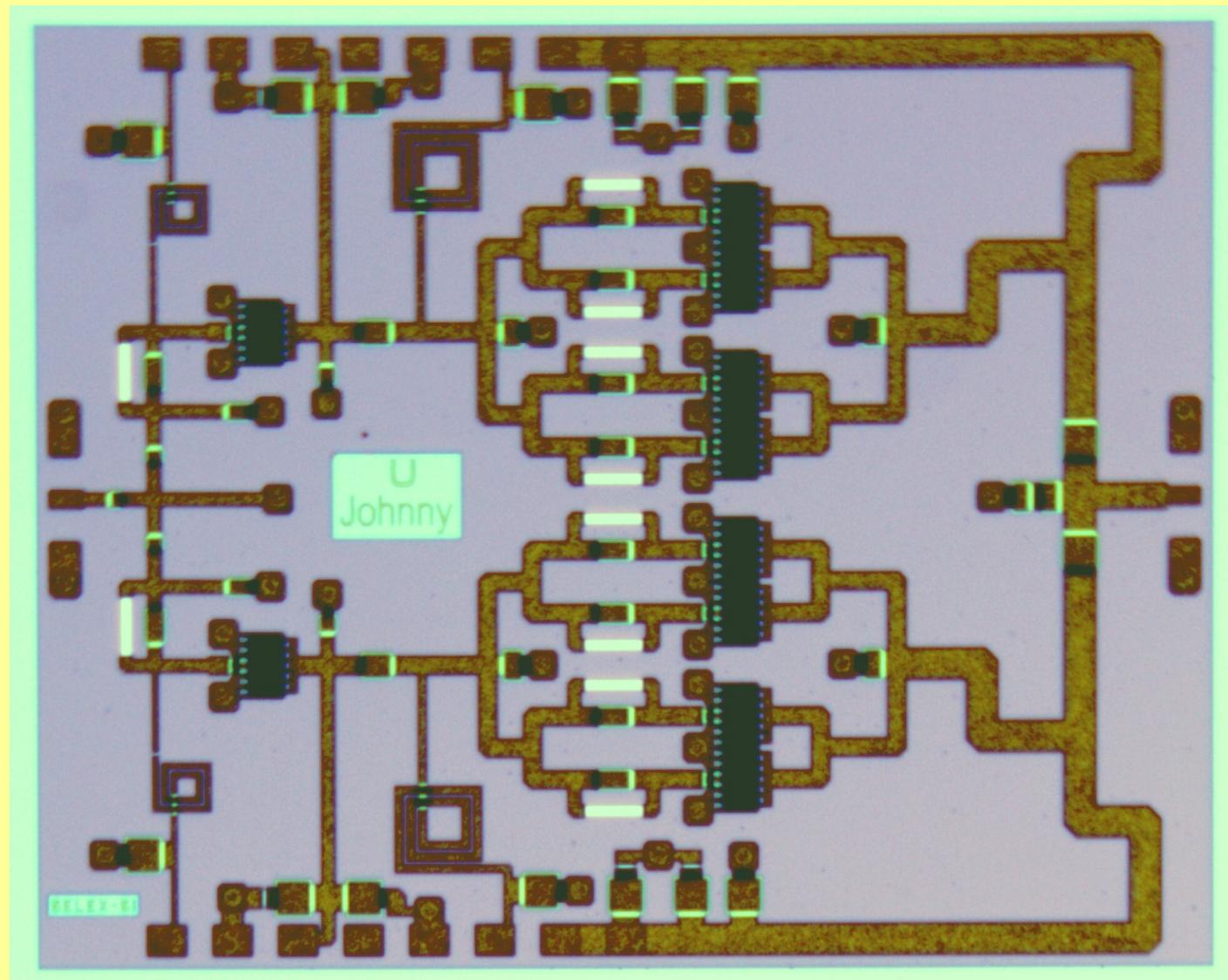




## Examples:
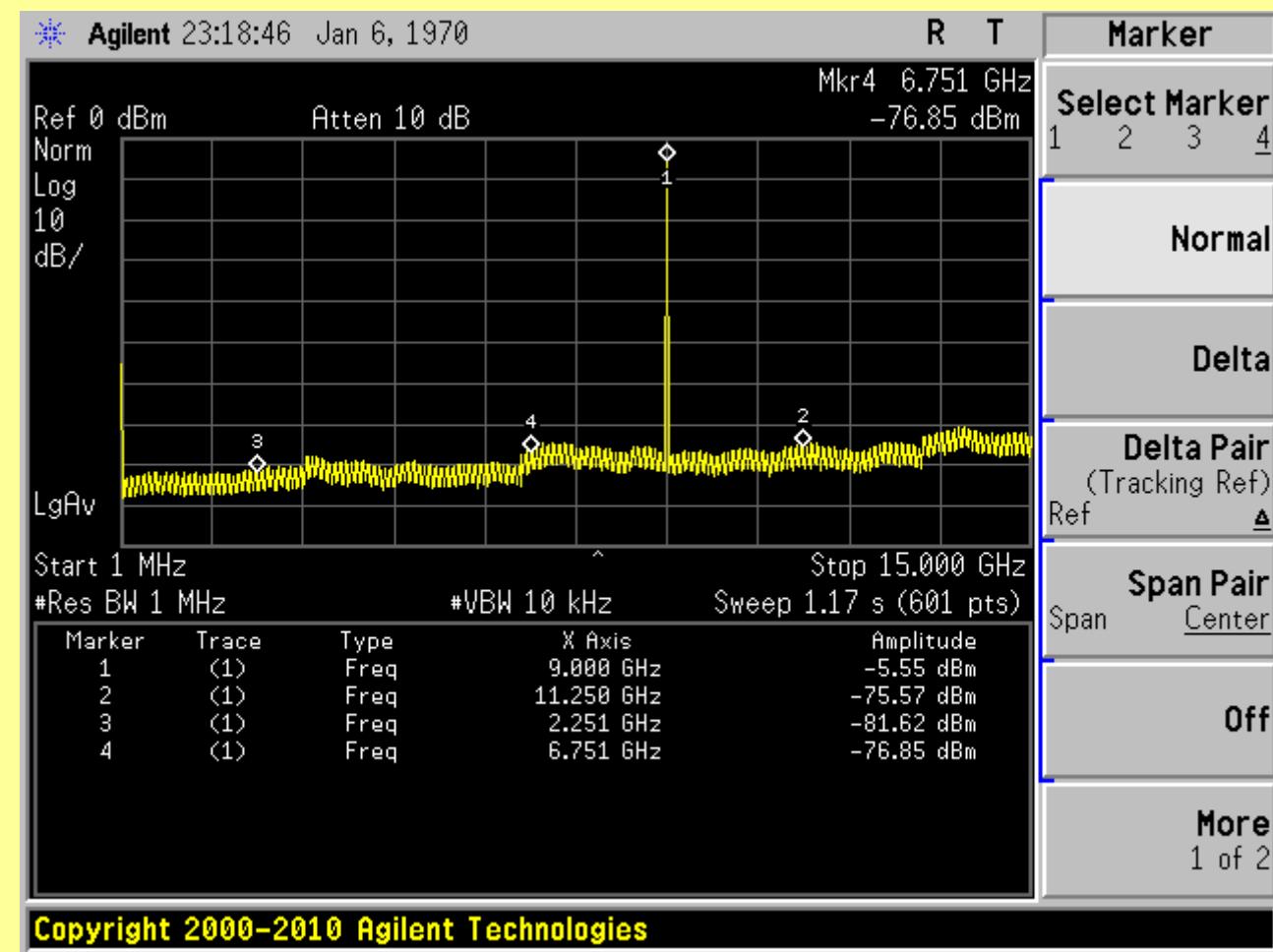
### 8-FET monolithic power amplifier

The amplifier is linear under small-signal conditions





## Examples:

### 8-FET monolithic power amplifier


A spurious signal appears under large-signal drive  
(Pin = 15 dBm)

The spurious frequencies are correlated

$f_s$

$f_0 - f_s$

$f_0 + f_s$


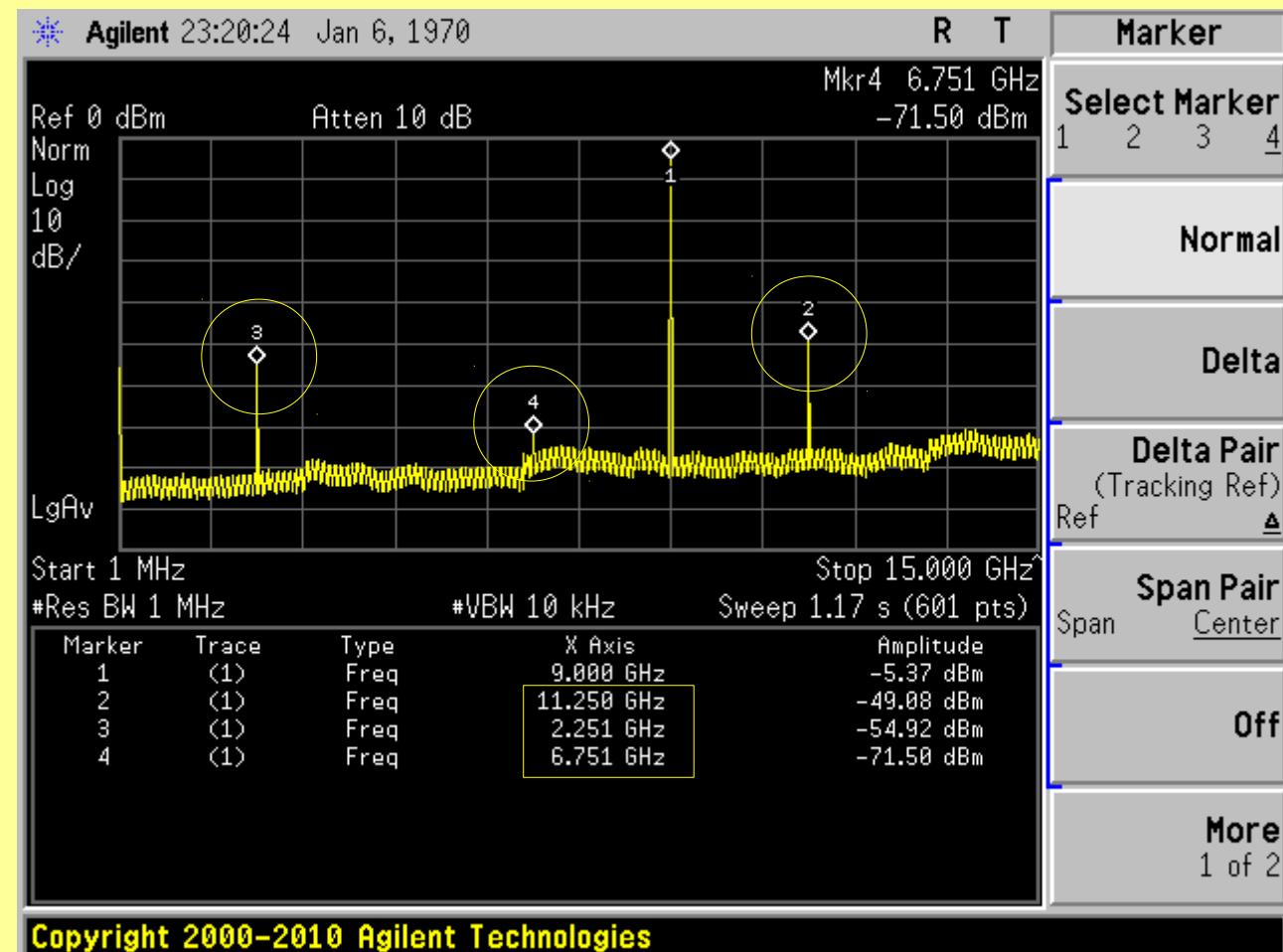




## Examples:

**The load falls into the unstable area**

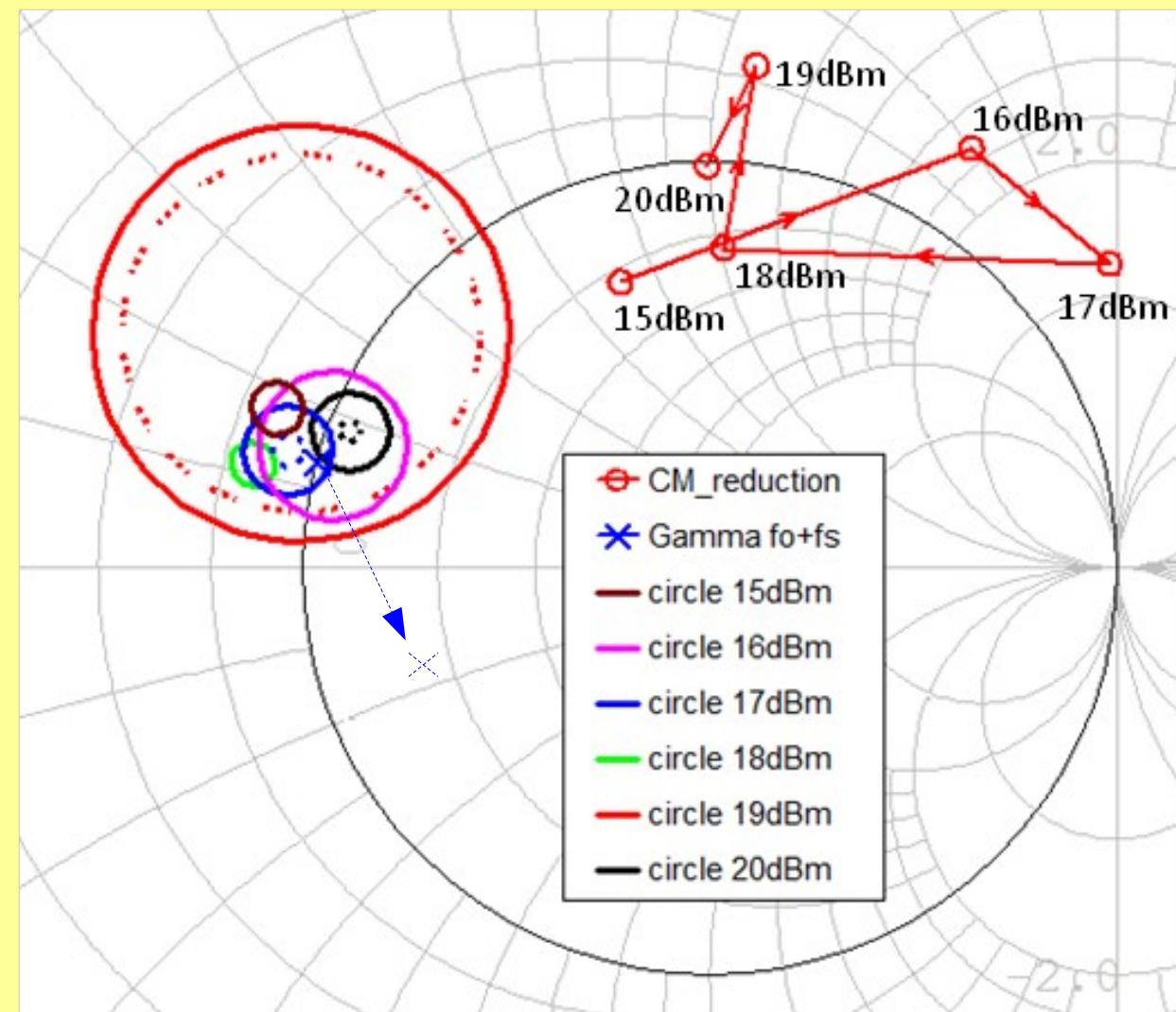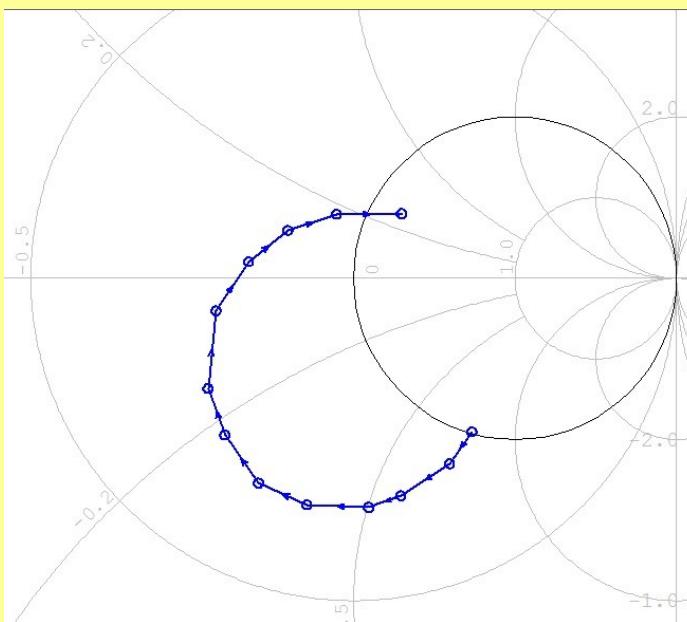**The one-port stability criterion (Lee) shows instability**



**Solution: move the load outside of the unstable area**





## Examples:

**Two versions (600 MHz):**


**First amplifier stable under small- and large-signal drive**

**Second amplifier redesigned for large-signal instability**
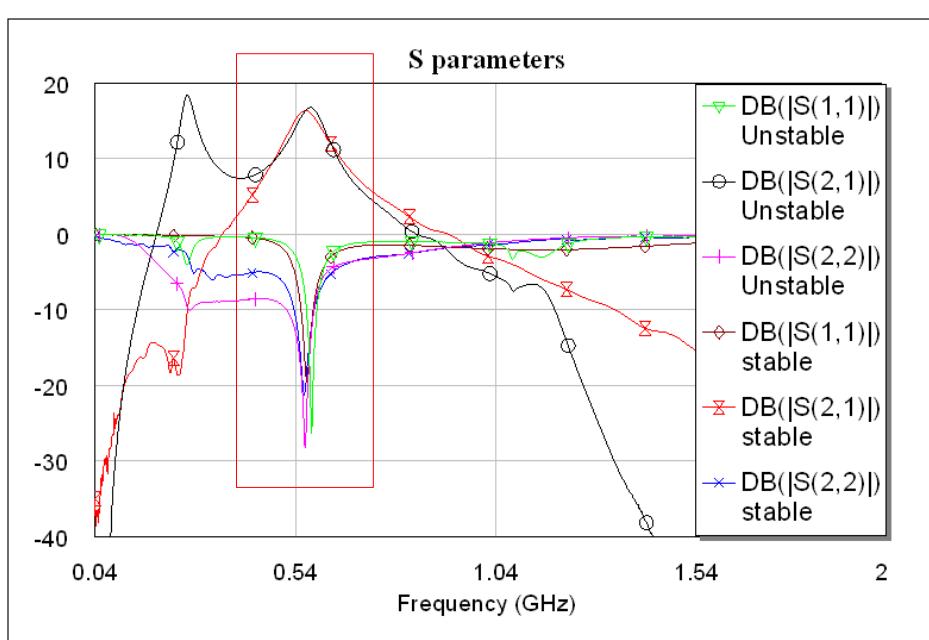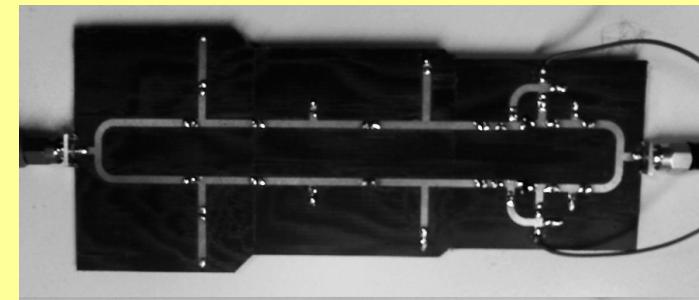
## **2-device hybrid balanced power amplifier**



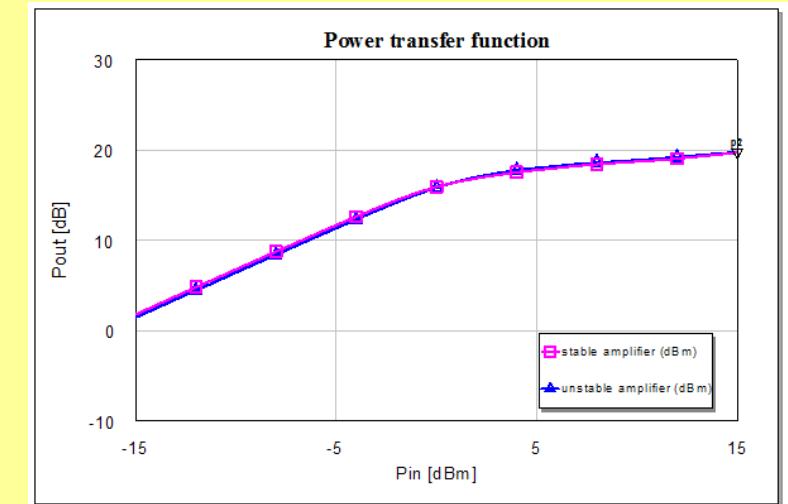**Linear performances very close at large-signal frequency**




**Simulated output power are very close**




## Examples:

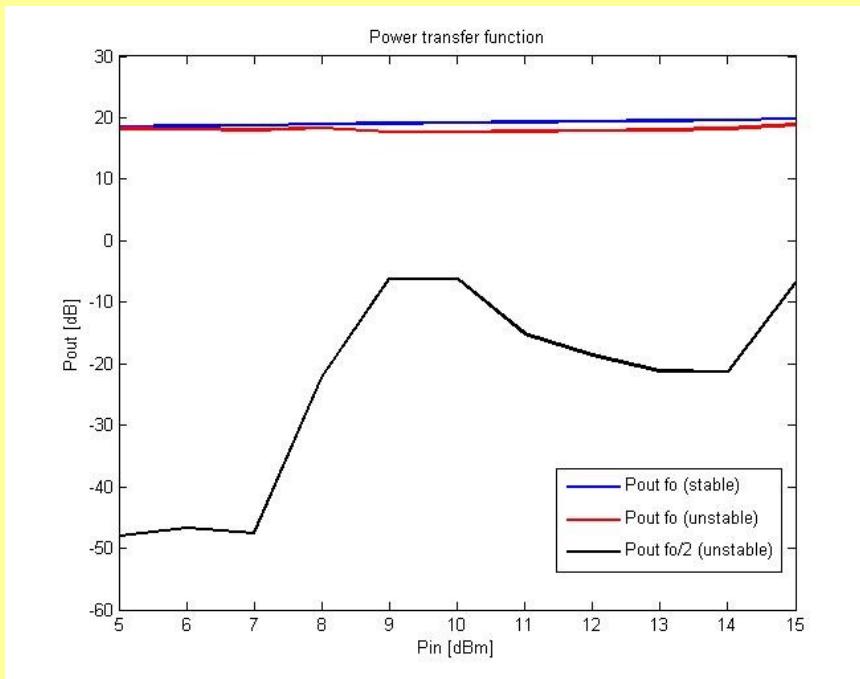
### 2-FET hybrid balanced power amplifier



Measured output power very different

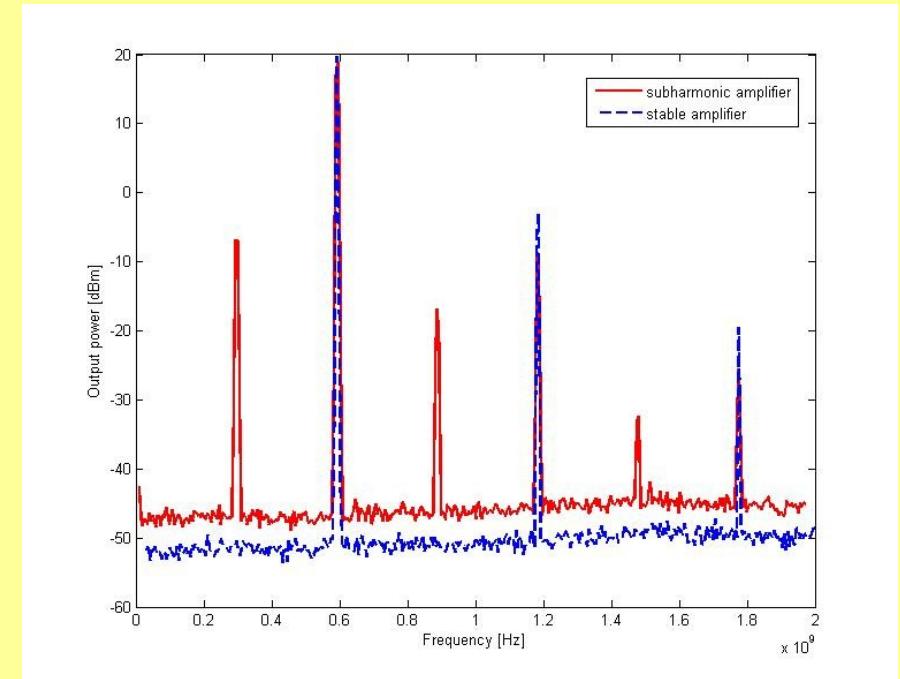

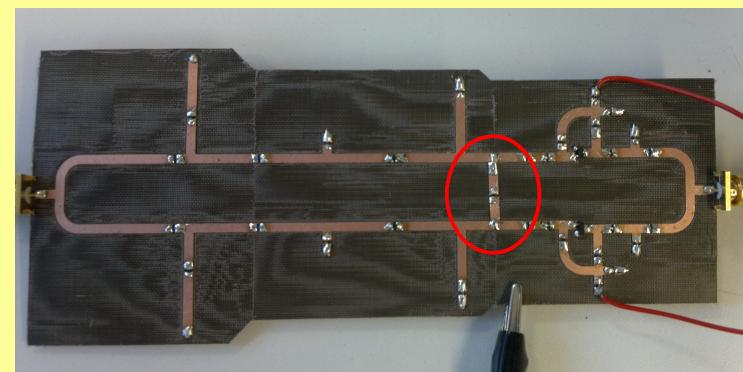Spectra show a spurious signal at  $f_o / 2$



Instability suppressed with a shunt resistance



## Conclusions:

- \* ***Stability under large-signal conditions can be addressed via the conversion matrix***
  
- \* ***Poles of a conversion function can be located and moved by optimisation***
  
- \* ***Stability can be enforced by direct design of loads in stable / unstable regions of the Smith Chart***